

# Chapter 2




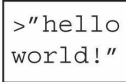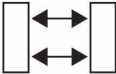
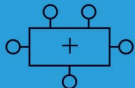

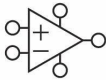


## ***Digital Design and Computer Architecture, 2<sup>nd</sup> Edition***

---

David Money Harris and Sarah L. Harris

# Chapter 2 :: Topics


- Introduction
- Boolean Equations
- Boolean Algebra
- From Logic to Gates
- Multilevel Combinational Logic
- X's and Z's, Oh My
- Karnaugh Maps
- Combinational Building Blocks
- Timing

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
<b>Logic</b>	
Digital Circuits	
Analog Circuits	
Devices	
Physics	
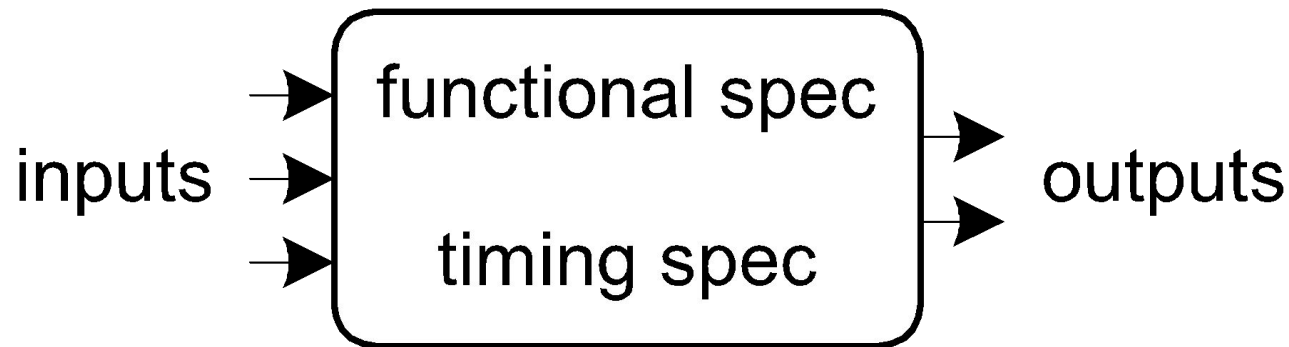
# Introduction


A logic circuit is composed of:

- Inputs
- Outputs
- Functional specification
- Timing specification



 
# Circuits

- Nodes
  - Inputs:  $A, B, C$
  - Outputs:  $Y, Z$
  - Internal:  $n1$
- Circuit elements
  - $E1, E2, E3$
  - Each a circuit



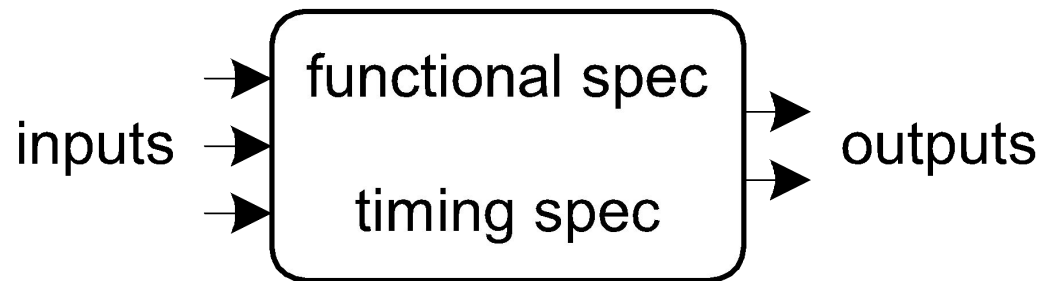
# Types of Logic Circuits

- **Combinational Logic**
  - Memoryless
  - Outputs determined by current values of inputs
- **Sequential Logic**
  - Has memory
  - Outputs determined by previous and current values of inputs


 
# Rules of Combinational Composition


- Every element is combinational
- Every node is either an input or connects to *exactly one* output
- The circuit contains no cyclic paths
- **Example:**



# Boolean Equations

- Functional specification of outputs in terms of inputs
- **Example:**  $S = F(A, B, C_{in})$

$$C_{out} = F(A, B, C_{in})$$

 

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

# Some Definitions

- Complement: variable with a bar over it  
 $\bar{A}, \bar{B}, \bar{C}$
- Literal: variable or its complement  
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- Implicant: product of literals  
 $ABC, AC, BC$
- Minterm: product that includes all input variables  
 $ABC, ABC, ABC$
- Maxterm: sum that includes all input variables  
 $(A+B+C), (A+B+C), (A+B+C)$



# Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE
- Thus, a sum (OR) of products (AND terms)

<b>A</b>	<b>B</b>	<b>Y</b>	<b>minterm</b>	<b>minterm name</b>
0	0	0	$\overline{A} \overline{B}$	$m_0$
0	1	1	$\overline{A} B$	$m_1$
1	0	0	$A \overline{B}$	$m_2$
1	1	1	$A B$	$m_3$

$$Y = F(A, B) =$$

# Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE
- Thus, a sum (OR) of products (AND terms)

<b>A</b>	<b>B</b>	<b>Y</b>	<b>minterm</b>	<b>minterm name</b>
0	0	0	$\bar{A} \bar{B}$	$m_0$
0	1	1	$\bar{A} B$	$m_1$
1	0	0	$A \bar{B}$	$m_2$
1	1	1	$A B$	$m_3$

$$Y = F(A, B) =$$

# Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE
- Thus, a sum (OR) of products (AND terms)

<b>A</b>	<b>B</b>	<b>Y</b>	<b>minterm</b>	<b>minterm name</b>
0	0	0	$\bar{A} \bar{B}$	$m_0$
0	1	1	$\bar{A} B$	$m_1$
1	0	0	$A \bar{B}$	$m_2$
1	1	1	$A B$	$m_3$

$$Y = F(A, B) = \bar{A}B + AB = \Sigma(1, 3)$$

# Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row has a **maxterm**
- A maxterm is a sum (OR) of literals
- Each maxterm is FALSE for that row (and only that row)
- Form function by ANDing the maxterms for which the output is FALSE
- Thus, a product (AND) of sums (OR terms)

<b>A</b>	<b>B</b>	<b>Y</b>	<b>maxterm</b>	<b>maxterm name</b>
0	0	0	$A + B$	$M_0$
0	1	1	$A + \overline{B}$	$M_1$
1	0	0	$\overline{A} + B$	$M_2$
1	1	1	$\overline{A} + \overline{B}$	$M_3$

$$Y = F(A, B) = (A + B)(A + \overline{B}) = \Pi(0, 2)$$

# Boolean Equations Example

- You are going to the cafeteria for lunch
  - You won't eat lunch ( $\bar{E}$ )
  - If it's not open ( $\bar{O}$ ) or
  - If they only serve corndogs ( $C$ )
- Write a truth table for determining if you will eat lunch ( $E$ ).

$O$	$C$	$E$
0	0	
0	1	
1	0	
1	1	

# Boolean Equations Example

- You are going to the cafeteria for lunch
  - You won't eat lunch ( $\bar{E}$ )
  - If it's not open ( $\bar{O}$ ) or
  - If they only serve corndogs ( $C$ )
- Write a truth table for determining if you will eat lunch ( $E$ ).

$O$	$C$	$E$
0	0	0
0	1	0
1	0	1
1	1	0

# SOP & POS Form

- SOP – sum-of-products

$O$	$C$	$E$	minterm	
0	0		$\overline{O}$	$\overline{C}$
0	1		$\overline{O}$	$C$
1	0		$O$	$\overline{C}$
1	1		$O$	$C$

- POS – product-of-sums

$O$	$C$	$E$	maxterm		
0	0		$O$	+	$C$
0	1		$O$	+	$\overline{C}$
1	0		$\overline{O}$	+	$C$
1	1		$\overline{O}$	+	$\overline{C}$

# SOP & POS Form

- SOP – sum-of-products

<i>O</i>	<i>C</i>	<i>E</i>	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

$$E = O\overline{C}$$

$$= \Sigma(2)$$

- POS – product-of-sums

<i>O</i>	<i>C</i>	<i>E</i>	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

$$E = (O + C)(O + \overline{C})(\overline{O} + \overline{C})$$

$$= \Pi(0, 1, 3)$$



# Boolean Algebra

- Axioms and theorems to **simplify** Boolean equations
- Like regular algebra, but simpler: variables have only two values (1 or 0)
- **Duality** in axioms and theorems:
  - ANDs and ORs, 0's and 1's interchanged

# Boolean Axioms

	Axiom		Dual		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$		Binary field
A2	$\bar{0} = 1$	A2'	$\bar{1} = 0$		NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$		AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$		AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$		AND/OR



	Theorem		Dual		Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$		Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$		Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$		Idempotency
T4		$\bar{\bar{B}} = B$			Involution
T5	$B \bullet \bar{B} = 0$	T5'	$B + \bar{B} = 1$		Complements

# T1: Identity Theorem

- $B \cdot 1 = B$
- $B + 0 = B$

# T1: Identity Theorem

- $B \cdot 1 = B$
- $B + 0 = B$

 
 


# T2: Null Element Theorem

- $B \cdot 0 = 0$
- $B + 1 = 1$

# T2: Null Element Theorem

- $B \cdot 0 = 0$
- $B + 1 = 1$

 
 


# T3: Idempotency Theorem

- $B \cdot B = B$
- $B + B = B$

# T3: Idempotency Theorem

- $B \cdot B = B$
- $B + B = B$

  




# T4: Identity Theorem

- $\overline{\overline{B}} = B$

# T4: Identity Theorem

- $\overline{\overline{B}} = B$


 


# T5: Complement Theorem

- $B \cdot \bar{B} = 0$
- $B + \bar{B} = 1$
  
# T5: Complement Theorem

- $B \cdot \bar{B} = 0$
- $B + \bar{B} = 1$



# Boolean Theorems Summary

	Theorem		Dual	Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements

# Boolean Theorems of Several Vars

	Theorem		Dual	Name
T6	$B \cdot C = C \cdot B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \cdot C) \cdot D = B \cdot (C \cdot D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \cdot C) + (B \cdot D) = B \cdot (C + D)$	T8'	$(B + C) \cdot (B + D) = B + (C \cdot D)$	Distributivity
T9	$B \cdot (B + C) = B$	T9'	$B + (B \cdot C) = B$	Covering
T10	$(B \cdot C) + (B \cdot \overline{C}) = B$	T10'	$(B + C) \cdot (B + \overline{C}) = B$	Combining
T11	$(B \cdot C) + (\overline{B} \cdot D) + (C \cdot D)$ $= B \cdot C + \overline{B} \cdot D$	T11'	$(B + C) \cdot (\overline{B} + D) \cdot (C + D)$ $= (B + C) \cdot (\overline{B} + D)$	Consensus
T12	$\overline{B_0 \cdot B_1 \cdot B_2 \dots}$ $= (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots}$ $= (\overline{B_0} \cdot \overline{B_1} \cdot \overline{B_2} \dots)$	De Morgan's Theorem

**Note:** T8' differs from traditional algebra: OR (+) distributes over AND (•)

# Simplifying Boolean Equations

## Example 1:

$$Y = AB + \bar{A}B$$

# Simplifying Boolean Equations

## Example 1:

$$\begin{aligned} Y &= AB + \bar{A}B \\ &= B(A + \bar{A}) \quad \text{T8} \\ &= B(1) \quad \text{T5'} \\ &= B \quad \text{T1} \end{aligned}$$



# Simplifying Boolean Equations

## Example 2:

$$Y = A(AB + ABC)$$

# Simplifying Boolean Equations

## Example 2:

$$Y = A(AB + ABC)$$

$$= A(AB(1 + C)) \quad T8$$

$$= A(AB(1)) \quad T2'$$



$$= A(AB) \quad T1$$

$$= (AA)B \quad T7$$



$$= AB \quad T3$$
  
# DeMorgan's Theorem

- $Y = \overline{AB} = \overline{A} + \overline{B}$



 
 
- $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$



# Bubble Pushing



- **Backward:**

- Body changes
- Adds bubbles to inputs

  


- **Forward:**

- Body changes
- Adds bubble to output

  

 
# Bubble Pushing

- What is the Boolean expression for this circuit?


 
# Bubble Pushing


- What is the Boolean expression for this circuit?




$$Y = AB + CD$$
 
# Bubble Pushing Rules

- Begin at output, then work toward inputs
- Push bubbles on final output back
- Draw gates in a form so bubbles cancel




# Bubble Pushing Example


 







# Bubble Pushing Example

 

# Bubble Pushing Example

  


# Bubble Pushing Example

   

$$Y = \overline{A}BC + \overline{D}$$
 
# From Logic to Gates

- Two-level logic: ANDs followed by ORs
- Example:  $Y = \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + A\overline{B}C$




# Circuit Schematics Rules

- Inputs on the left (or top)
- Outputs on right (or bottom)
- Gates flow from left to right
- Straight wires are best


# Circuit Schematic Rules (cont.)

- Wires always connect at a T junction
- A dot where wires cross indicates a connection between the wires
- Wires crossing *without* a dot make no connection


wires connect  
at a T junction

 

wires connect  
at a dot

 

 
wires crossing  
without a dot do  
not connect



# Multiple-Output Circuits

 - Example: Priority Circuit**

Output asserted  
corresponding to  
most significant  
TRUE input




$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0				
0	0	0	1				1
0	0	1	0			1	
0	0	1	1			1	
0	1	0	0		1		
0	1	0	1		1		
0	1	1	0		1		
0	1	1	1		1		
1	0	0	0	1			
1	0	0	1	1			
1	0	1	1	1			
1	1	0	1	1			
1	1	1	0	1			
1	1	1	1	1			
1	1	1	1	1			

# Multiple-Output Circuits

 - Example: Priority Circuit**

Output asserted  
corresponding to  
most significant  
TRUE input




$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0
1	1	1	1	1	0	0	0



# Priority Circuit Hardware

$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

 


# Don't Cares

$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0
1	1	1	1	1	0	0	0

$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0
 
# Contention: X

- Contention: circuit tries to drive output to 1 **and** 0
  - Actual value somewhere in between
  - Could be 0, 1, or in forbidden zone
  - Might change with voltage, temperature, time, noise
  - Often causes excessive power dissipation




- **Warnings:**
  - Contention usually indicates a **bug**.
  - **X** is used for “don’t care” and contention - look at the context to tell them apart

# Floating: Z

- Floating, high impedance, open, high Z
- Floating output might be 0, 1, or somewhere in between
  - A voltmeter won't indicate whether a node is floating


## Tristate Buffer

 

$E$	$A$	$Y$
0	0	Z
0	1	Z
1	0	0
1	1	1
 
# Tristate Busses

- Floating nodes are used in tristate busses
  - Many different drivers
  - Exactly one is active at once



# Karnaugh Maps (K-Maps)

- Boolean expressions can be minimized by combining terms
- K-maps minimize equations graphically
- $PA + P\bar{A} = P$

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	0	0	0

		AB			
		00	01	11	10
C	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

# K-Map

- Circle 1's in adjacent squares
- In Boolean expression, include only literals whose true and complement form are *not* in the circle

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	0	0	0

$$Y = AB$$

# 3-Input K-Map

Y C		AB		00	01	11	10
		0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$A\bar{B}\bar{C}$	$A\bar{B}C$	
		1	$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$	

Truth Table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

K-Map

Y C		AB		00	01	11	10
		0					
		1					





# 3-Input K-Map

		Y				
		C				
		AB	00	01	11	10
C	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$A\bar{B}\bar{C}$	$A\bar{B}C$	
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$	

Truth Table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

K-Map

		Y				
		C				
		AB	00	01	11	10
C	0	0	1	1	0	
	1	0	1	0	0	

$$Y = \bar{A}B + B\bar{C}$$

# K-Map Definitions

- **Complement:** variable with a bar over it  
 $\bar{A}, \bar{B}, \bar{C}$
- **Literal:** variable or its complement  
 $\bar{A}, A, B, \bar{B}, C, \bar{C}$
- **Implicant:** product of literals  
 $ABC, AC, BC$
- **Prime implicant:** implicant corresponding to the largest circle in a K-map

# K-Map Rules

- Every 1 must be circled at least once
- Each circle must span a power of 2 (i.e. 1, 2, 4) squares in each direction
- Each circle must be as large as possible
- A circle may wrap around the edges
- A “don't care” (X) is circled only if it helps minimize the equation

# 4-Input K-Map

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Y CD \ AB		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				

# 4-Input K-Map

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Y CD \ AB		AB			
		00	01	11	10
00	00	1	0	0	1
	01	0	1	0	1
11	11	1	1	0	0
	10	1	1	0	1

# 4-Input K-Map

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Y		AB			
		00	01	11	10
CD	00	1	0	0	1
	01	0	1	0	1
	11	1	1	0	0
	10	1	1	0	1

$$Y = \bar{A}C + \bar{A}BD + A\bar{B}\bar{C} + \bar{B}\bar{D}$$

# K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Y CD \ AB		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				

# K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

		Y			
		AB			
CD		00	01	11	10
	00	1	0	X	1
01	0	X	X	1	
11	1	1	X	X	
10	1	1	X	X	



# K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Y		AB			
		00	01	11	10
CD	00	1	0	X	1
	01	0	X	X	1
	11	1	1	X	X
	10	1	1	X	X


$$Y = A + \bar{B}\bar{D} + C$$

# Combinational Building Blocks

- Multiplexers
- Decoders
 
# Multiplexer (Mux)

- Selects between one of  $N$  inputs to connect to output
- $\log_2 N$ -bit select input – control input
- Example: **2:1 Mux**



S	$D_1$	$D_0$	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

S	Y
0	$D_0$
1	$D_1$


# Multiplexer Implementations

- **Logic gates**

- Sum-of-products form


Y	$D_0 D_1$	00	01	11	10
S	0	0	0	1	1
1	0	1	1	0	0

$$Y = D_0 \bar{S} + D_1 S$$

 

- **Tristates**

 - For an N-input mux, use N tristates
- Turn on exactly one to select the appropriate input




# Logic using Multiplexers

- Using the mux as a lookup table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = AB$$

 

# Logic using Multiplexers


- Reducing the size of the mux

$$Y = AB$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


  

A	Y
0	0
1	B

 

 
# Decoders

- $N$  inputs,  $2^N$  outputs
- One-hot outputs: only one output HIGH at once



$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0


# Decoder Implementation

 



# Logic Using Decoders



- OR minterms

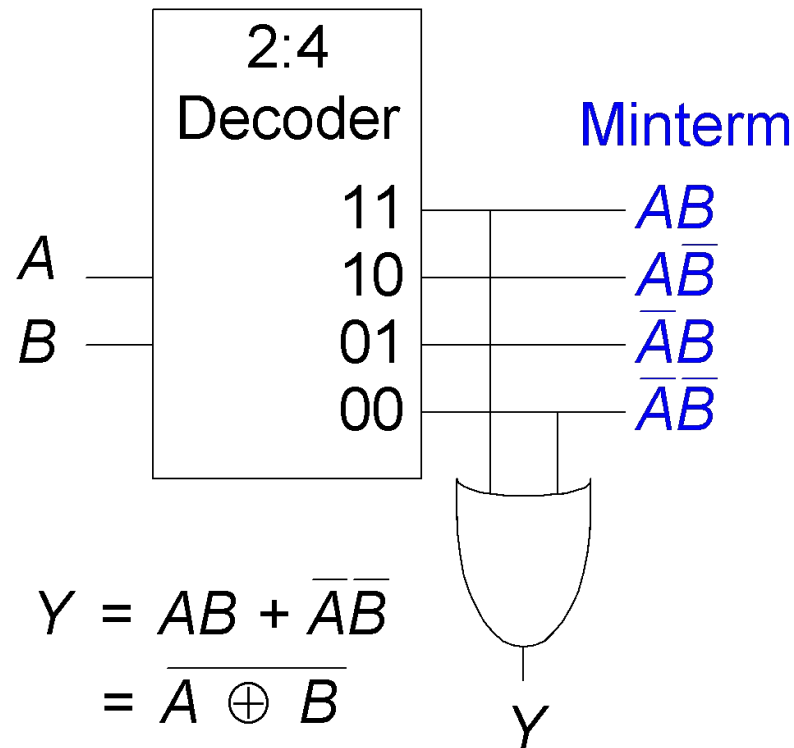

ENOUGH FOR TODAY!

  
# Timing

- Delay between input change and output changing
- How to build fast circuits?


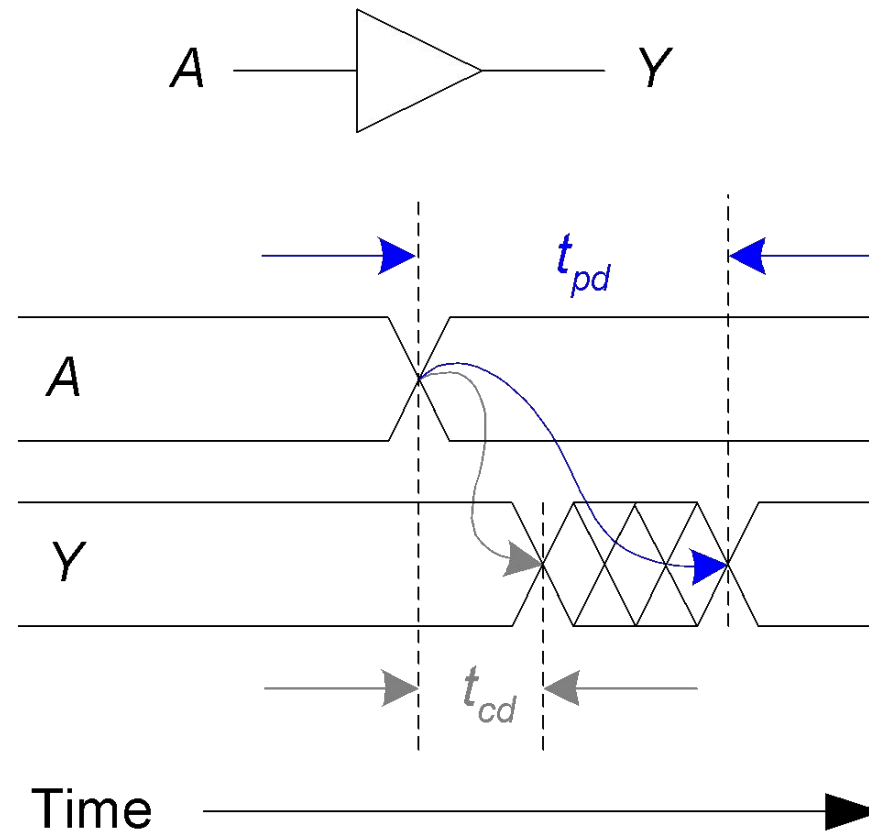
# Propagation & Contamination Delay


- **Propagation delay:**  $t_{pd}$  = max delay from input to output
- **Contamination delay:**  $t_{cd}$  = min delay from input to output



# Propagation & Contamination Delay

- Delay is caused by
  - Capacitance and resistance in a circuit
  - Speed of light limitation
- Reasons why  $t_{pd}$  and  $t_{cd}$  may be different:
  - Different rising and falling delays
  - Multiple inputs and outputs, some of which are faster than others
  - Circuits slow down when hot and speed up when cold

# Critical (Long) & Short Paths

 

**Critical (Long) Path:**  $t_{pd} = 2t_{pd\_AND} + t_{pd\_OR}$


**Short Path:**  $t_{cd} = t_{cd\_AND}$

# Glitches

- When a single input change causes an output to change multiple times
 
# Glitch Example

- What happens when  $A = 0$ ,  $C = 1$ ,  $B$  falls?





		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0



$$Y = \bar{A}\bar{B} + BC$$



# Glitch Example (cont.)

 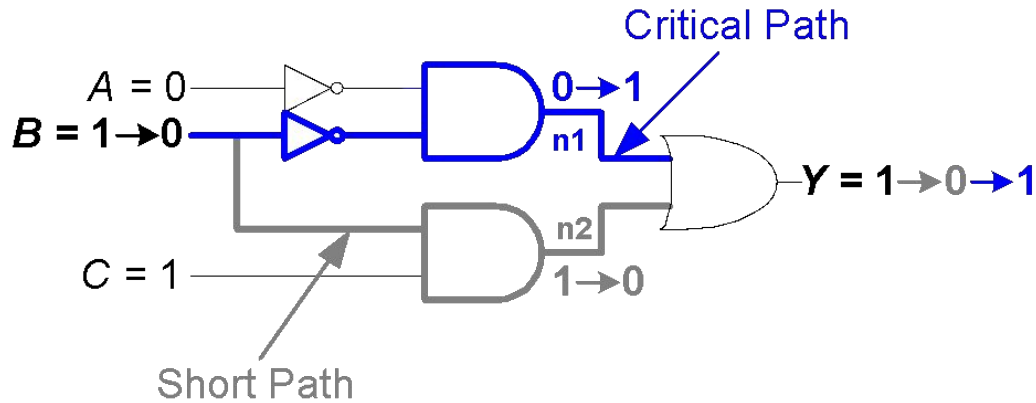

# Fixing the Glitch

  

# Why Understand Glitches?

- Glitches don't cause problems because of **synchronous design** conventions (see Chapter 3)
- It's important to **recognize** a glitch: in simulations or on oscilloscope
- Can't get rid of all glitches – simultaneous transitions on multiple inputs can also cause glitches