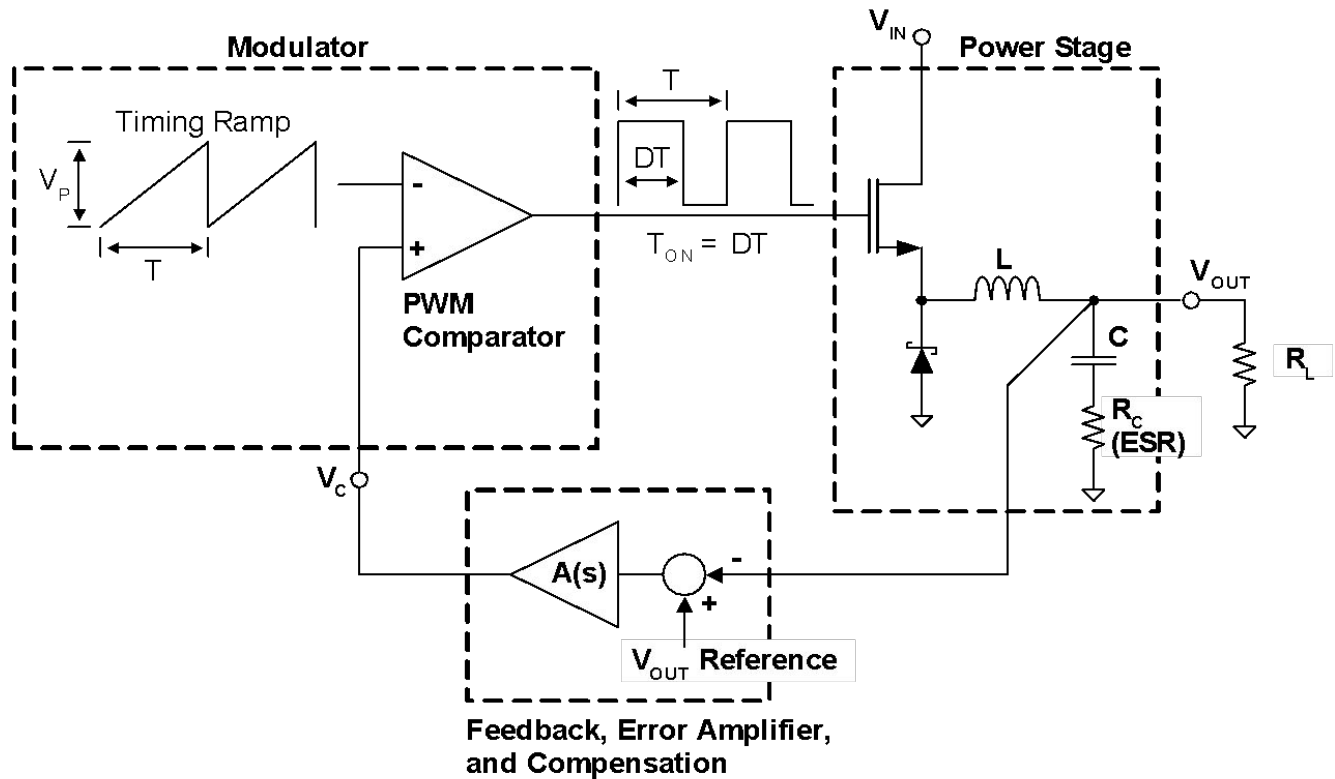


# ***Switching Power Supplies A to Z***

## ***Basic Switcher Architectures***


Thanks to John Bittner

# Voltage Mode Buck Regulator Basic Architecture



# Feedback, Error Amplifier, and Compensation – Two Types

**Gm Amp:**

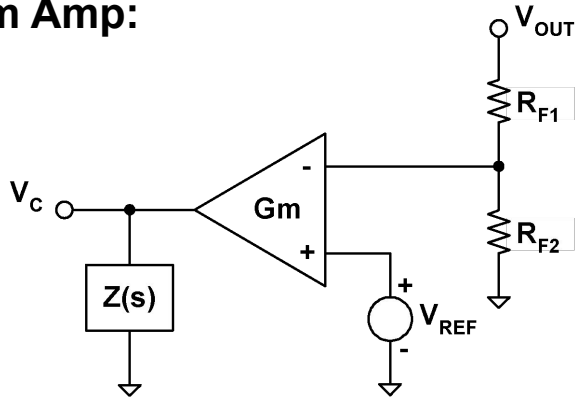


$$\frac{V_C}{V_{OUT}} = -\frac{R_{F2}}{R_{F1} + R_{F2}} \bullet Gm \bullet Z(s)$$

$$= -\frac{V_{REF}}{V_{OUT}} \bullet A(s) \quad A(s) = Gm \bullet Z(s)$$

Gain is a function of the feedback ratio, so regulator loop gain increases inversely with  $V_{OUT}$ . Gain is also affected by changes in  $A(s)$ .

**Op-Amp:**

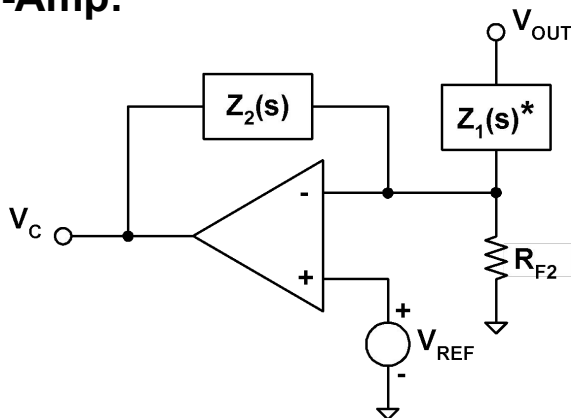

$$\frac{V_C}{V_{OUT}} = -\frac{Z_2(s)}{Z_1(s)}$$

Loop gain is independent of op-amp's open loop gain and the feedback ratio.

\*  $Z_1(s) = R_{F1}$  at DC:

$$\therefore V_{OUT} (DC) = V_{REF} \frac{R_{F1} + R_{F2}}{R_{F2}} \quad 3$$

# Voltage Mode Buck Regulator Loop Gain

---

- Modulator and Power Stage gain:

$$\frac{V_{OUT}}{V_C} = \frac{V_{IN}}{V_P} \bullet \frac{1 + sR_C C}{1 + s(R_C C + L/R_L) + s^2 LC}$$


- Feedback, Error Amplifier, and Compensation gain (Gm-type Error Amp):

$$\frac{V_C}{V_{OUT}} = -\frac{V_{REF}}{V_{OUT}} \bullet A(s)$$


- Regulator loop gain, H(s):

$$H(s) = \frac{V_{REF}}{V_{OUT}} \bullet A(s) \bullet \frac{V_{IN}}{V_P} \bullet \frac{1 + sR_C C}{1 + s^2(R_C C + L/R_L) + s^2 LC}$$
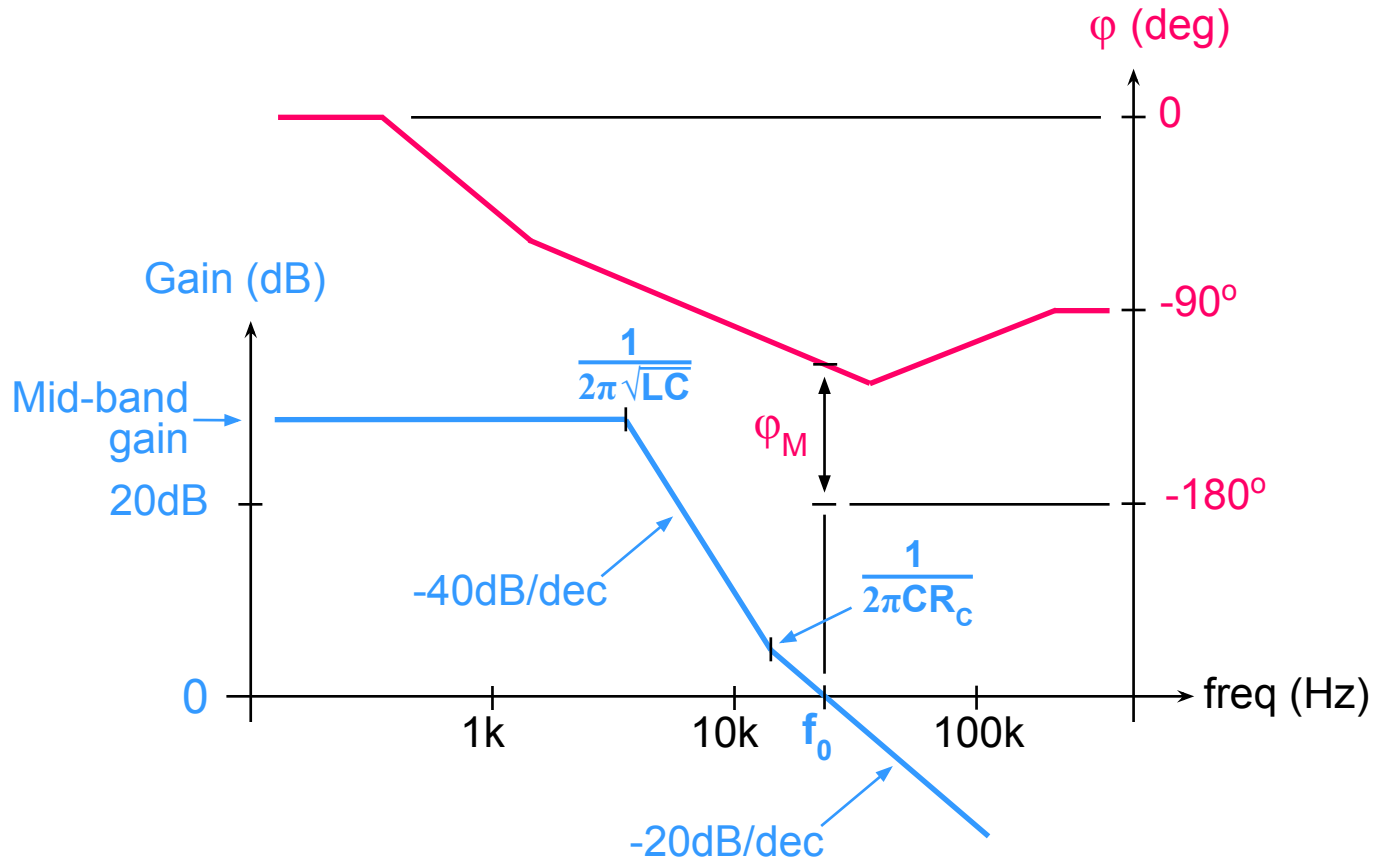
# Voltage-Mode Buck Regulator Frequency Response


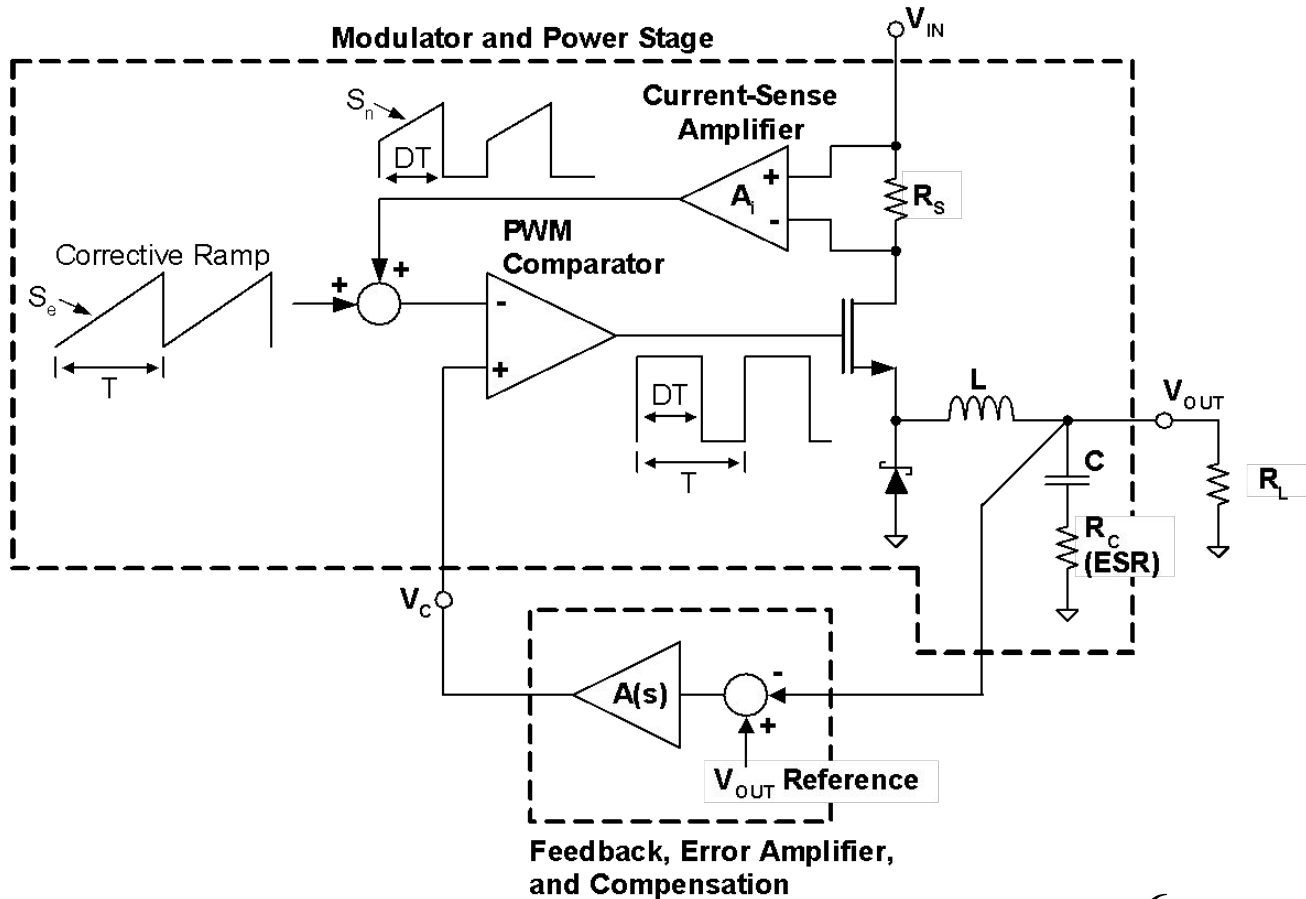
# Current Mode Buck Regulator Basic Architecture



# Current Mode Buck Regulator Loop Gain

- Gain of Modulator and Power Stage:

$$\frac{V_{OUT}}{V_C} = \frac{R_L}{R_i} \bullet \frac{1}{1 + \frac{R_L T}{L} (m_C D' - 0.5)} \bullet \frac{1 + sR_C C}{1 + \frac{s}{\omega_P}} \bullet \frac{1}{1 + \frac{s}{\omega_N Q_P} + \frac{s^2}{\omega_N^2}}$$

$$R_i = A_i \bullet R_s$$

$$D' = 1 - D$$

$$m_C = 1 + \frac{S_e}{S_n}$$

$S_e$  = corrective ramp slope

$S_n$  = positive slope current-sense waveform

$$\omega_P = \frac{1}{CR_L} + \frac{T}{LC} (m_C D' - 0.5)$$

$$\omega_N = 2\pi \bullet \left( \frac{f_{SW}}{2} \right) = \frac{\pi}{T}$$

$$Q_P = \frac{1}{\pi(m_C D' - 0.5)}$$

# Current Mode Buck Regulator Loop Gain

---

- Feedback, Error Amplifier, and Compensation gain (Gm-type Error Amp):

$$\frac{V_C}{V_{OUT}} = -\frac{V_{REF}}{V_{OUT}} \bullet A(s) \quad A(s) = Gm \bullet Z(s)$$

- Regulator loop gain:


$$H(s) = -\frac{V_{REF}}{V_{OUT}} \bullet A(s) \bullet \frac{R_L}{R_i} \bullet K \bullet \frac{1 + sR_c C}{1 + \frac{s}{\omega_p}} \bullet Fh(s)$$

$$K = \frac{1}{1 + \frac{R_L T_{sw}}{L} (m_c D' - 0.5)}$$


$$Fh(s) = \frac{1}{1 + \frac{s}{\omega_N Q_P} + \frac{s^2}{\omega_N^2}}$$



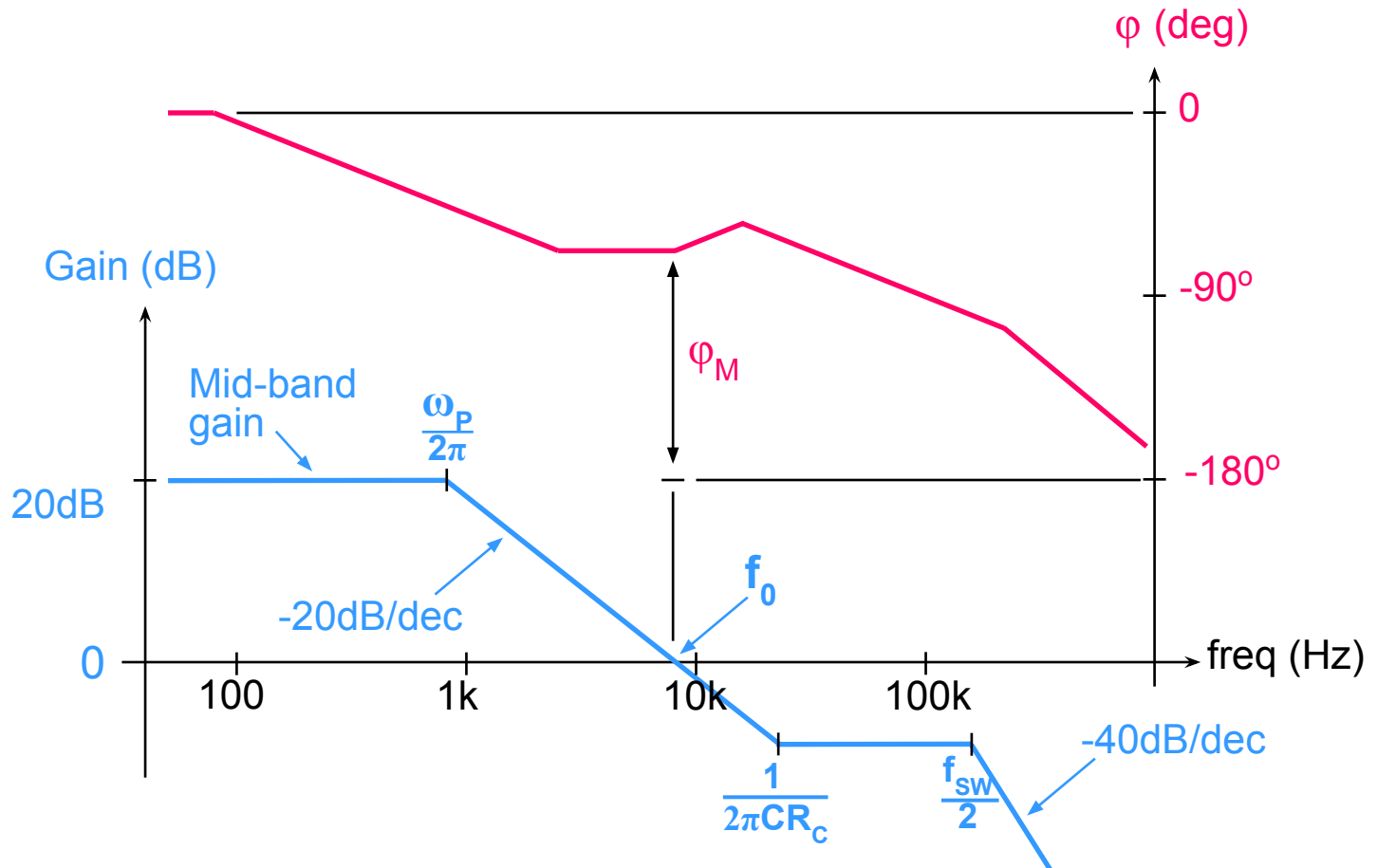
# Current-Mode Buck Regulator Frequency Response


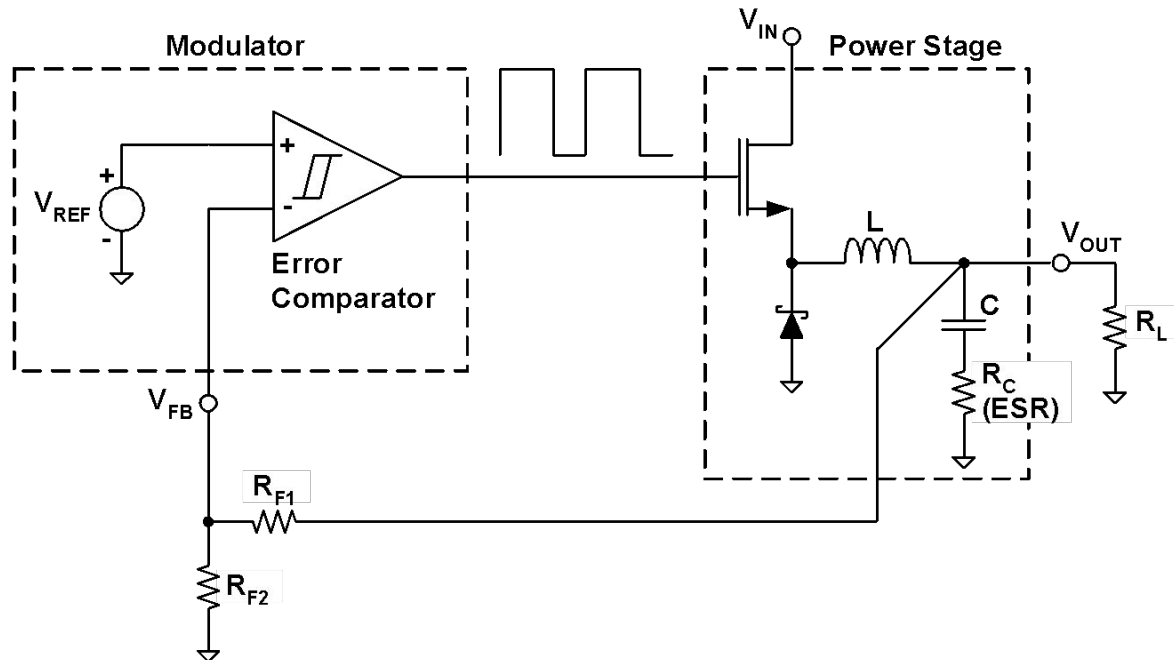
# Hysteretic Buck Regulator Basic Architecture


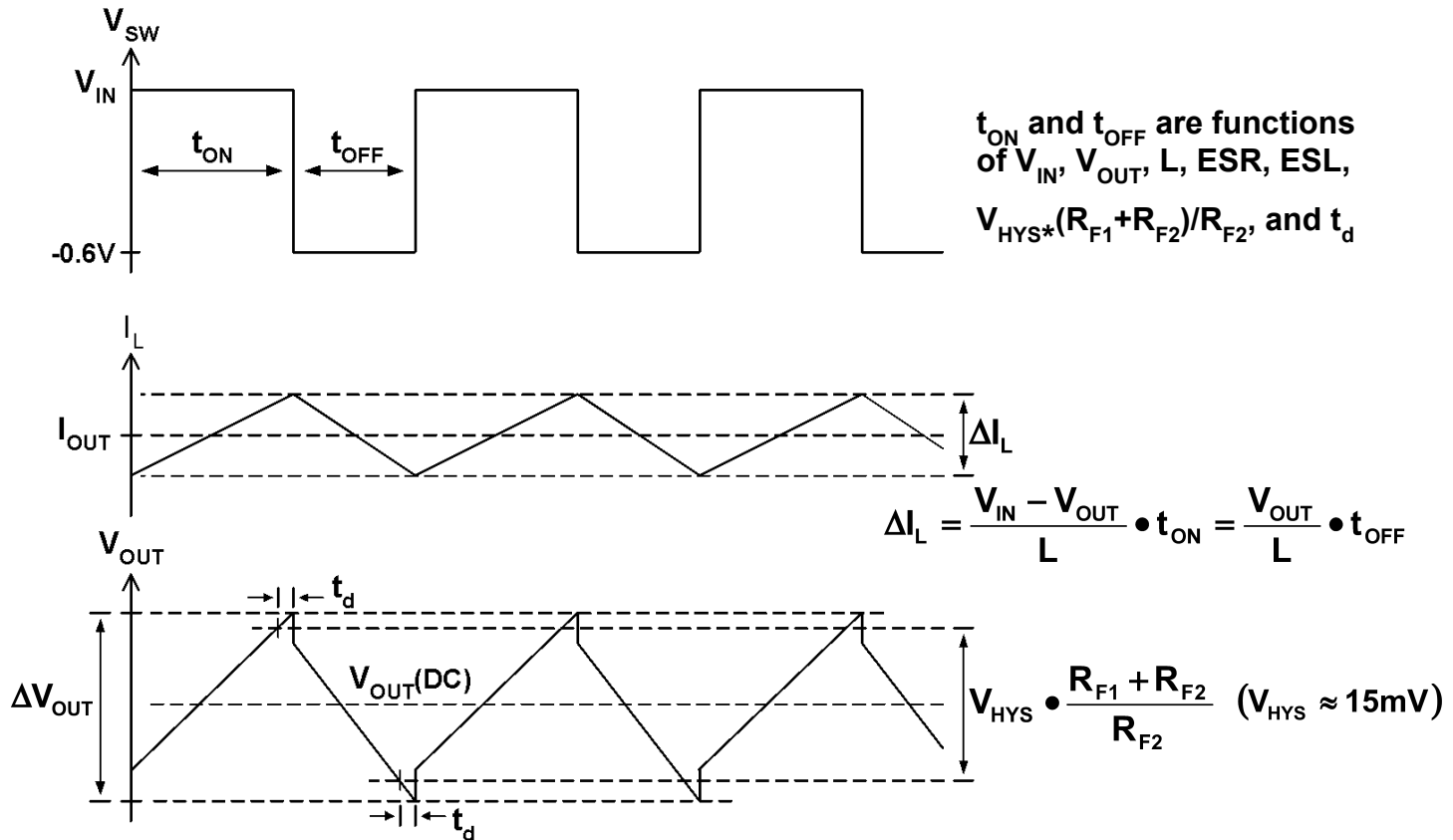
# Hysteretic Buck Regulator Switching Waveforms



# Calculating Hysteretic Regulator Switching Frequency

- In most cases, switching frequency is determined by output ripple voltage ( $\Delta V_{OUT}$ ) resulting from ESR. Amplitude of  $\Delta V_{OUT}$  is described by the following two equations:


$$\Delta V_{OUT} = \frac{V_{IN} - V_{OUT}}{L} \cdot DT \cdot ESR \quad DT = t_{ON} \quad D = \frac{V_{OUT}}{V_{IN}}$$

$$\Delta V_{OUT} = V_{HYS} \cdot \frac{R_{F1} + R_{F2}}{R_{F2}} + \left[ ESR \cdot \left( \frac{V_{IN} - V_{OUT}}{L} + \frac{V_{OUT}}{L} \right) \cdot t_d \right]$$

- Combining these two equations yields an expression for the switching frequency


$$f_{SW} = \frac{V_{OUT}}{V_{IN}} \cdot \frac{(V_{IN} - V_{OUT}) \cdot ESR}{\left( V_{HYS} \cdot \frac{R_{F1} + R_{F2}}{R_{F2}} \cdot L \right) + (V_{IN} \cdot ESR \cdot t_d)}$$
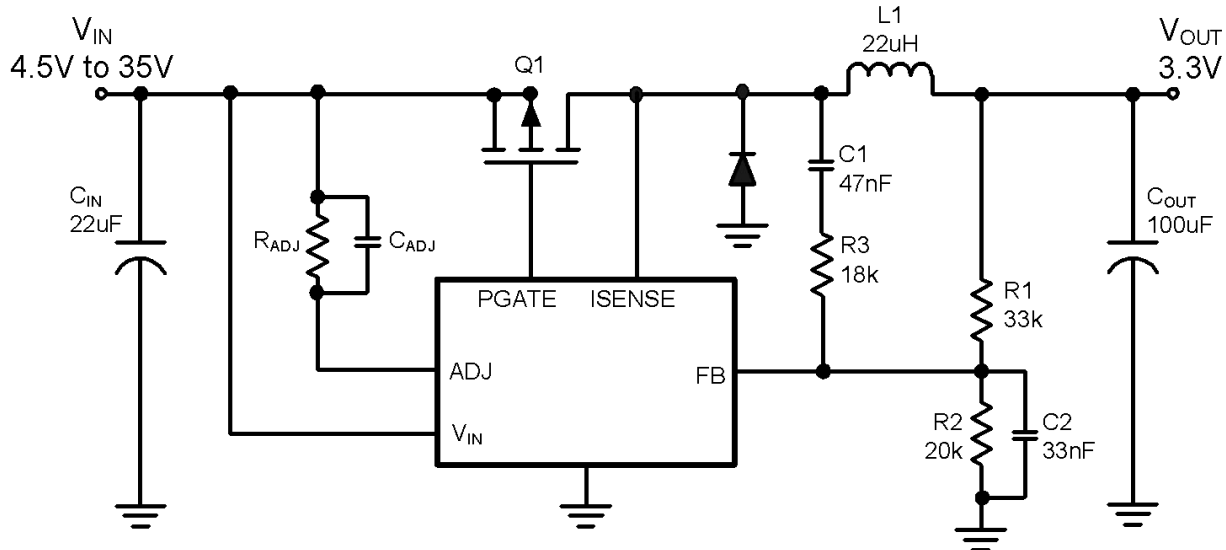
# Compensating for excessive ESL in output capacitor




$C_{OUT}$  has excessive ESL, so  $\Delta V_{OUT}$  has large voltage steps that result in erratic switching.  $C2$  filters-out ESL voltage step at FB pin.  $C1$ ,  $C3$  and  $R3$  generate triangle waveform that determines the switching frequency.
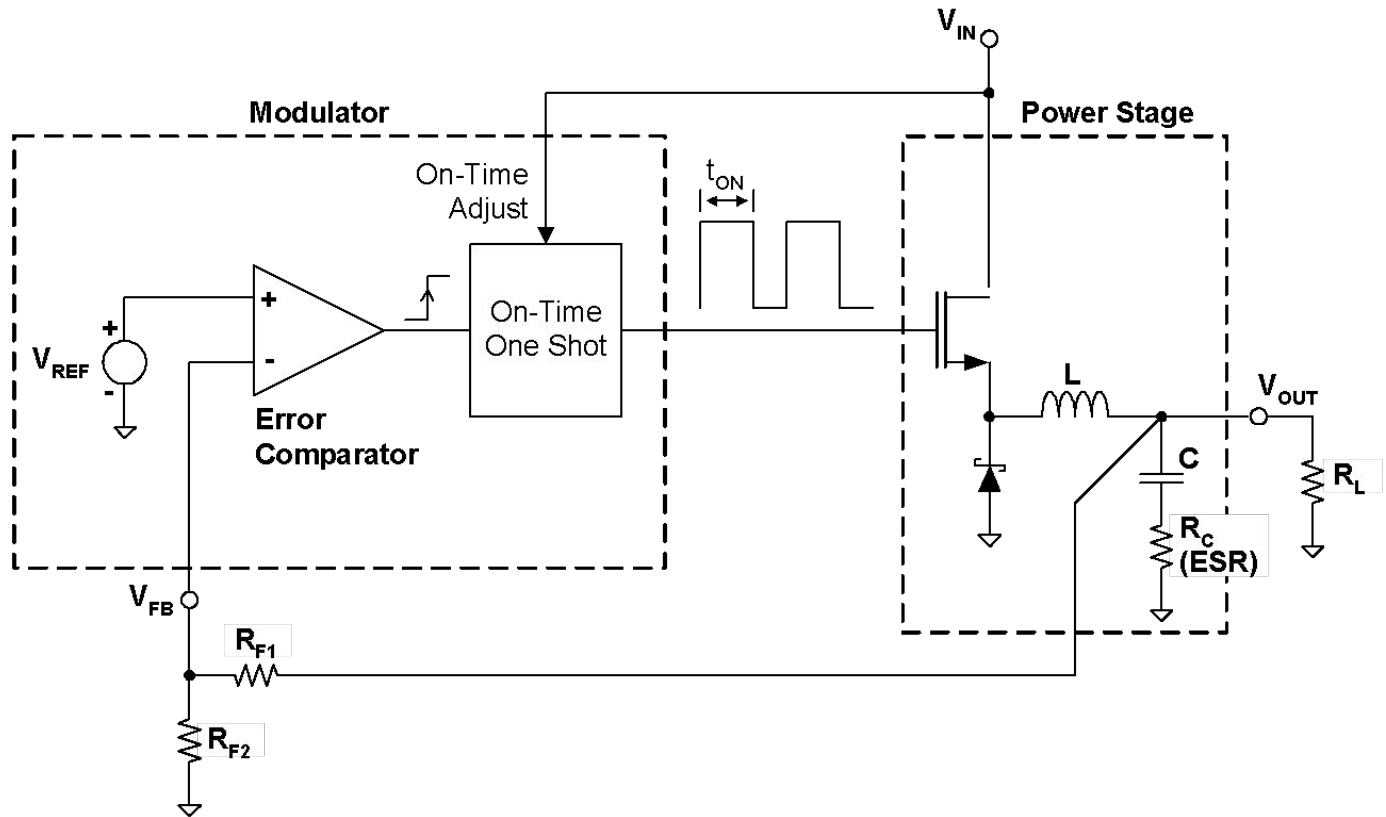
# Constant On-Time Buck Regulator Basic Architecture


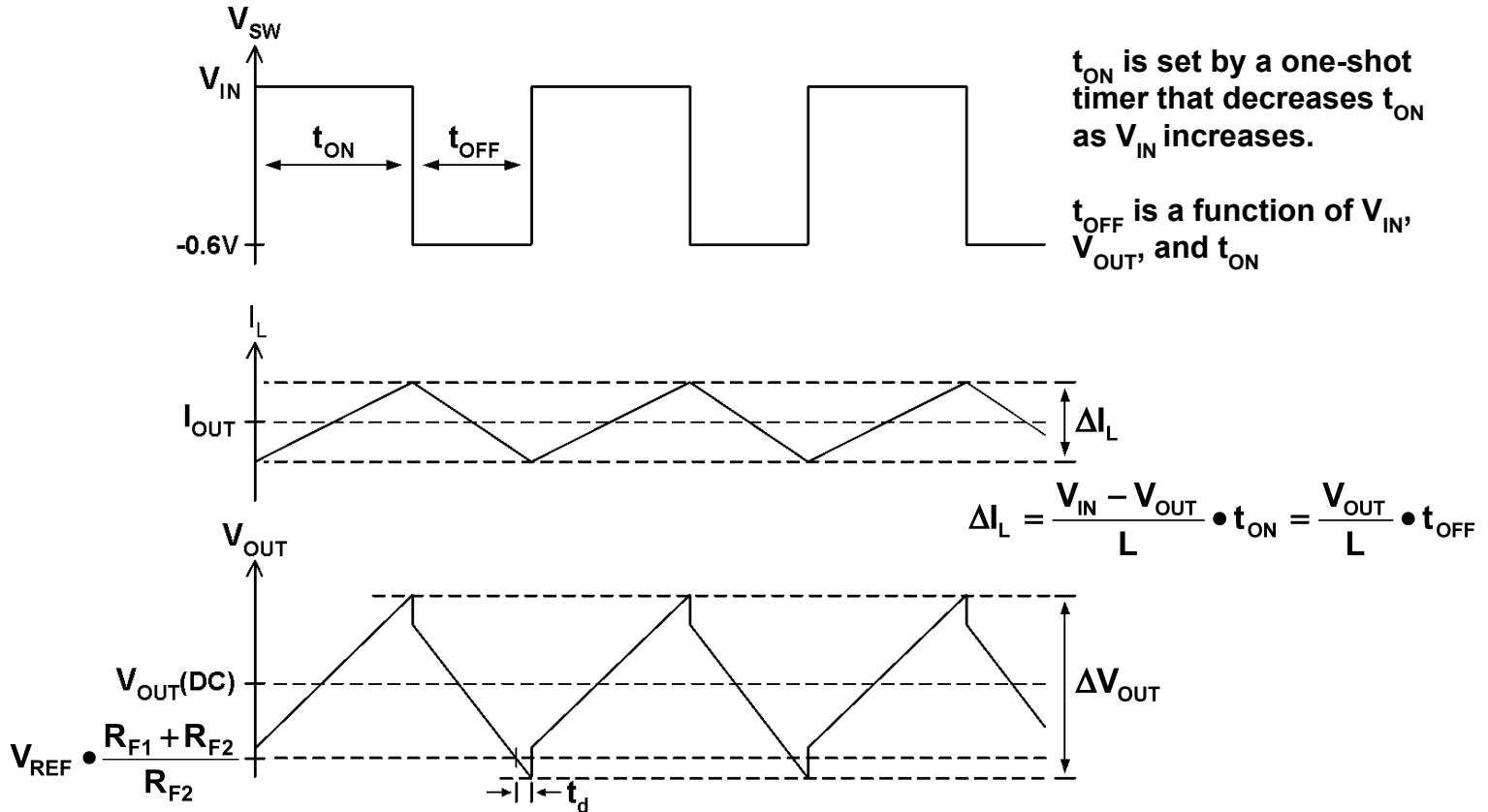
# Constant On-time Buck Regulator Switching Waveforms



# Calculating Constant On-Time Regulator Switching Frequency

---

- $t_{ON}$  is a constant, so the regulator must adjust  $t_{OFF}$  to the value necessary to maintain charge balance in the inductor. This is expressed by the following equation:

$$\frac{V_{IN} - V_{OUT}}{L} \bullet t_{ON} = \frac{V_{OUT}}{L} \bullet (T - t_{ON}) \quad t_{OFF} = (T - t_{ON})$$

- Solving this equation for  $1/T$  yields an expression for the switching frequency:

$$f_{SW} = \frac{V_{OUT}}{t_{ON} \bullet V_{IN}}$$