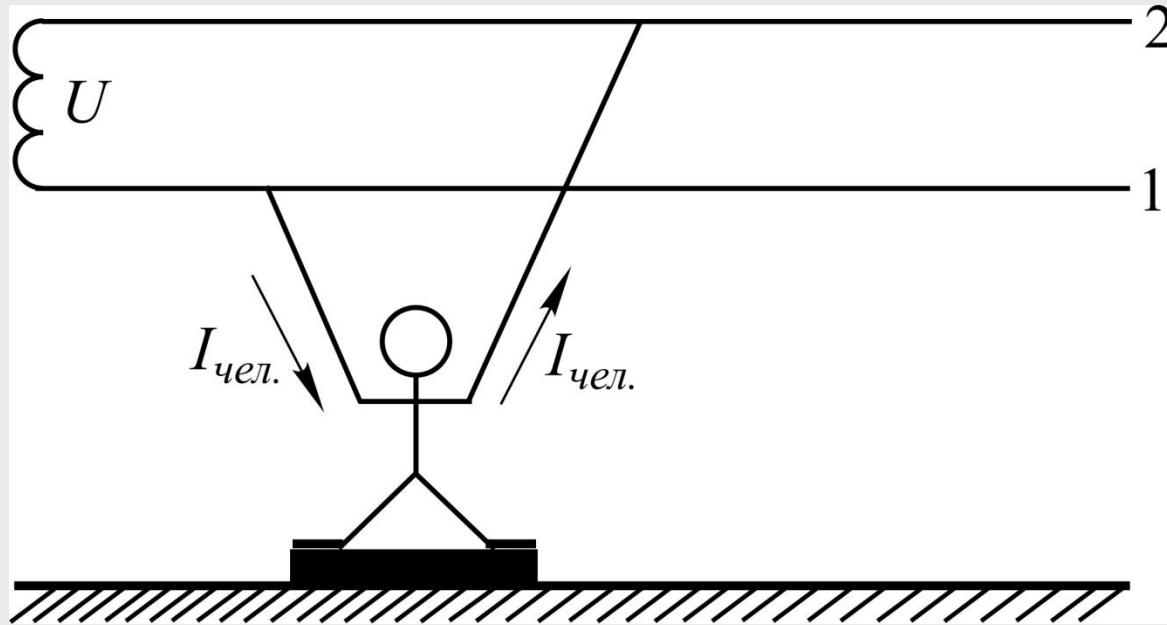


Анализ опасности поражения током в различных электрических сетях

Глазырин М.А.


Двухфазное прикосновение



$$I_{\div\grave{\text{a}}\ddot{\text{e}}.} = \frac{U_{\ddot{\text{e}}}}{R_{\div\grave{\text{a}}\ddot{\text{e}}.}} = \frac{U_{\hat{\text{o}}} \sqrt{3}}{R_{\div\grave{\text{a}}\ddot{\text{e}}.}}$$


$$I_{\div\grave{\text{a}}\ddot{\text{e}}.} = \frac{U}{R_{\div\grave{\text{a}}\ddot{\text{e}}.}}$$

Однофазное прикосновение

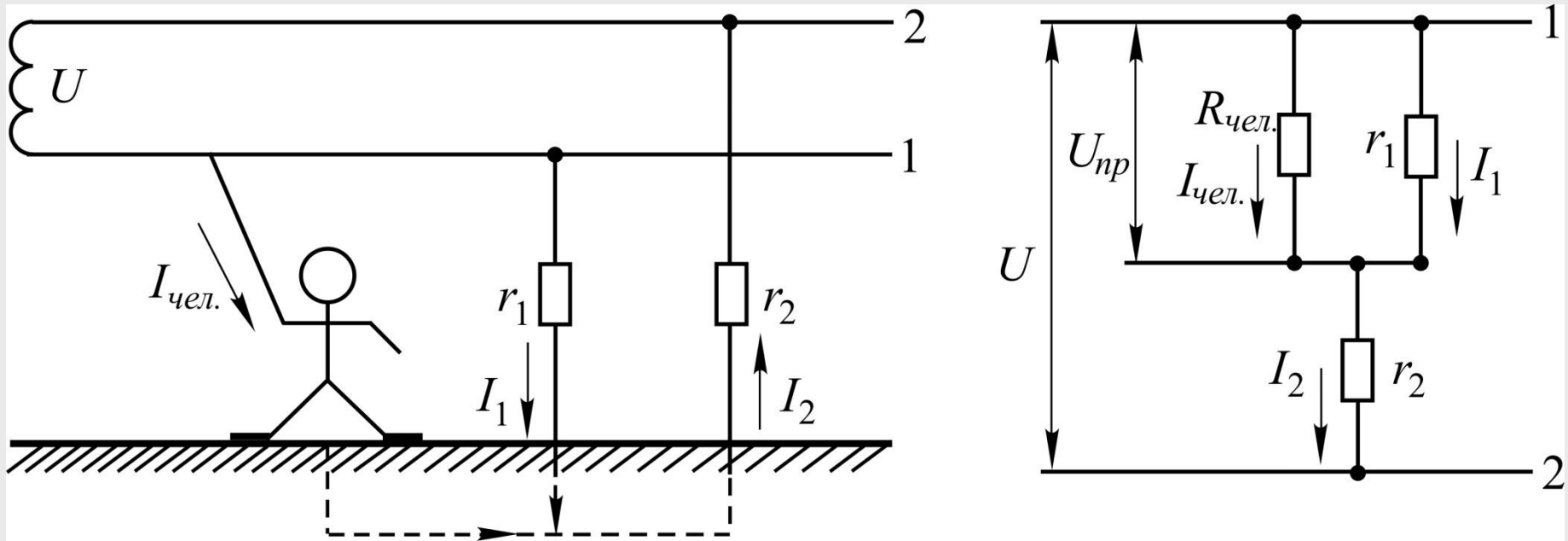

$$I_{\dot{\text{а}}\ddot{\text{е}}.} = \frac{U_{\ddot{\text{и}}\delta}}{R_{\dot{\text{а}}\ddot{\text{е}}.}} = \frac{U \cdot r_1}{r_1 \cdot r_2 + r_1 \cdot R_{\dot{\text{а}}\ddot{\text{е}}.} + r_2 \cdot R_{\dot{\text{а}}\ddot{\text{е}}.}}$$


Однофазное прикосновение

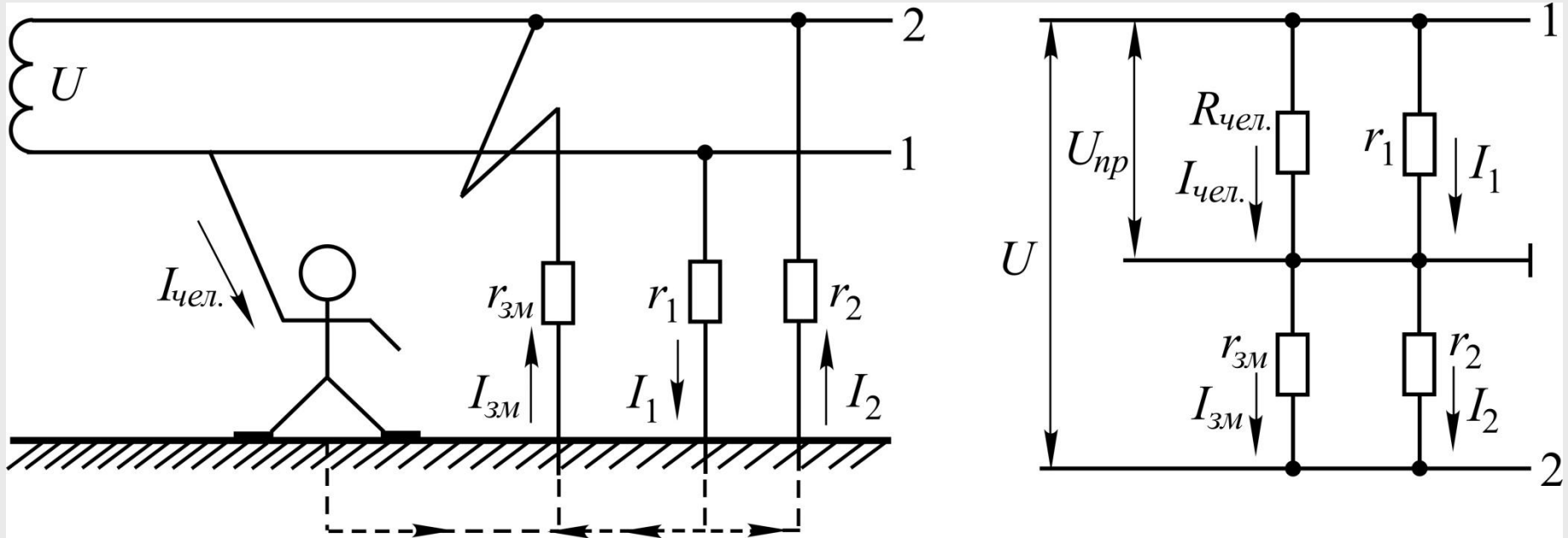

$$I_{\div\grave{\text{a}}\ddot{\text{e}}.} = \frac{U_{i\delta}}{R_{\div\grave{\text{a}}\ddot{\text{e}}.}} = \frac{U \cdot r_1}{r_1 \cdot r_2 \dot{Y} + r_1 \cdot R_{\div\grave{\text{a}}\ddot{\text{e}}.} + r_2 \dot{Y} \cdot R_{\div\grave{\text{a}}\ddot{\text{e}}.}}$$

$$I_{\div\grave{\text{a}}\ddot{\text{e}}.} \approx \frac{U}{R_{\div\grave{\text{a}}\ddot{\text{e}}.}}$$


Однофазное прикосновение

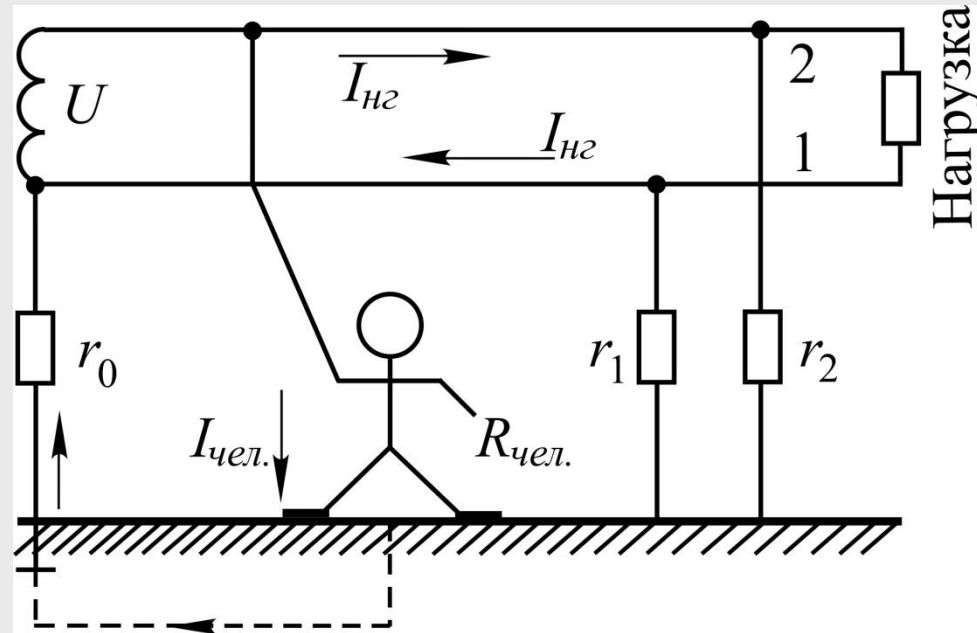

$$I_{\dot{a}\ddot{e}.} = \frac{U}{R_{\dot{a}\ddot{e}.} + r_0}$$


$$I_{\dot{a}\ddot{e}.} = \frac{U}{R_{\dot{a}\ddot{e}.} + r_{\dot{i}} + r_{\hat{i}\acute{a}} + r_0}$$

Однофазное прикосновение

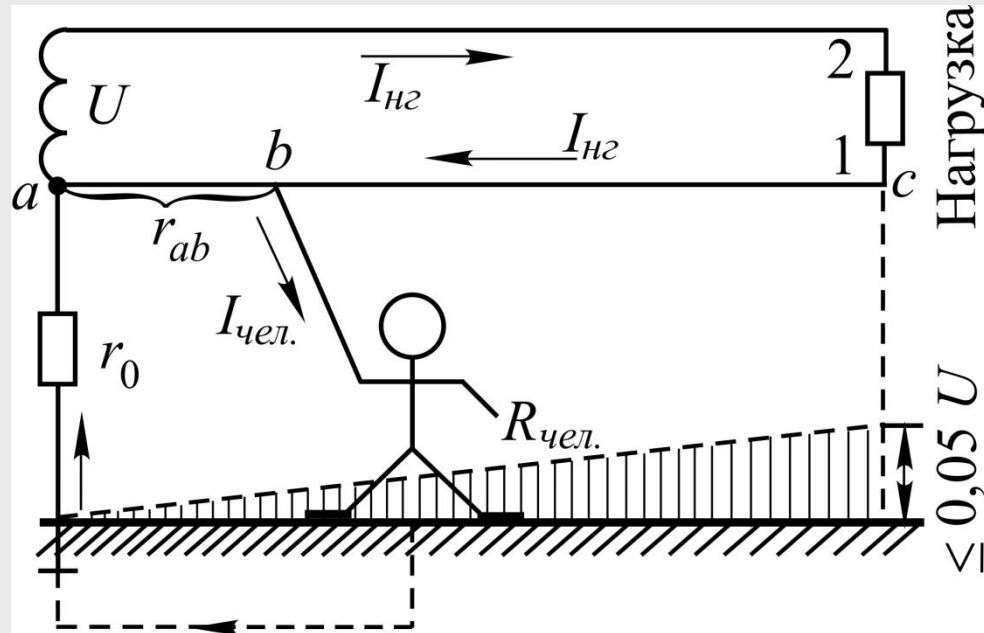


$$I_{\dot{a}\ddot{e}.} = \frac{U_{ab}}{R_{\dot{a}\ddot{e}.} + r_0} \quad I_{\dot{a}\ddot{e}.} = \frac{U_{ab}}{R_{\dot{a}\ddot{e}.} + r_i + r_{i\acute{a}} + r_0}$$

Однофазное прикосновение

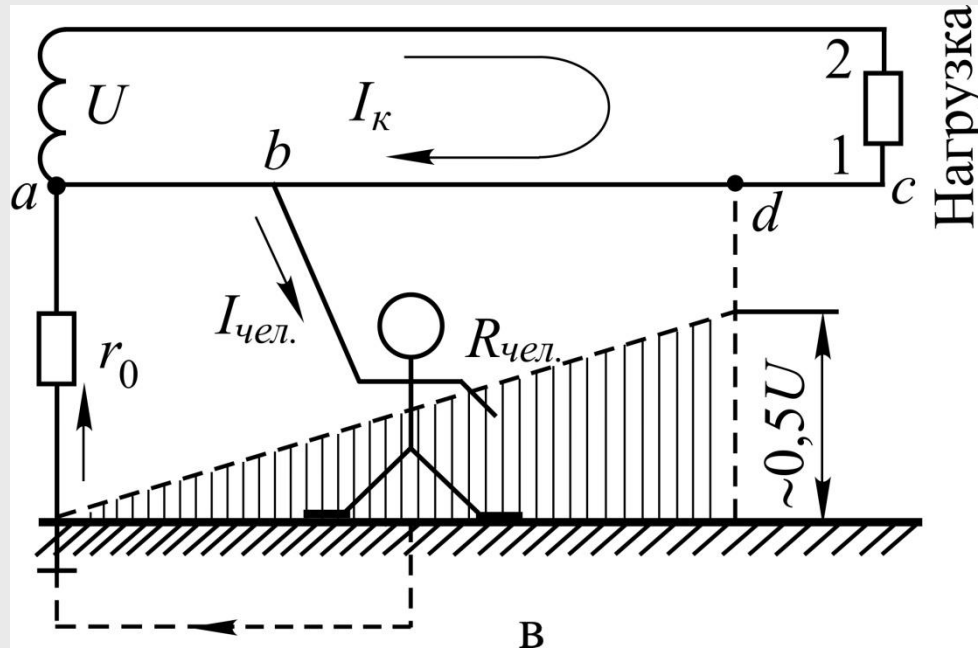

$$I_{\dot{a}\ddot{e}.} = \frac{U_{ab}}{R_{\dot{a}\ddot{e}.} + r_0} \quad I_{\dot{a}\ddot{e}.} = \frac{U_{ab}}{R_{\dot{a}\ddot{e}.} + r_i + r_{i\acute{a}} + r_0}$$

Однофазное прикосновение

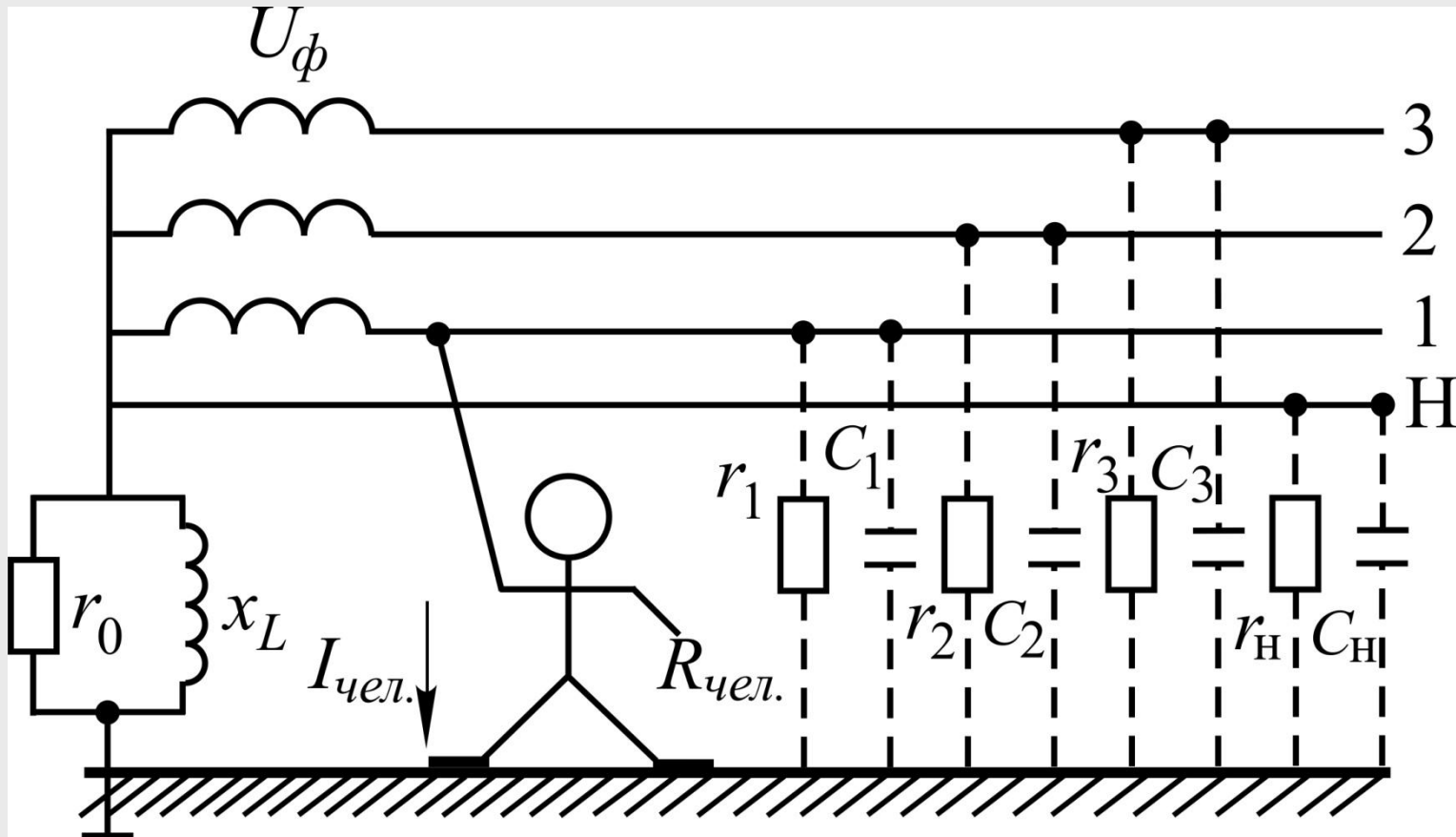

$$I_{\dot{a}\ddot{e}.} = \dot{U}_{\dot{i}\delta} \underline{Y}_{\dot{a}\ddot{e}.} = U_{\dot{o}} \underline{Y}_{\dot{a}\ddot{e}.} \frac{\underline{Y}_2 (1 - a^2) + \underline{Y}_3 (1 - a) + \underline{Y}_i + \underline{Y}_0}{\underline{Y}_1 + \underline{Y}_2 + \underline{Y}_3 + \underline{Y}_i + \underline{Y}_0 + \underline{Y}_{\dot{a}\ddot{e}.}}$$



Однофазное прикосновение

$$\underline{Y}_0 = \frac{1}{r_0}$$

$$\underline{Y}_1 = \underline{Y}_2 = \underline{Y}_3 = \underline{Y}_i \approx 0$$

$$I_{\dot{a}\ddot{e}.} = \frac{U_{\hat{o}}}{R_{\dot{a}\ddot{e}.} + r_0}$$

Однофазное прикосновение

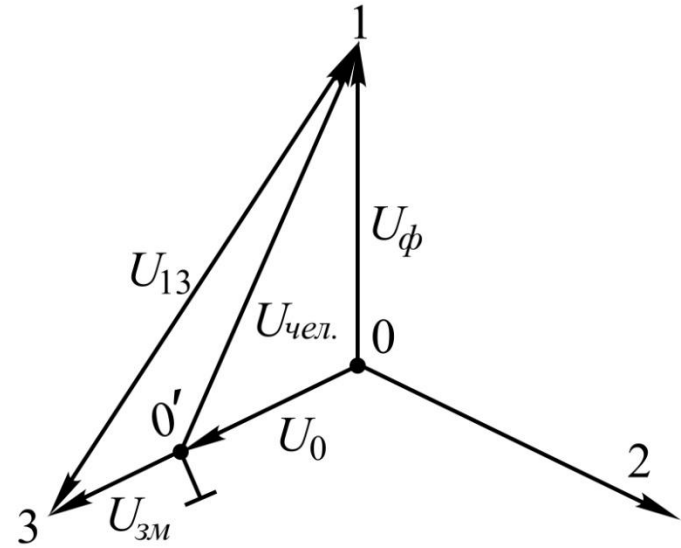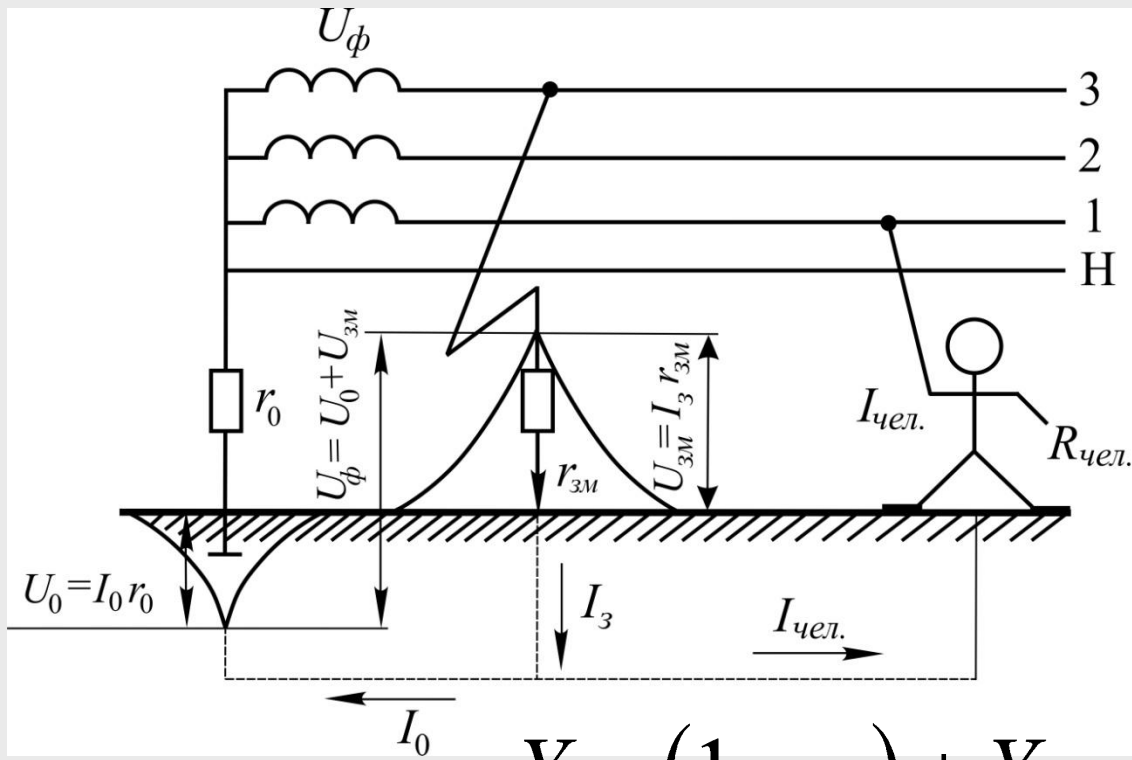


$$I_{\div\grave{\text{a}}\ddot{\text{e}}.} = U_{\hat{\text{o}}} \frac{Y_{\div\grave{\text{c}}\grave{\text{i}}} (1-a) + Y_0}{Y_{\div\grave{\text{c}}\grave{\text{i}}} + Y_0 + Y_{\div\grave{\text{a}}\ddot{\text{e}}.}}$$

$$I_{\div\grave{\text{a}}\ddot{\text{e}}.} = U_{\hat{\text{o}}} \frac{r_{\div\grave{\text{c}}\grave{\text{i}}} + r_0 \sqrt{3}}{r_{\div\grave{\text{c}}\grave{\text{i}}} r_0 + R_{\div\grave{\text{a}}\ddot{\text{e}}.} (r_{\div\grave{\text{c}}\grave{\text{i}}} + r_0)}$$

Однофазное прикосновение



$$I_{\div\ddot{a}\ddot{e}.} = \frac{U_{\hat{o}}}{R_{\div\ddot{a}\ddot{e}.} + \underline{Z} / 3}$$
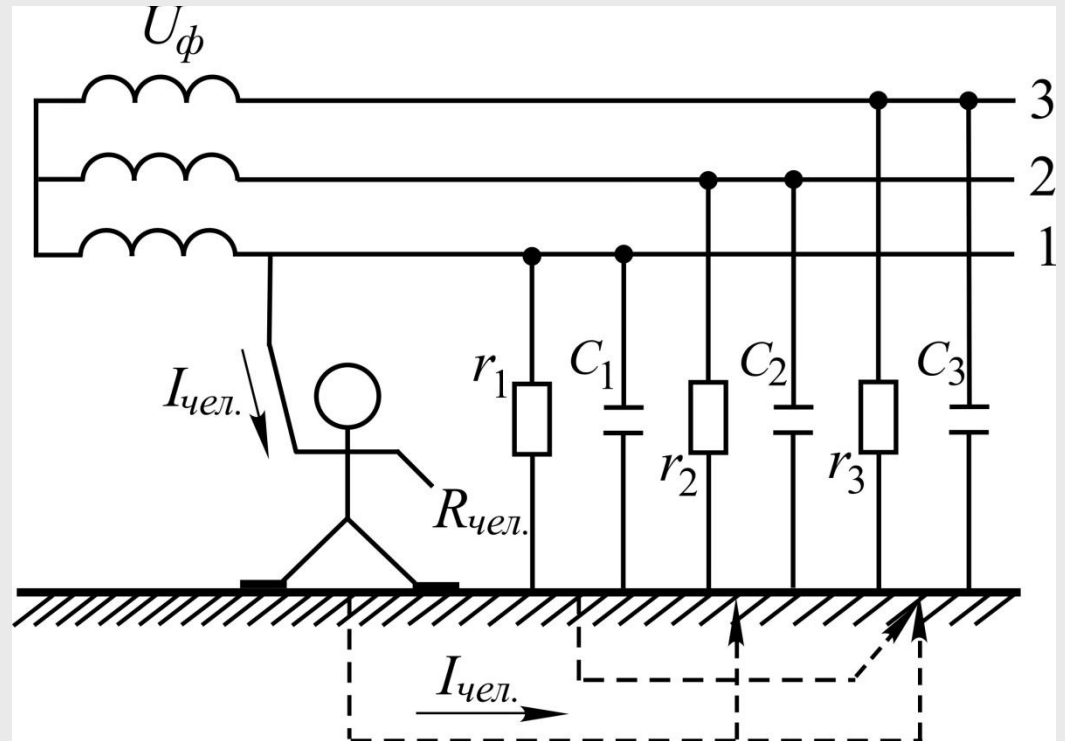
$$I_{\div\ddot{a}\ddot{e}.} = \frac{U_{\hat{o}}}{R_{\div\ddot{a}\ddot{e}.} + r / 3}$$



$$I_{\div\ddot{a}\ddot{e}.} = \frac{U_{\hat{o}}}{\sqrt{9R_{\div\ddot{a}\ddot{e}.}^2 \omega^2 C^2 + 1}} = \frac{U_{\hat{o}}}{\sqrt{R_{\div\ddot{a}\ddot{e}.}^2 + \left(\frac{\tilde{\sigma}_{\tilde{N}}}{3}\right)^2}}$$

Однофазное прикосновение

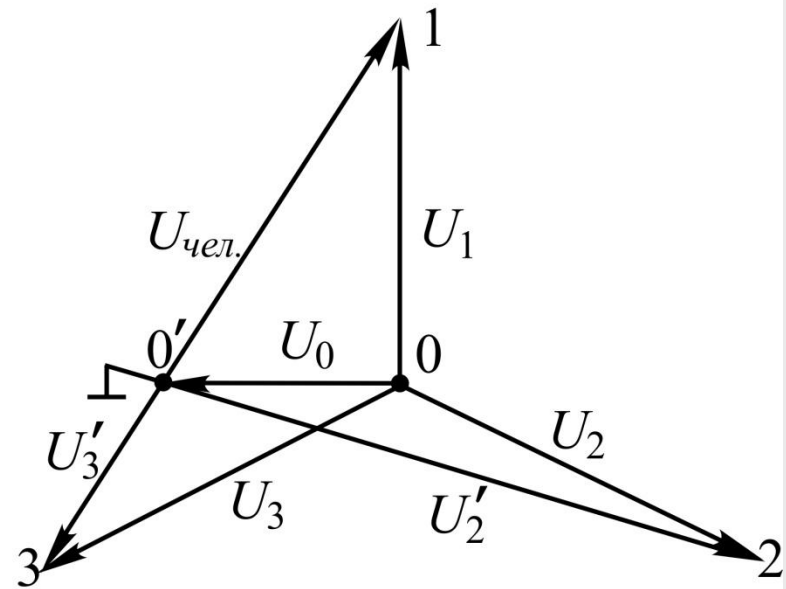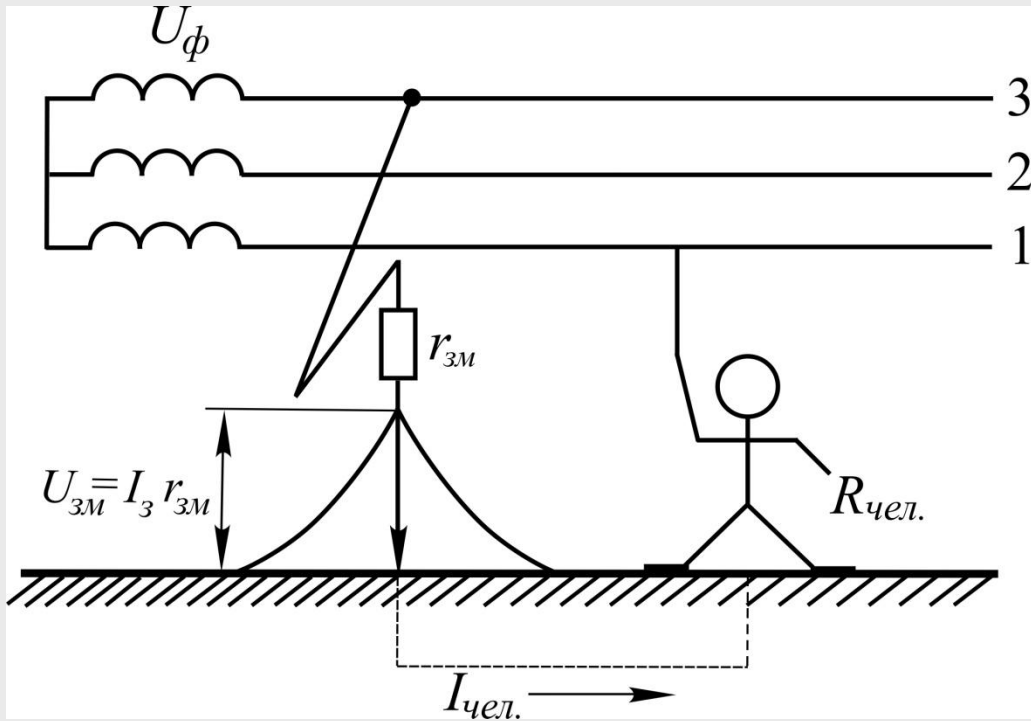

$$I_{\div \grave{a} \ddot{e}.} = U_{\hat{o}} \frac{Y_{\div \grave{a} \ddot{e}.} \underline{Y}_3 (1-a)}{\underline{Y}_3 + Y_{\div \grave{a} \ddot{e}.}}$$

$$I_{\div \grave{a} \ddot{e}.} = \frac{U_{\hat{o}} \sqrt{3}}{R_{\div \grave{a} \ddot{e}.} + r_{\grave{c}i}}$$

$$I_{\div \grave{a} \ddot{e}.} \approx \frac{U_{\hat{o}} \sqrt{3}}{R_{\div \grave{a} \ddot{e}.}}$$