

# Chapter 7

Virtex Arithmetic Structures

# Overview

- Addition and subtraction
- Multiplication
- DSP48
- DSP48E


# Basic Adder Equations

$$S_i = A_i \text{ XOR } B_i \text{ XOR } C_i$$

$$C_{i+1} = A_i B_i + (A_i \text{ XOR } B_i) C_i$$

Note: not unique expression for  $C_{i+1}$

# Basic Ripple Adder

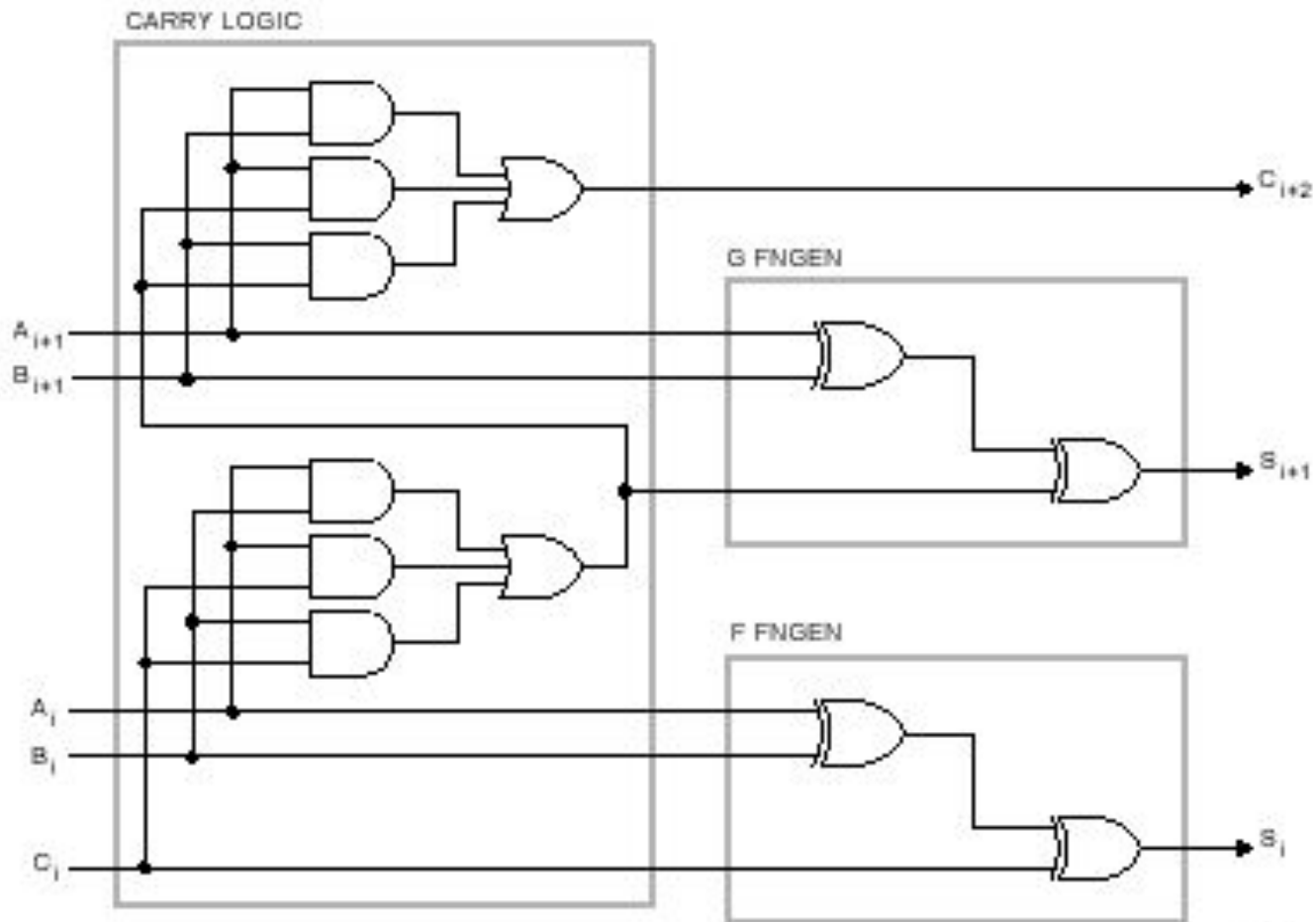

# Fast Carry Chains


A	B	C	C <sub>OUT</sub>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

A = B, C<sub>OUT</sub> = A


A ≠ B, C<sub>OUT</sub> = C<sub>IN</sub>

A = B, C<sub>OUT</sub> = A


XC002A

 

# Tracing Carry Chain

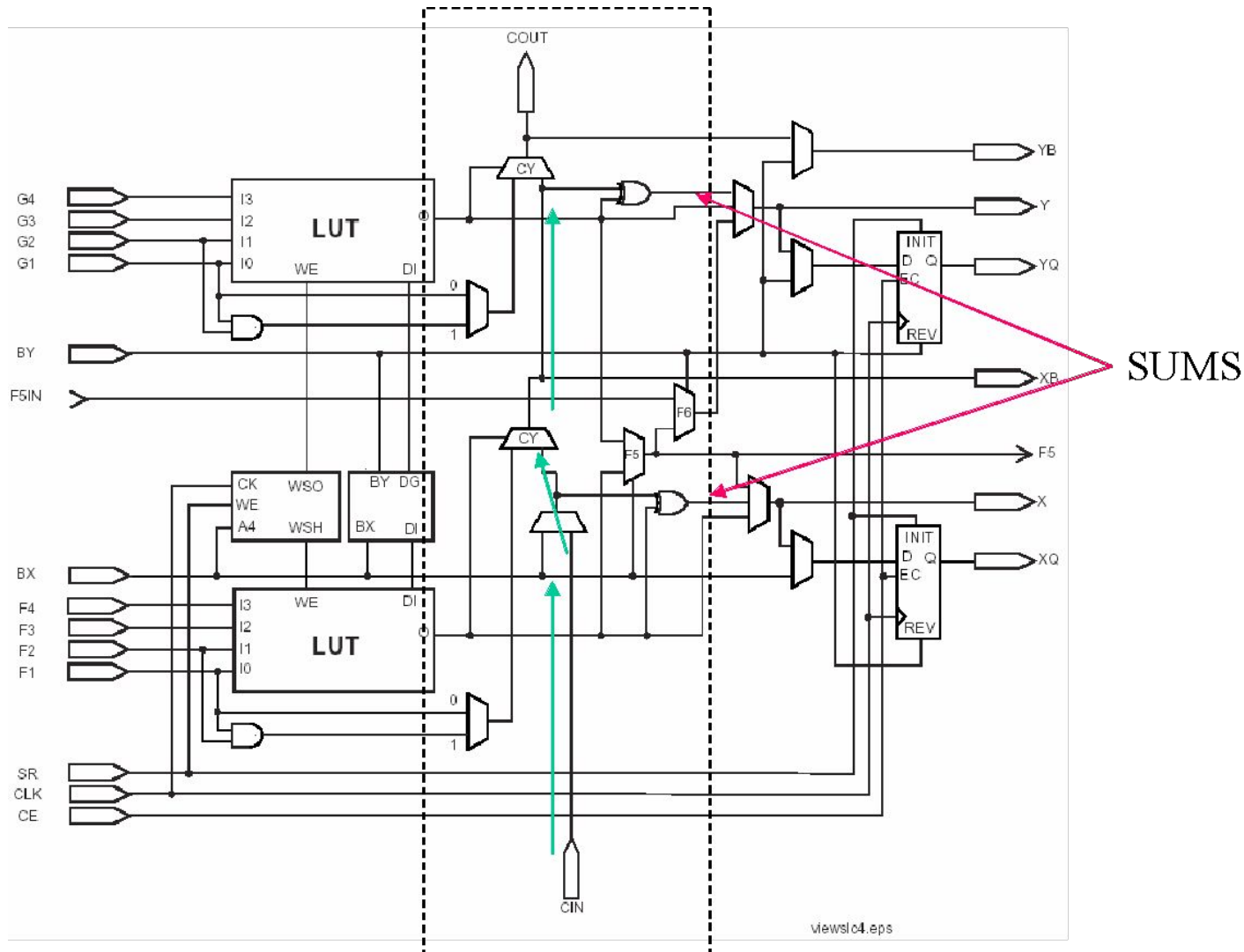

# Counters Built from Adders

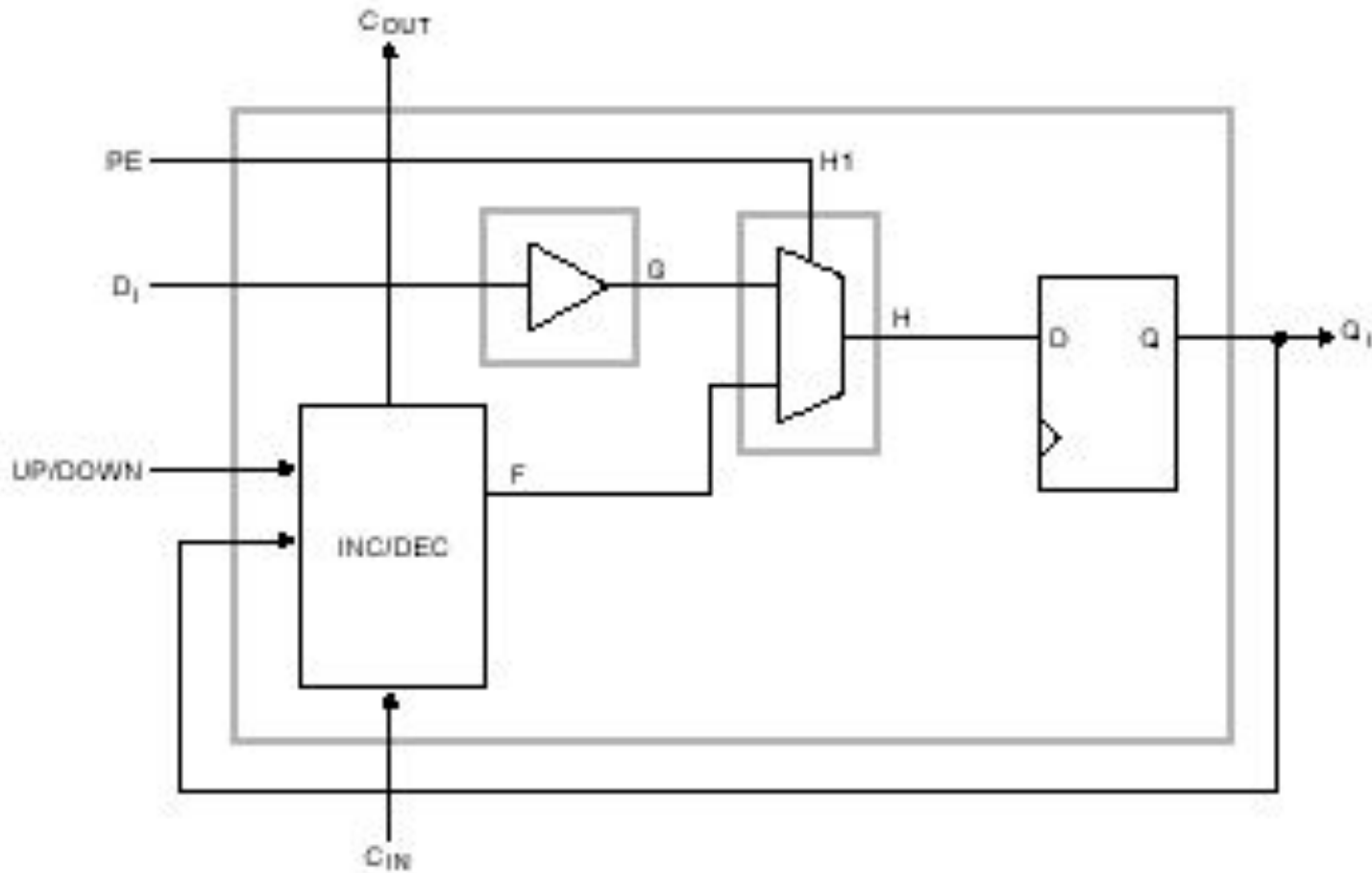

# Multiplication Review

$$\begin{array}{rcccccc} & & & & A_3 & A_2 & A_1 & A_0 \\ & & & & \times & B_1 & B_0 \\ \hline & & & & & A_3 B_0 & A_2 B_0 & A_1 B_0 & A_0 B_0 \\ A_3 B_1 & & & & & A_2 B_1 & A_1 B_1 & A_0 B_1 \\ \hline P_5 & P_4 & P_3 & P_2 & P_1 & P_0 \end{array}$$

Just like in the third grade . . .



# Fabric Based Multiplier

(comment: should be  $C_{OUT}$ )


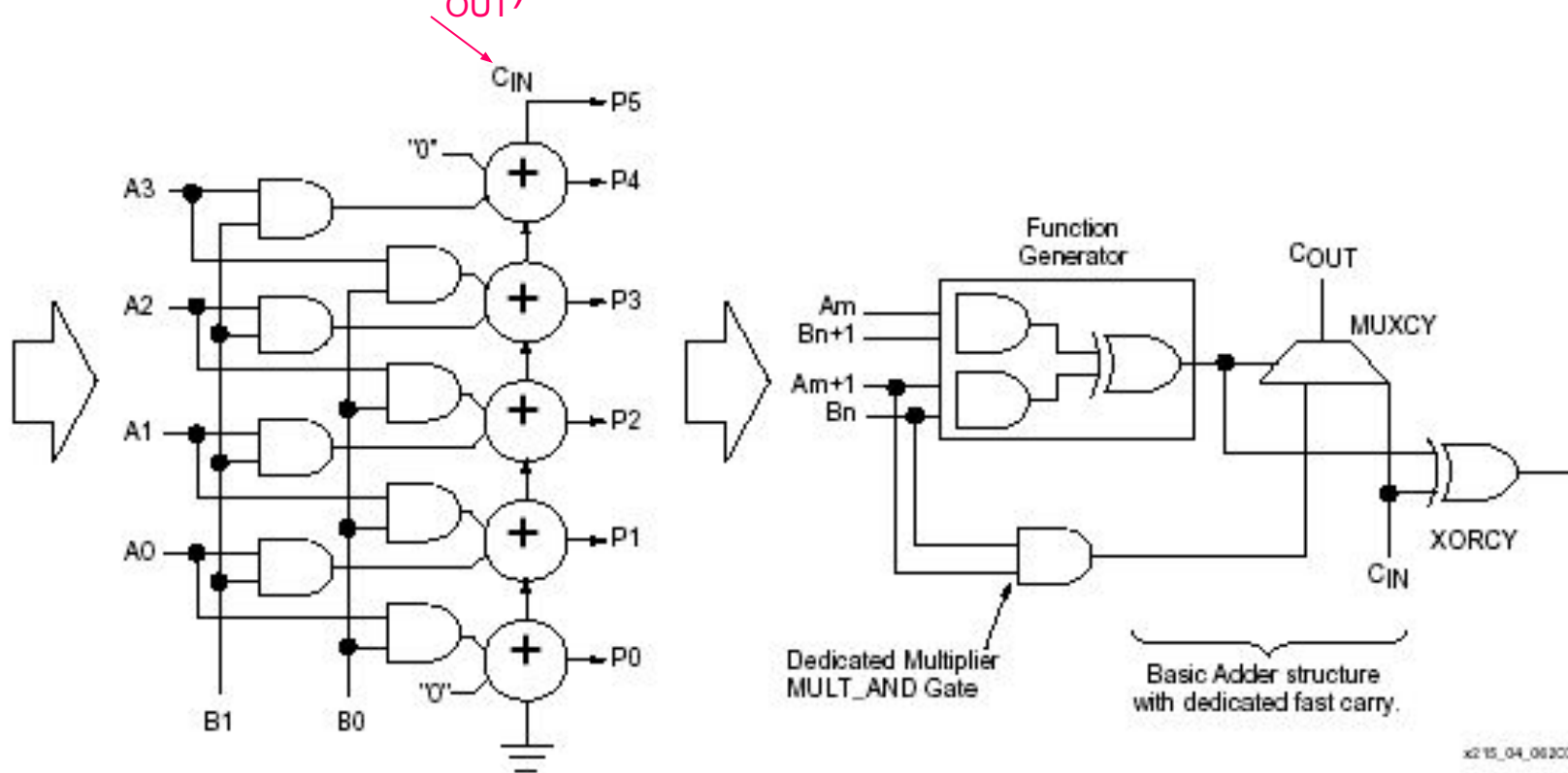


Figure 5: N x 2 Full Multiplier Implementation

# Mult/AND Identification

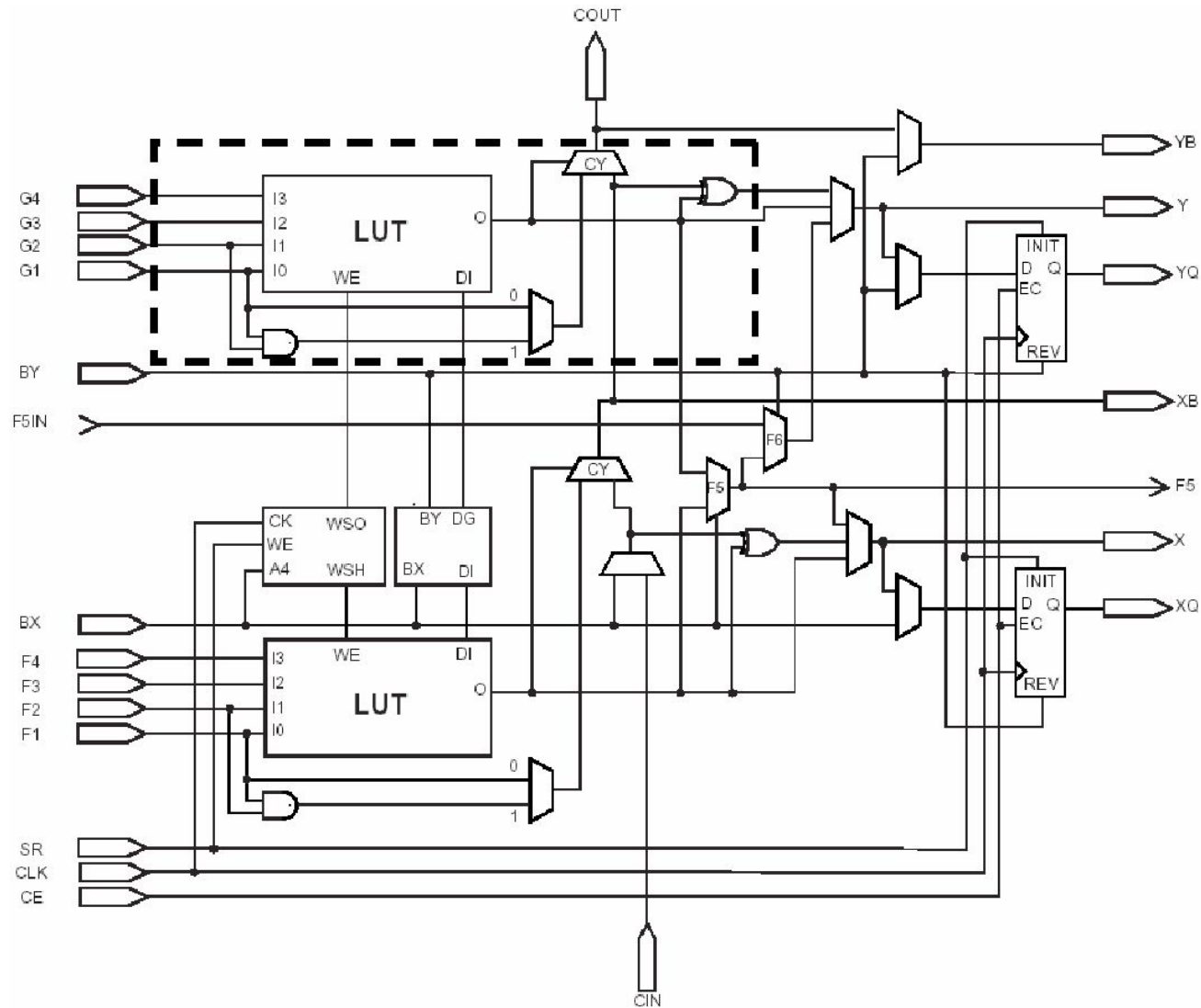


# Block Multipliers

- Xilinx Spartan 3/E and Virtex II = 18 bit
- Applications needing fewer bits can tie off higher order bits appropriately
- Applications needing more bits must either:
  - Cascade block multipliers
  - Combine blocks with fabric multipliers
- Other uses for block multipliers

# Virtex II/Spartan 3/E Block Multipliers

Primitive	A Width	B Width	P Width	Signed/Unsigned	Output
MULT18X18	18	18	36	Signed (Two's Complement)	Combinatorial
MULT18X18S	18	18	36	Signed (Two's Complement)	Registered

 

Combinational 2's Complement




Sequential 2's Complement

# Spartan 3 Multiplier Mix

Device	Multiplier Columns	Multipliers
XC3S50	1	4
XC3S200	2	12
XC3S400	2	16
XC3S1000	2	24
XC3S1500	2	32
XC3S2000	2	40
XC3S4000	4	96
XC3S5000	4	104

With this many multipliers, better be something we can do with them if we Don't need this many. Also, must be other sizes we can create – somehow. See **XAPP 467**

# 22 X 16 Bit Multiplier

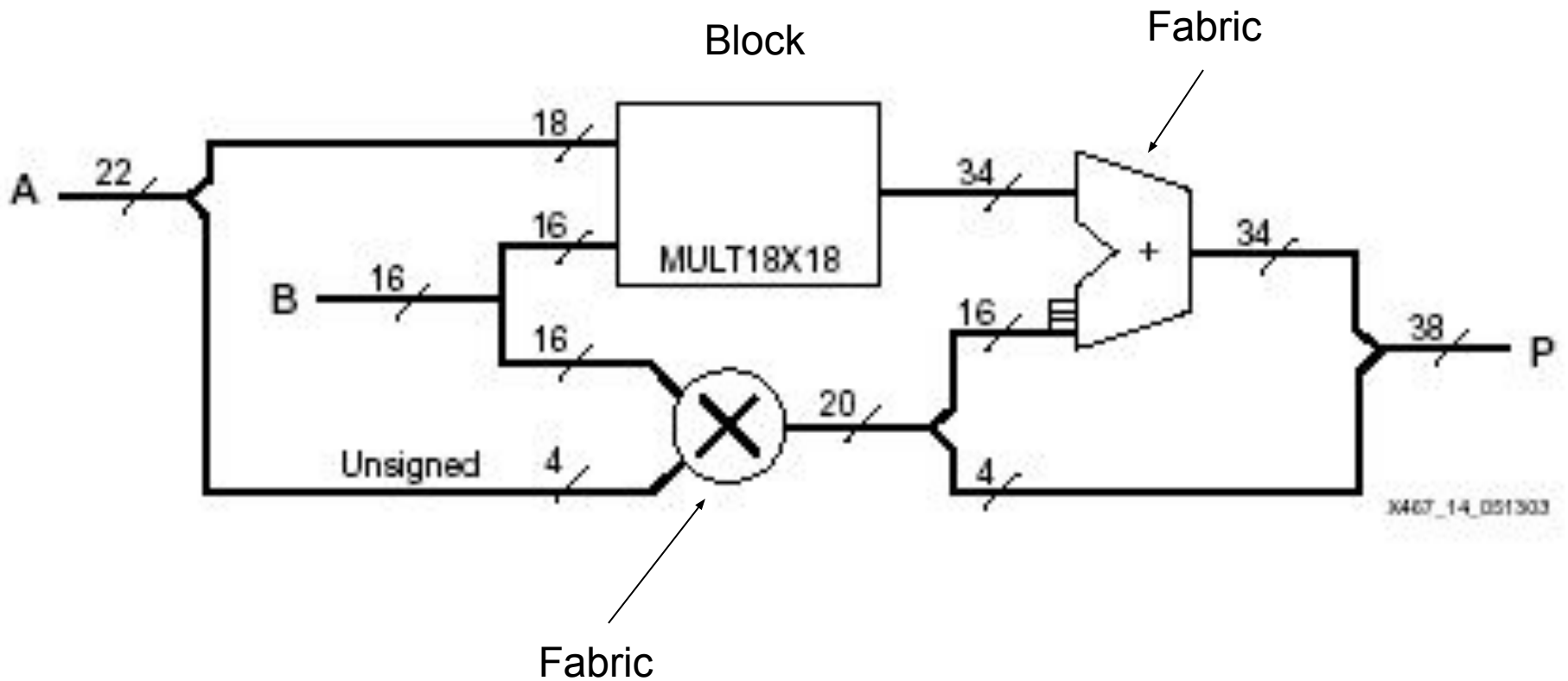

# Other Uses


- Multiply several small numbers with one block multiplier
- Division by repeated multiplication
- Barrel shift using multiplier
- Take two's complement of a number
- Get the magnitude of a two's complement number
- There are others

# DSP 48

- Introduced for Virtex 4
- Designed to efficiently cascade
- Xilinx teamed with outside arithmetic specialists to get best speed/area blocks
- Supports multiple rounding formats
- Not present in all V4 families




# Two Slice DSP 48

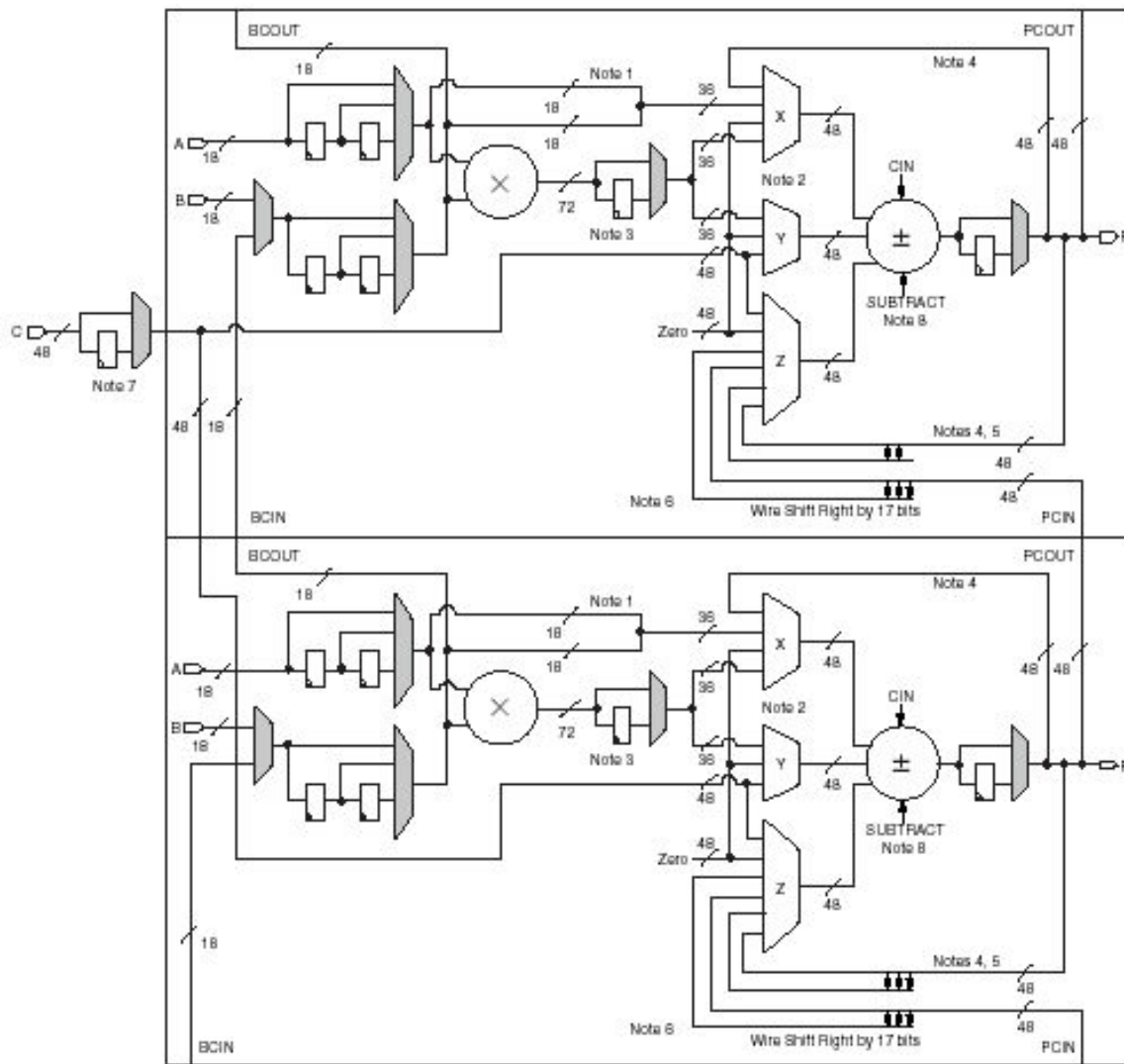

Top  
Slice


Bottom  
Slice

# Simplified DSP 48

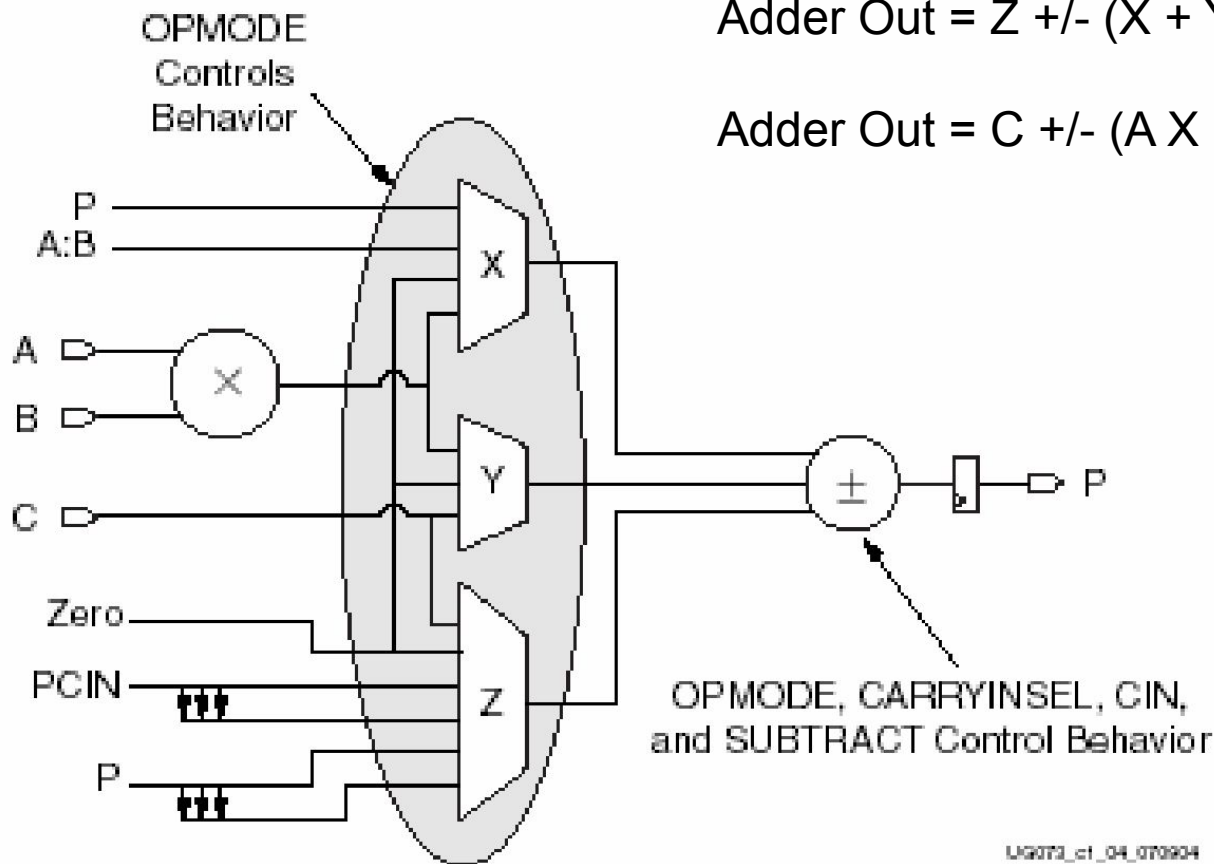


Hex OPMODE	Binary OPMODE	XYZ Multiplexer Outputs and Adder/Subtractor Output			
[6:0]	Z Y X	Z	Y	X	Adder/Subtractor Output
0x00	000 00 00	0	0	0	$\pm$ CIN
0x02	000 00 10	0	0	P	$\pm(P + \text{CIN})$
0x03	000 00 11	0	0	A:B	$\pm(A:B + \text{CIN})$
0x05	000 01 01	0	Note 1		$\pm(A \times B + \text{CIN})$
0x0c	000 11 00	0	C	0	$\pm(C + \text{CIN})$
0x0e	000 11 10	0	C	P	$\pm(C + P + \text{CIN})$
0x0f	000 11 11	0	C	A:B	$\pm(A:B + C + \text{CIN})$
0x10	001 00 00	PCIN	0	0	PCIN + CIN
0x12	001 00 10	PCIN	0	P	PCIN $\pm$ (P + CIN)
0x13	001 00 11	PCIN	0	A:B	PCIN $\pm$ (A:B + CIN)
0x15	001 01 01	PCIN	Note 1		PCIN $\pm$ (A $\times$ B + CIN)
0x1c	001 11 00	PCIN	C	0	PCIN $\pm$ (C + CIN)
0x1e	001 11 10	PCIN	C	P	PCIN $\pm$ (C + P + CIN)
0x1f	001 11 11	PCIN	C	A:B	PCIN $\pm$ (A:B + C + CIN)
0x20	010 00 00	P	0	0	P $\pm$ CIN
0x22	010 00 10	P	0	P	P $\pm$ (P + CIN)
0x23	010 00 11	P	0	A:B	P $\pm$ (A:B + CIN)
0x25	010 01 01	P	Note 1		P $\pm$ (A $\times$ B + CIN)
0x2c	010 11 00	P	C	0	P $\pm$ (C + CIN)
0x2e	010 11 10	P	C	P	P $\pm$ (C + P + CIN)
0x2f	010 11 11	P	C	A:B	P $\pm$ (A:B + C + CIN)
0x30	011 00 00	C	0	0	C $\pm$ CIN
0x32	011 00 10	C	0	P	C $\pm$ (P + CIN)
0x33	011 00 11	C	0	A:B	C $\pm$ (A:B + CIN)
0x35	011 01 01	C	Note 1		C $\pm$ (A $\times$ B + CIN)
0x3c	011 11 00	C	C	0	C $\pm$ (C + CIN)
0x3e	011 11 10	C	C	P	C $\pm$ (C + P + CIN)
0x3f	011 11 11	C	C	A:B	C $\pm$ (A:B + C + CIN)
0x50	101 00 00	Shift(PCIN)	0	0	Shift(PCIN) $\pm$ CIN
0x52	101 00 10	Shift(PCIN)	0	P	Shift(PCIN) $\pm$ (P + CIN)
0x53	101 00 11	Shift(PCIN)	0	A:B	Shift(PCIN) $\pm$ (A:B + CIN)
0x55	101 01 01	Shift(PCIN)	Note 1		Shift(PCIN) $\pm$ (A $\times$ B + CIN)
0x5c	101 11 00	Shift(PCIN)	C	0	Shift(PCIN) $\pm$ (C + CIN)
0x5e	101 11 10	Shift(PCIN)	C	P	Shift(PCIN) $\pm$ (C + P + CIN)
0x5f	101 11 11	Shift(PCIN)	C	A:B	Shift(PCIN) $\pm$ (A:B + C + CIN)
0x60	110 00 00	Shift(P)	0	0	Shift(P) $\pm$ CIN
0x62	110 00 10	Shift(P)	0	P	Shift(P) $\pm$ (P + CIN)
0x63	110 00 11	Shift(P)	0	A:B	Shift(P) $\pm$ (A:B + CIN)
0x65	110 01 01	Shift(P)	Note 1		Shift(P) $\pm$ (A $\times$ B + CIN)
0x6c	110 11 00	Shift(P)	C	0	Shift(P) $\pm$ (C + CIN)
0x6e	110 11 10	Shift(P)	C	P	Shift(P) $\pm$ (C + P + CIN)
0x6f	110 11 11	Shift(P)	C	A:B	Shift(P) $\pm$ (A:B + C + CIN)

# The DSP 48 Instruction Set

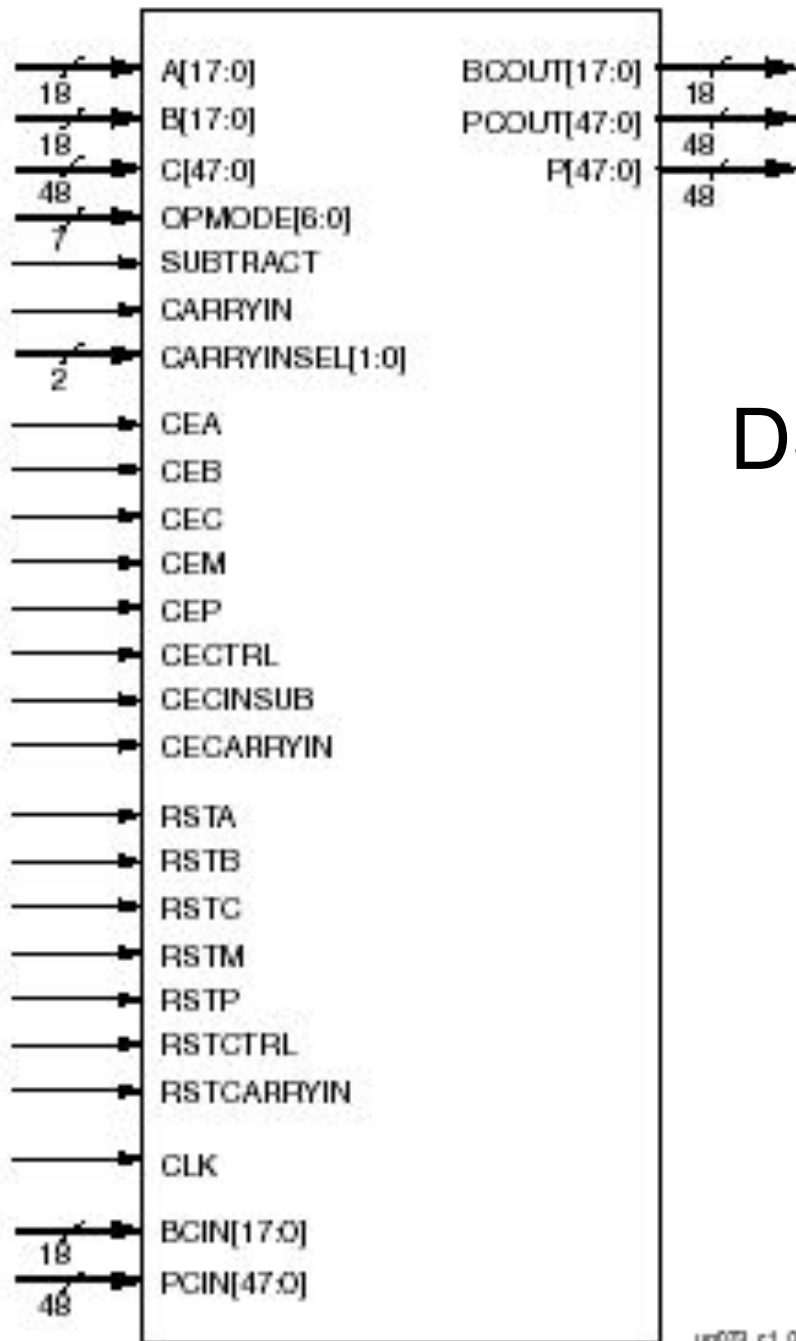


## DSP 48 Primitive Symbol

# DSP 48 Timing

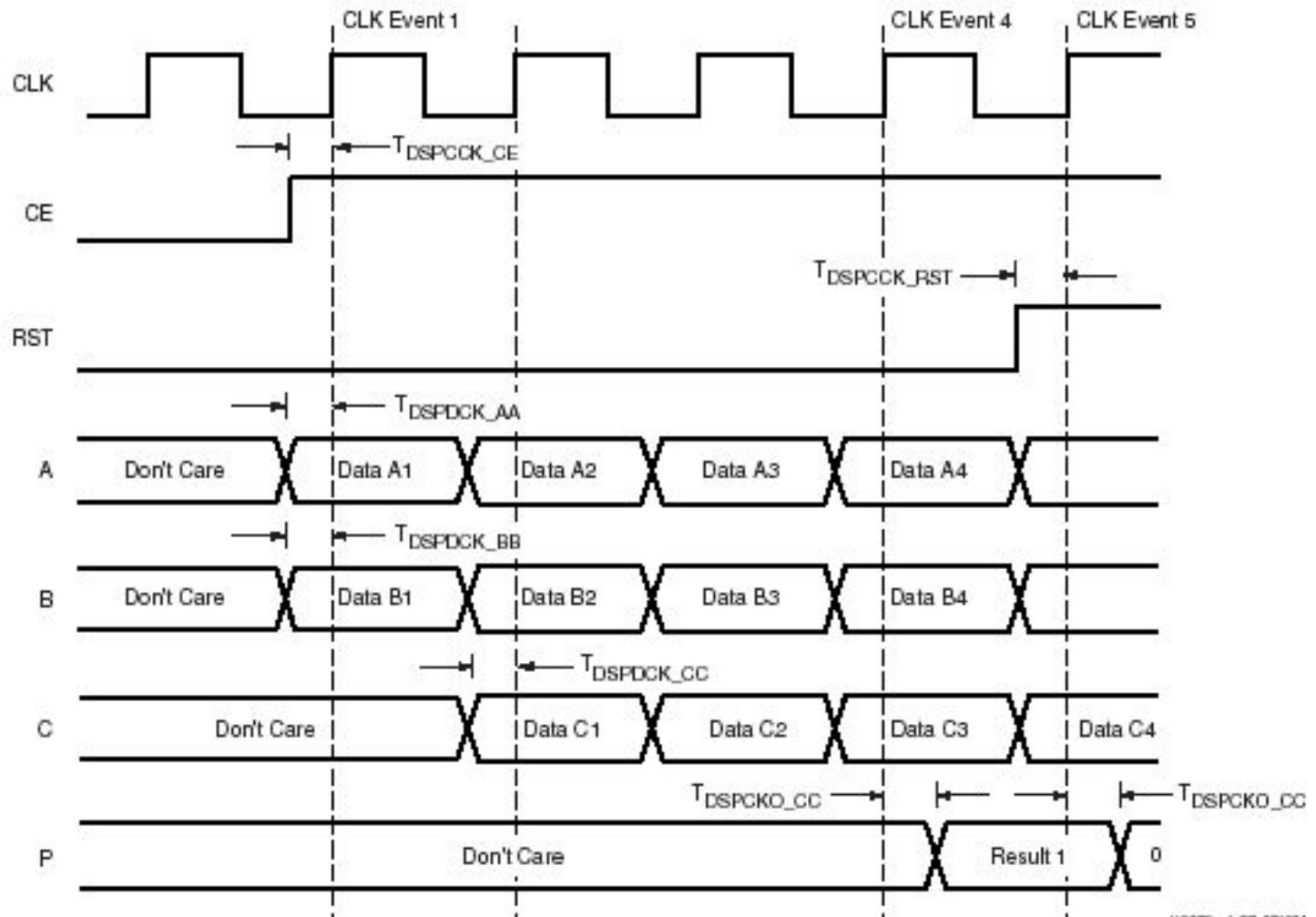

# Doing Other Things - SQRT

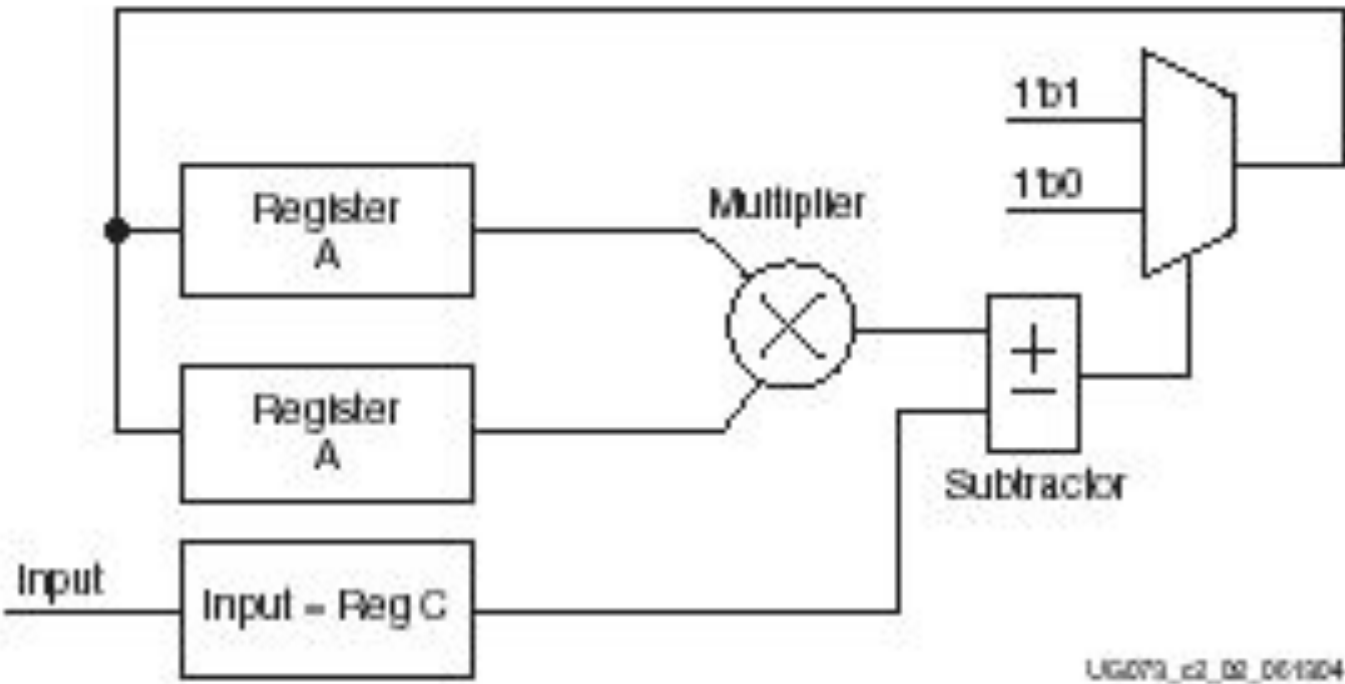


# Important to Do Other Things with DSP 48

- Divider
- Large multiplexer
- Barrel shifters
- Two's Complement converters
- Large counters
- Etc.

DSP 48 Handbook available on Xilinx website


# Virtex 5 DSP48E

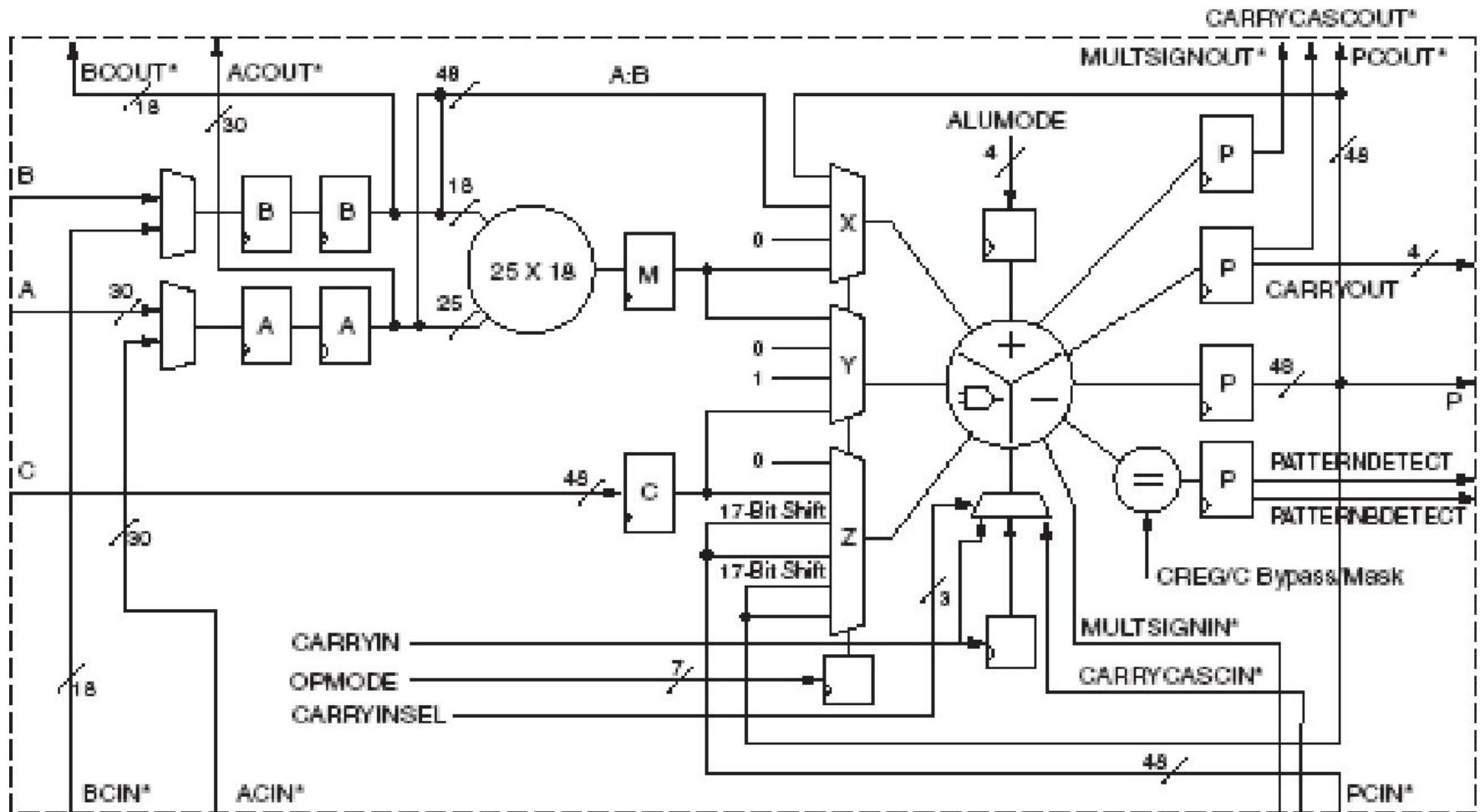

\*These signals are dedicated routing paths internal to the DSP48E column. They are not accessible via fabric routing resources.



# Simpler DSP48E

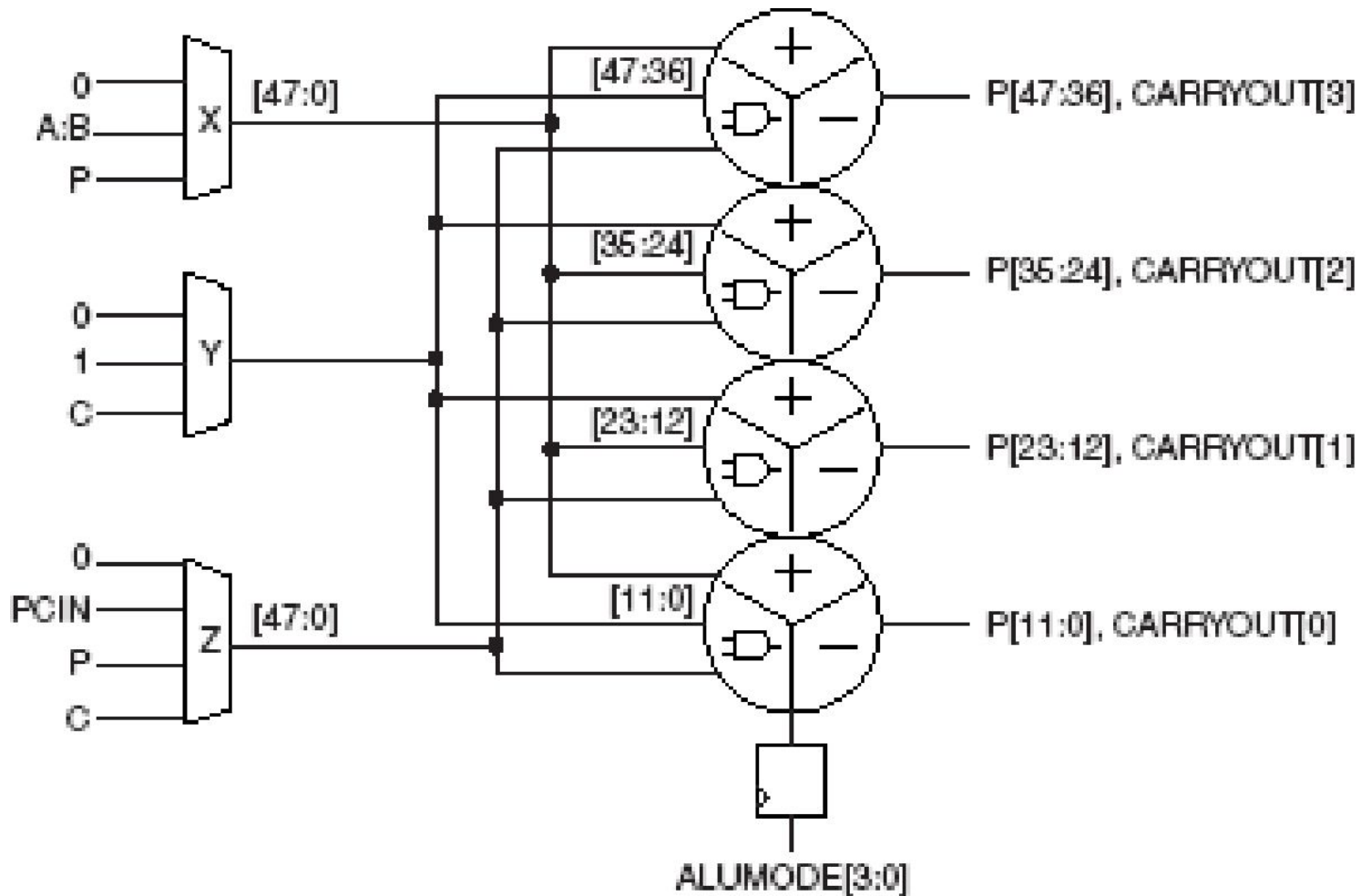

# Other Useful Functions

- Building up “word wise” logic
  - AND,OR
- Same list as for the DSP48

# Support

- Xilinx offers an elaborate (read:\$) set of tools that interface to the MatLab toolchain
- Focused on DSP algorithm development
- Permits “hardware in the loop” simulation
- Also working on higher level compile tools as DSP developers tend to be more mathematicians and less “hardware designers” (read: C, C++ oriented)