

$$Z_a = Z_b = Z_c$$

$$Z_a = z_a e^{j\varphi_a}$$

$$Z_b = z_b e^{j\varphi_b}$$

$$Z_c = z_c e^{j\varphi_c}$$

$$I_\lambda = I_\phi$$

$$I_A = I_B = I_C = I_\lambda$$

$$I_a = I_b = I_c = I_\phi$$

$$U_{\text{л}} = \sqrt{3}U_{\phi}; \quad U_{\phi} = \frac{U_{\text{л}}}{\sqrt{3}}$$


$$\dot{U}_a = U_{\phi} e^{j0^{\circ}} = U_{\phi}$$

$$\dot{U}_b = U_{\phi} e^{-j120^{\circ}}$$

$$\dot{U}_c = U_{\phi} e^{j120^{\circ}}$$

$U_{\text{л}}$	U_{ϕ}
660	380
380	220
220	127

problem 1

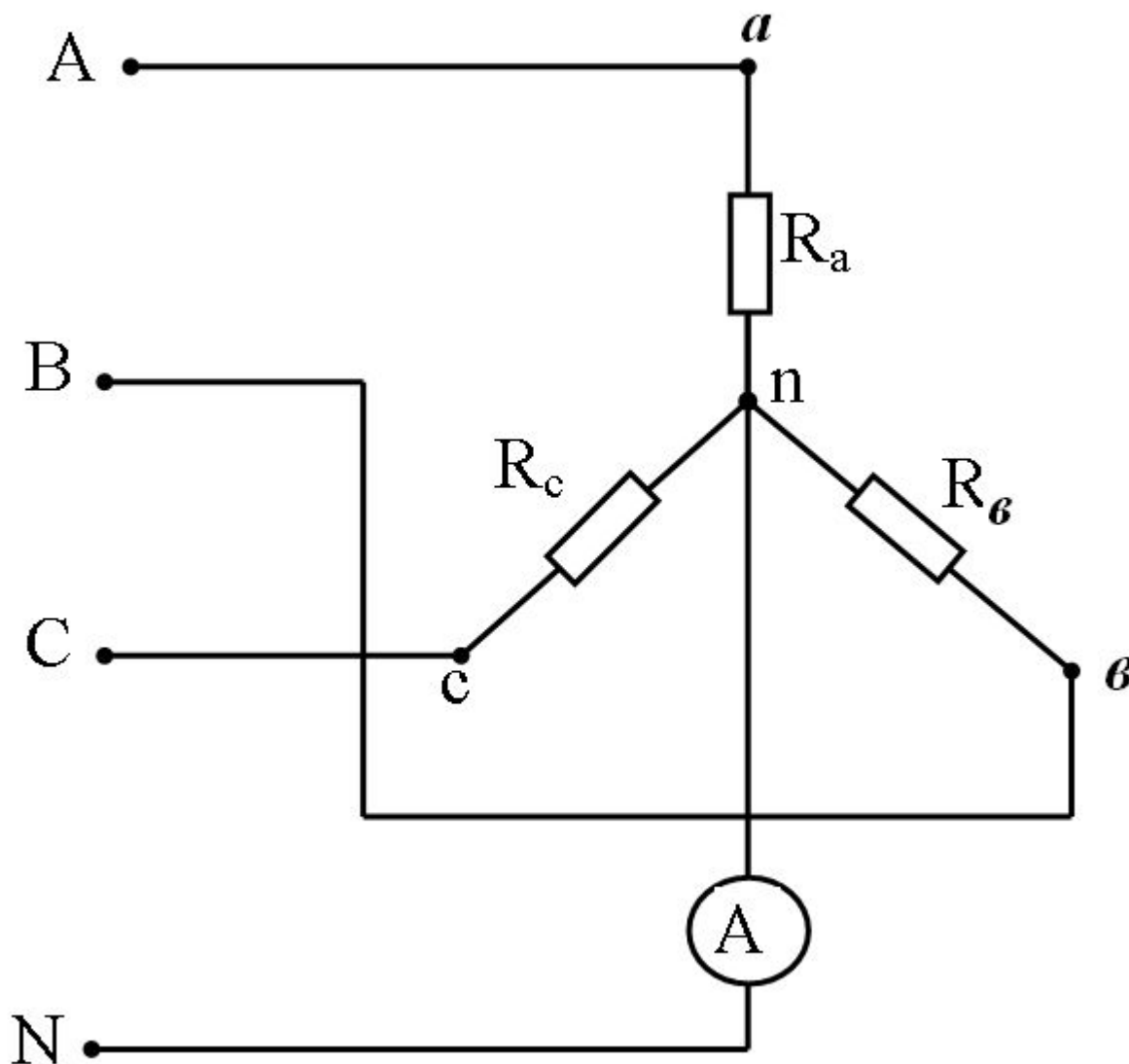

Given

$$\dot{R}_a = R_b = R_c = R = 20 \text{ Ohm}$$

$$V_L = 380 \text{ V}$$

Find:

$$I_a, I_b, I_c, I_N - ?$$



$$U_{\phi} = \frac{U_{\pi}}{\sqrt{3}} = 220 \text{ V}$$

$$\dot{I}_a = \frac{U_a}{Z_a} = \frac{U_{\phi} e^{j0^{\circ}}}{R_a} = \frac{U_{\phi}}{R} = I_{\phi} = 11 \text{ A}$$

$$\dot{I}_b = \frac{U_{\phi} e^{-j120^{\circ}}}{R} = I_{\phi} e^{-j120^{\circ}} = 11 e^{-j120^{\circ}} \text{ A}$$

$$\dot{I}_c = \frac{U_{\phi} e^{j120^{\circ}}}{R} = I_{\phi} e^{j120^{\circ}} = 11 e^{j120^{\circ}} \text{ A}$$

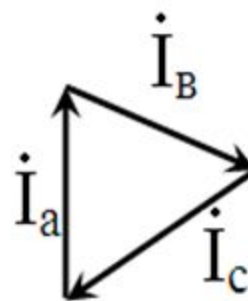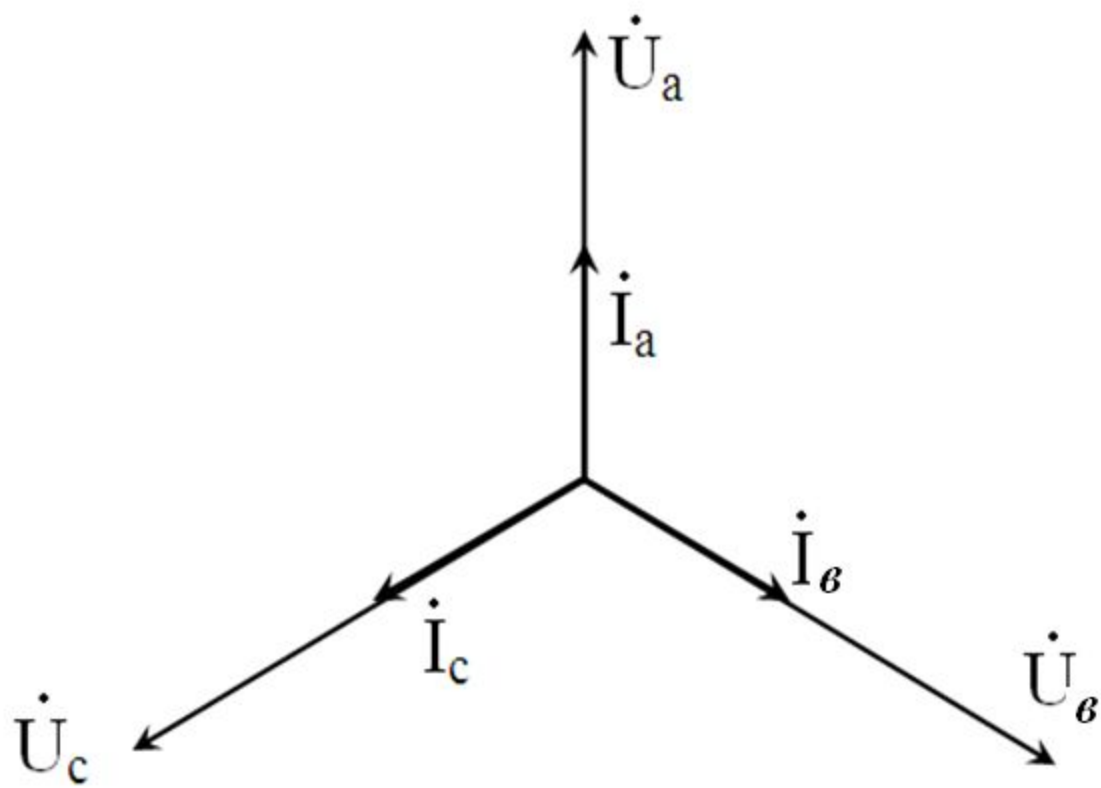
$$\dot{I}_a + \dot{I}_b + \dot{I}_c = 11 + 11 e^{-j120^{\circ}} + 11 e^{j120^{\circ}} = 0$$



$$\dot{I}_a + \dot{I}_b + \dot{I}_c = \dot{I}_N$$

$$\dot{I}_N = 0$$

Problem 2

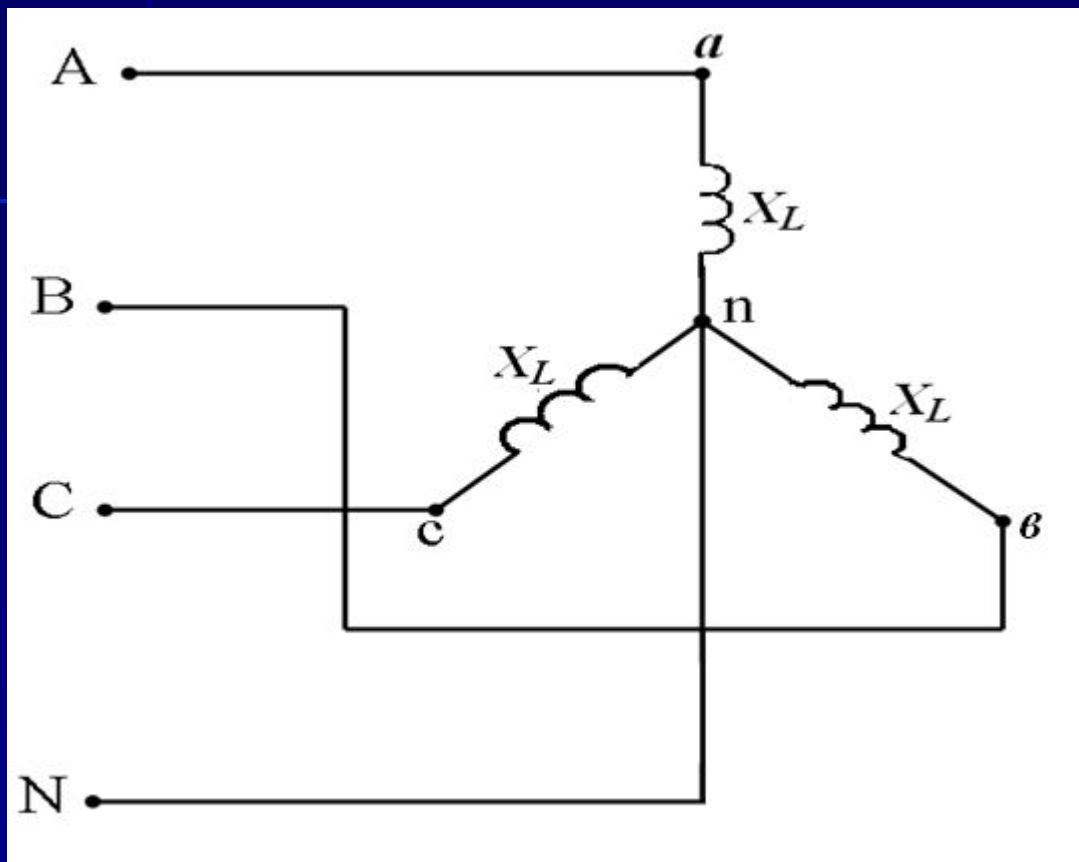

Given:

$$V_L = 380 \text{ V}$$

$$X_L = 20 \text{ Ohm}$$

Define:



$$I_a, I_b, I_c, I_N - ?$$

$$U_\phi = \frac{U_L}{\sqrt{3}} = 220 \text{ V}$$

$$\dot{I}_a = \frac{\dot{U}_a}{jX_L} = \frac{U_\phi}{e^{j90^\circ} X_L} = \frac{220}{20e^{j90^\circ}} = 11e^{-j90^\circ}$$


$$\dot{I}_e = \frac{\dot{U}_e}{jX_L} = \frac{220e^{-j120^\circ}}{20e^{j90^\circ}} = 11e^{-j210^\circ}$$
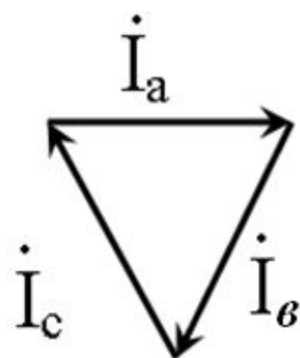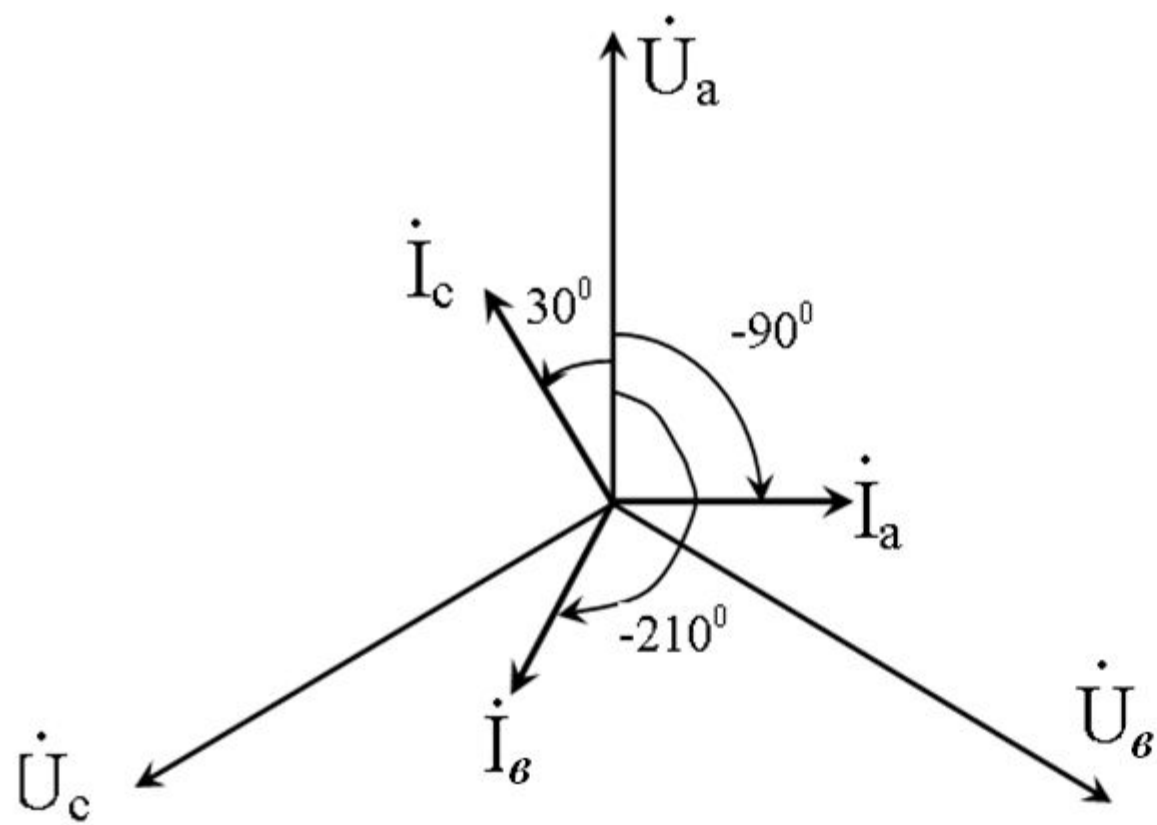
$$\dot{I}_c = \frac{\dot{U}_c}{jX_L} = \frac{220e^{j120^\circ}}{20e^{j90^\circ}} = 11e^{j30^\circ}$$



$$\dot{I}_N = 0$$

Problem 3

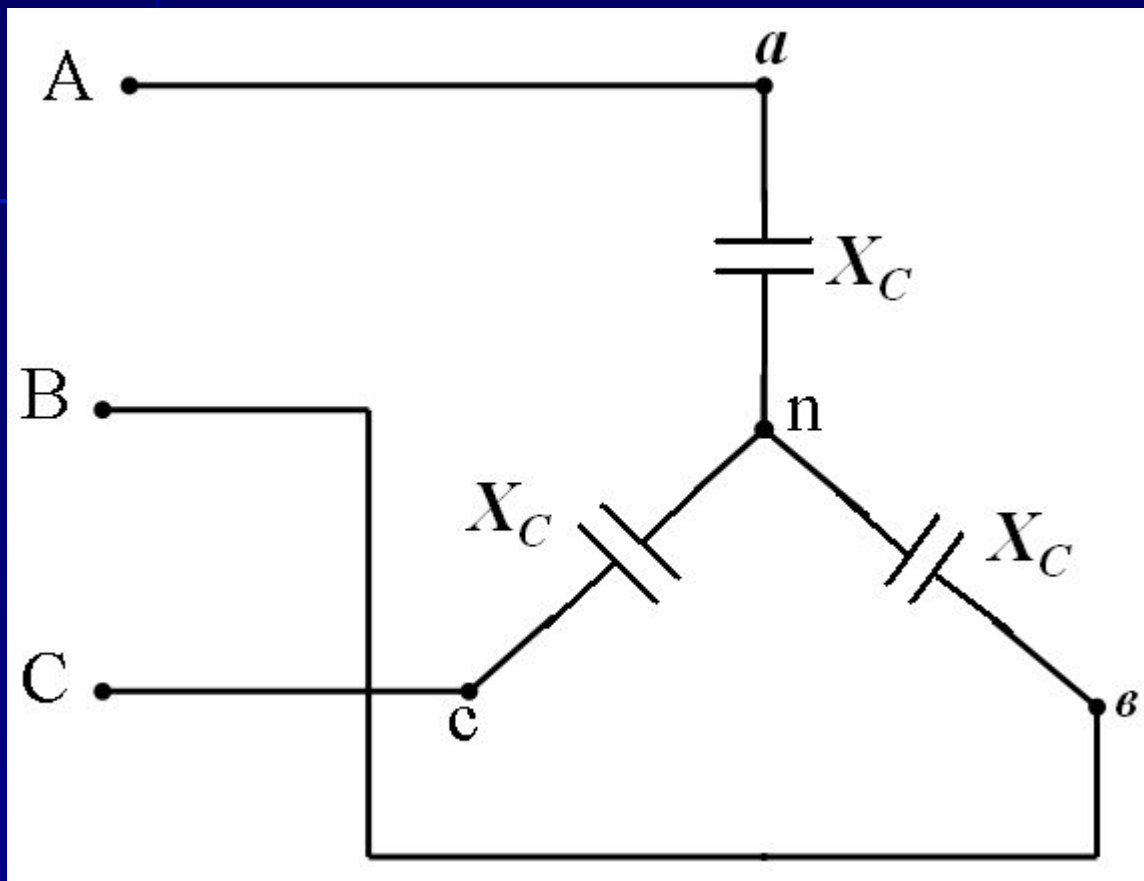

Given:

$$V_L = 660 \text{ V}$$

$$X_C = 10 \text{ Ohm}$$

Determine:



$$I_a, I_e, I_c, I_N - ?$$

$$U_\phi = \frac{U_\pi}{\sqrt{3}} = 380 \text{ B}$$

$$\dot{I}_a = \frac{\dot{U}_a}{-jX_c} = \frac{U_\phi}{e^{-j90^\circ} X_c} = \frac{380e^{j90^\circ}}{10} = 38e^{j90^\circ}$$


$$\dot{I}_e = \frac{\dot{U}_e}{-jX_c} = \frac{380e^{-j30^\circ}}{10} = 38e^{-j30^\circ}$$
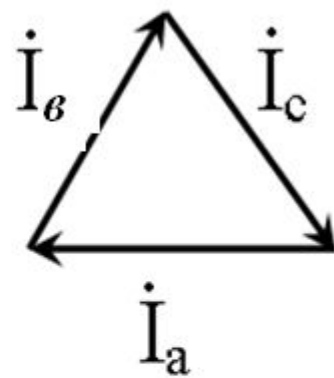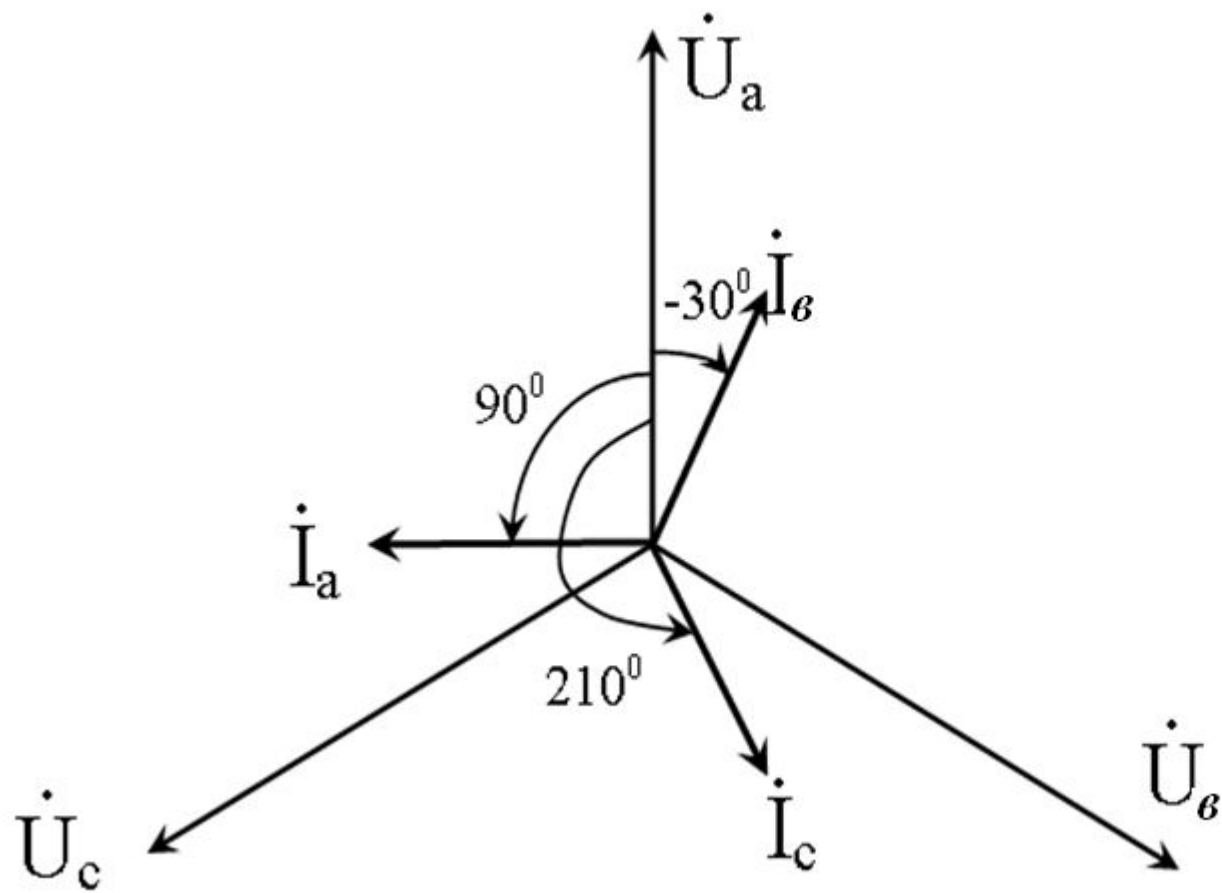
$$\dot{I}_c = \frac{\dot{U}_c}{-jX_c} = \frac{380e^{j210^\circ}}{10} = 38e^{j210^\circ}$$



$$\dot{I}_N = 0$$

Problem 4

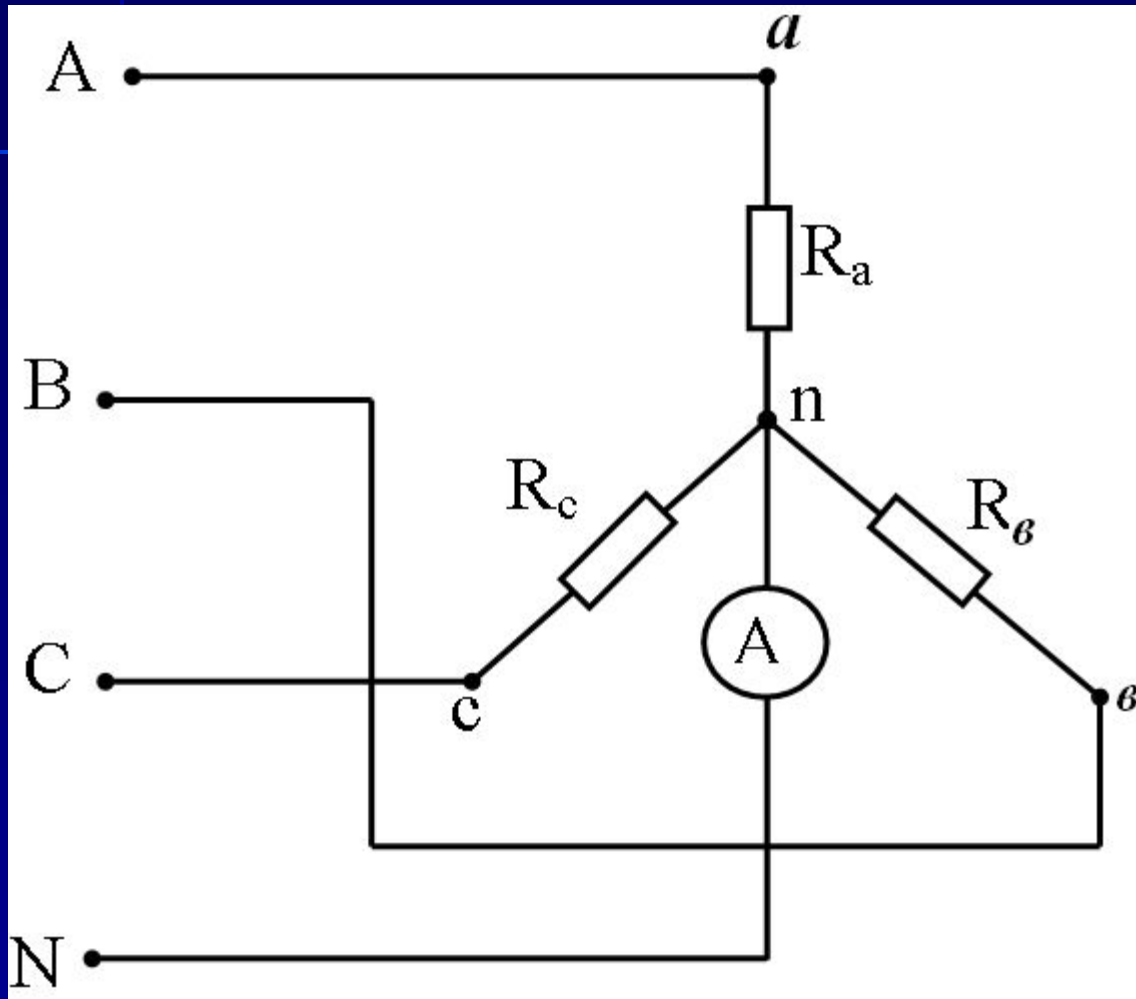

Given:

$$U_{\text{л}} = 220 \text{ B}$$

$$R_a = R_b = 10 \text{ Ом}$$

$$R_c = 20 \text{ Ом}$$


Define:

$$I_N - ?$$



$$U_{\phi} = \frac{U_{\text{л}}}{\sqrt{3}} = 127 \text{ B}$$

$$I_a = I_{\text{в}} = \frac{U_{\phi}}{R_a} = \frac{127}{10} = 12,7 \text{ A}$$
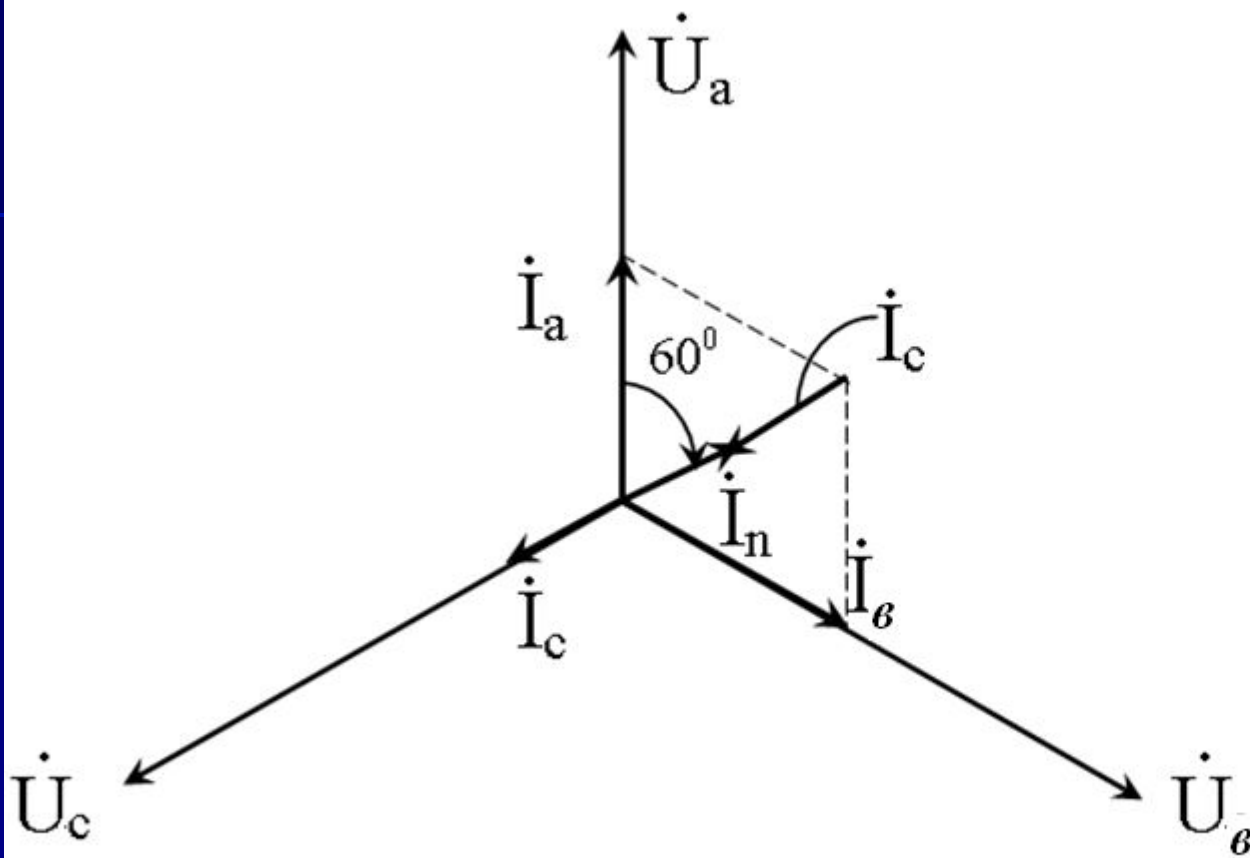
$$I_c = \frac{U_{\phi}}{R_c} = \frac{127}{20} = 6 \text{ A}$$



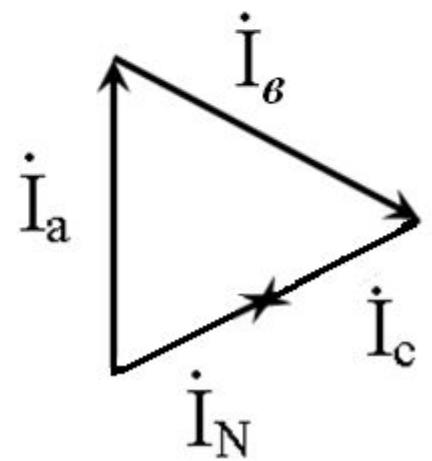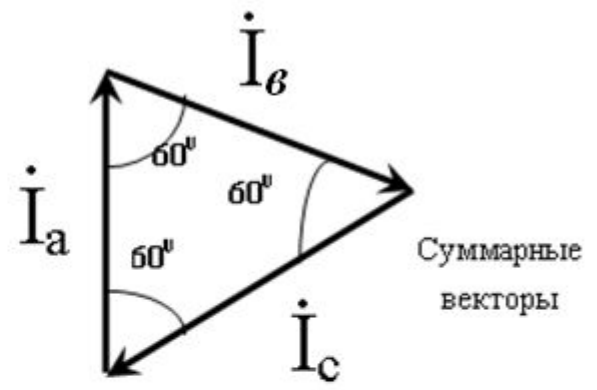
$$\dot{I}_a + \dot{I}_b + \dot{I}_c = \dot{I}_N$$



$$I_N = 6,7 e^{-j60^\circ}$$

Problem 5

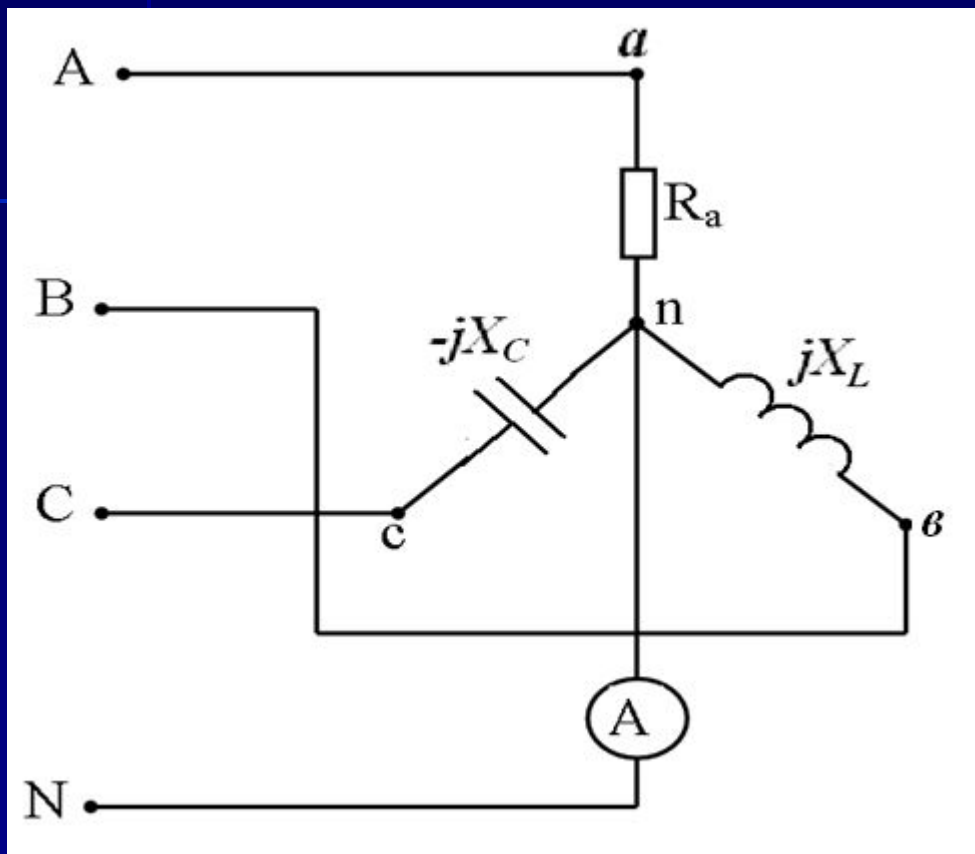

Given:


$$V_L = 380 \text{ V}$$

$$R_a = X_b = X_c = 10 \text{ ohm}$$

Define:

$$I_a, I_b, I_c, I_N - ?$$
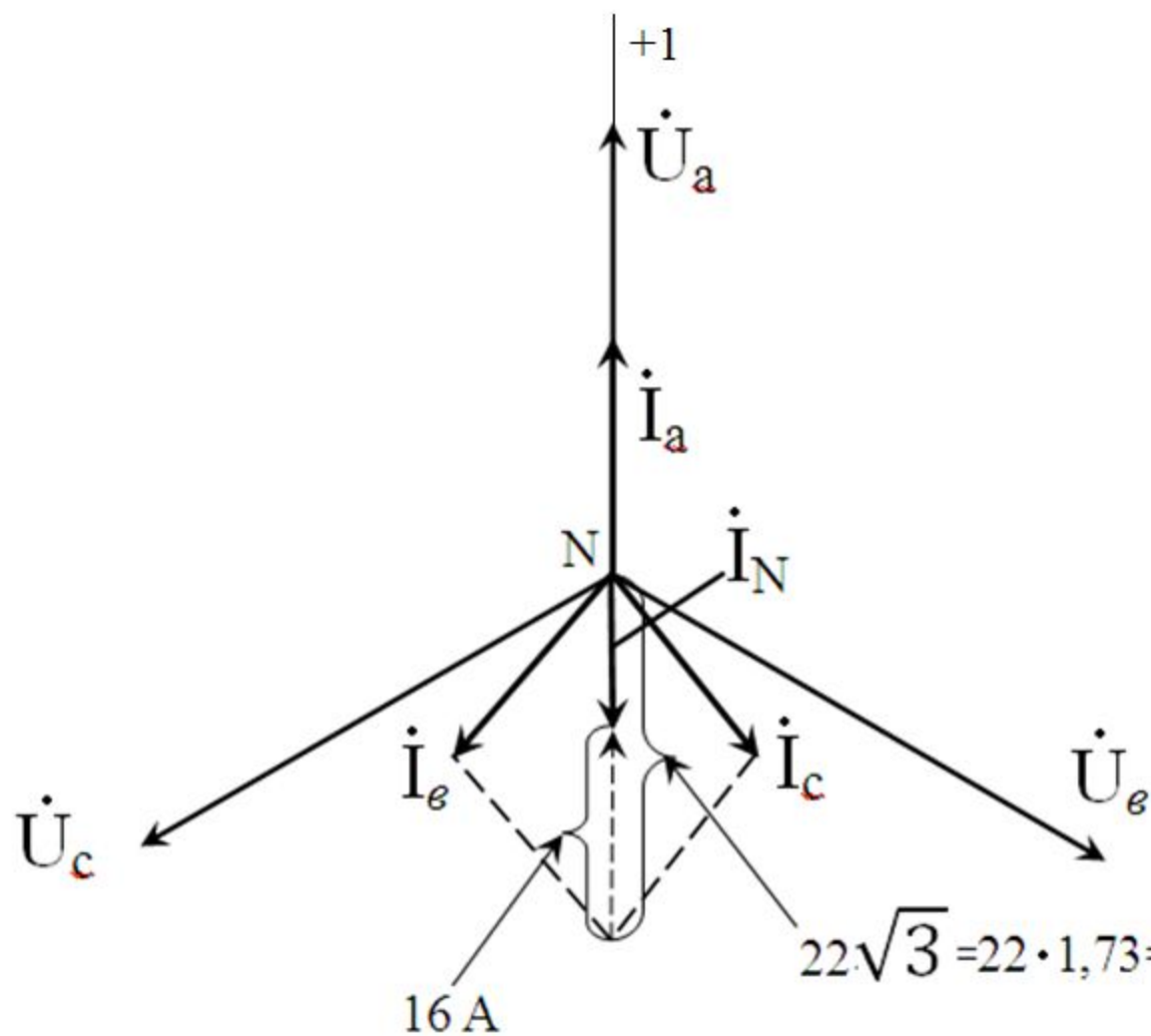
$$I_a = I_b = I_c = \frac{U_\phi}{Z_\phi} = \frac{220}{10} = 22 \text{ A}$$




$$\dot{I}_N = \dot{I}_a + \dot{I}_e + \dot{I}_c = 16e^{j180^\circ}$$

$$I_N = 16 \text{ A}$$

$$22\sqrt{3} = 22 \cdot 1.73 = 38 \text{ B}$$

$$38 - 22 = 16 \text{ A}$$

Если поменять с местами X_e и X_c

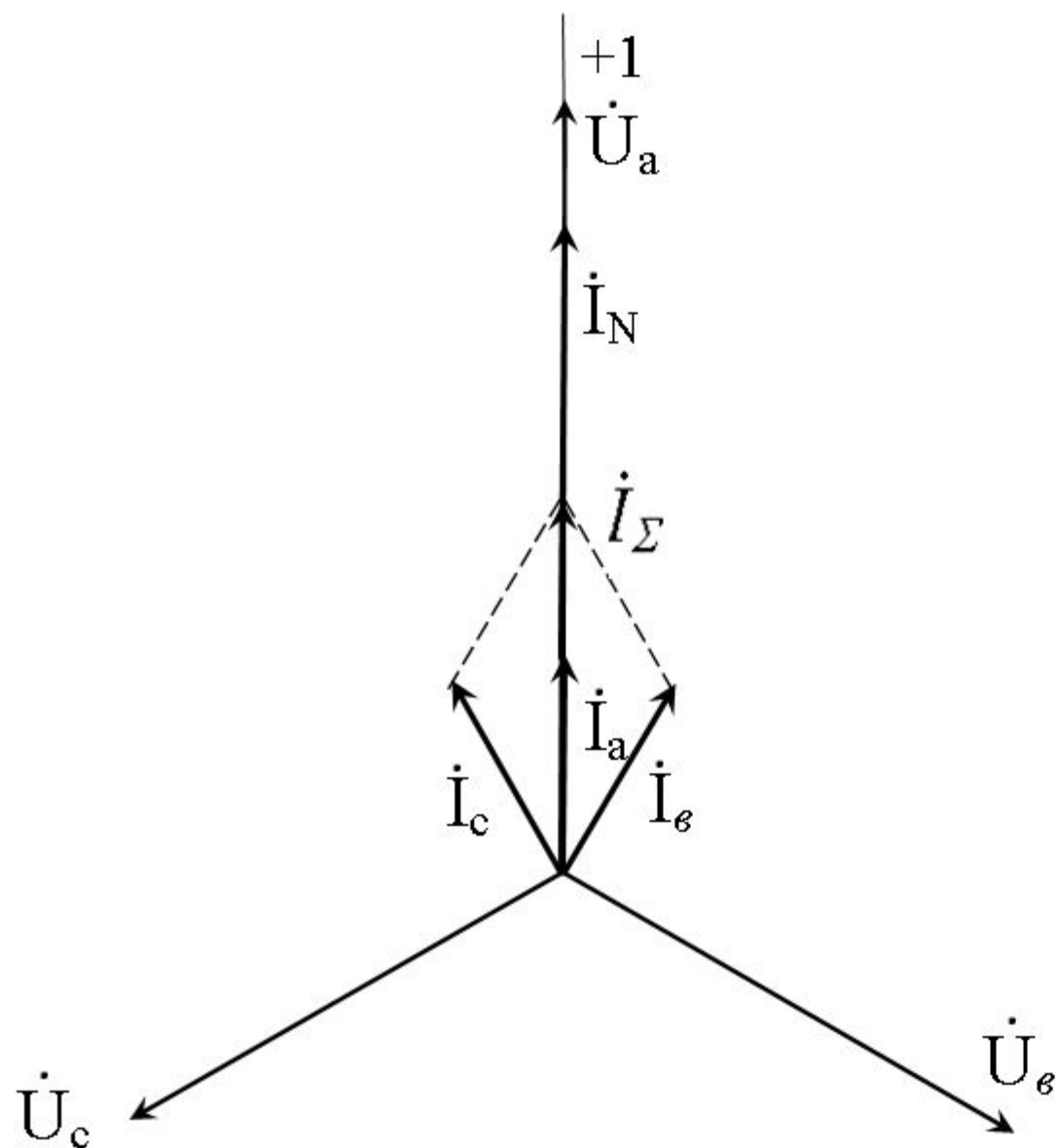

$$\dot{I}_a = \dot{I}_e = \dot{I}_c = 22 A$$


$$\text{Сумма } \dot{I}_e + \dot{I}_c = \dot{I}_\Sigma e^{j0} = 38 A$$

$$\dot{I}_N = 38 + 22 = 60 A$$

$$\begin{aligned} \dot{I}_N &= \dot{I}_a + \dot{I}_e + \dot{I}_c = \\ &= 60 e^{j0} = 60 A \end{aligned}$$

$$\dot{I}_N = 60 A$$

Problem 6

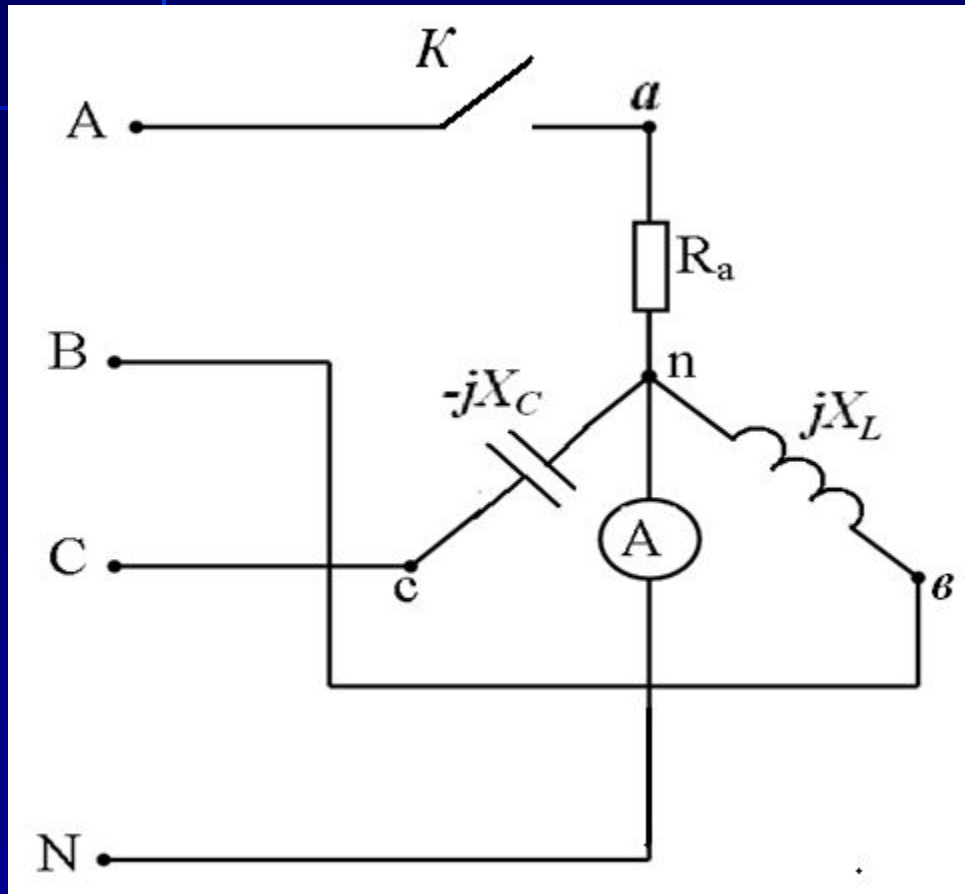


Given:

$$V_{\text{л}} = 380 \text{ V}$$

$$R_a = X_e = X_c = 10 \text{ Ohm}$$

Define:


$$I_N - ?$$

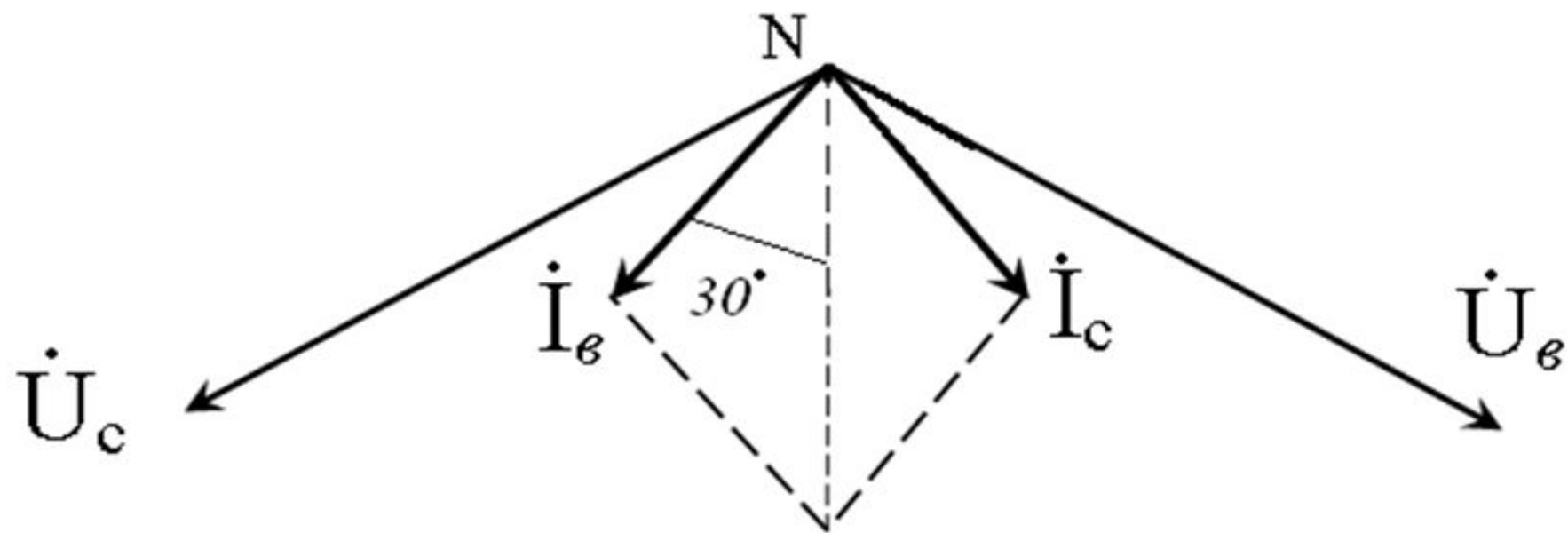

$$\dot{I}_N = \dot{I}_e + \dot{I}_c;$$

$$I_N = 38 \text{ A}$$

Problem 7

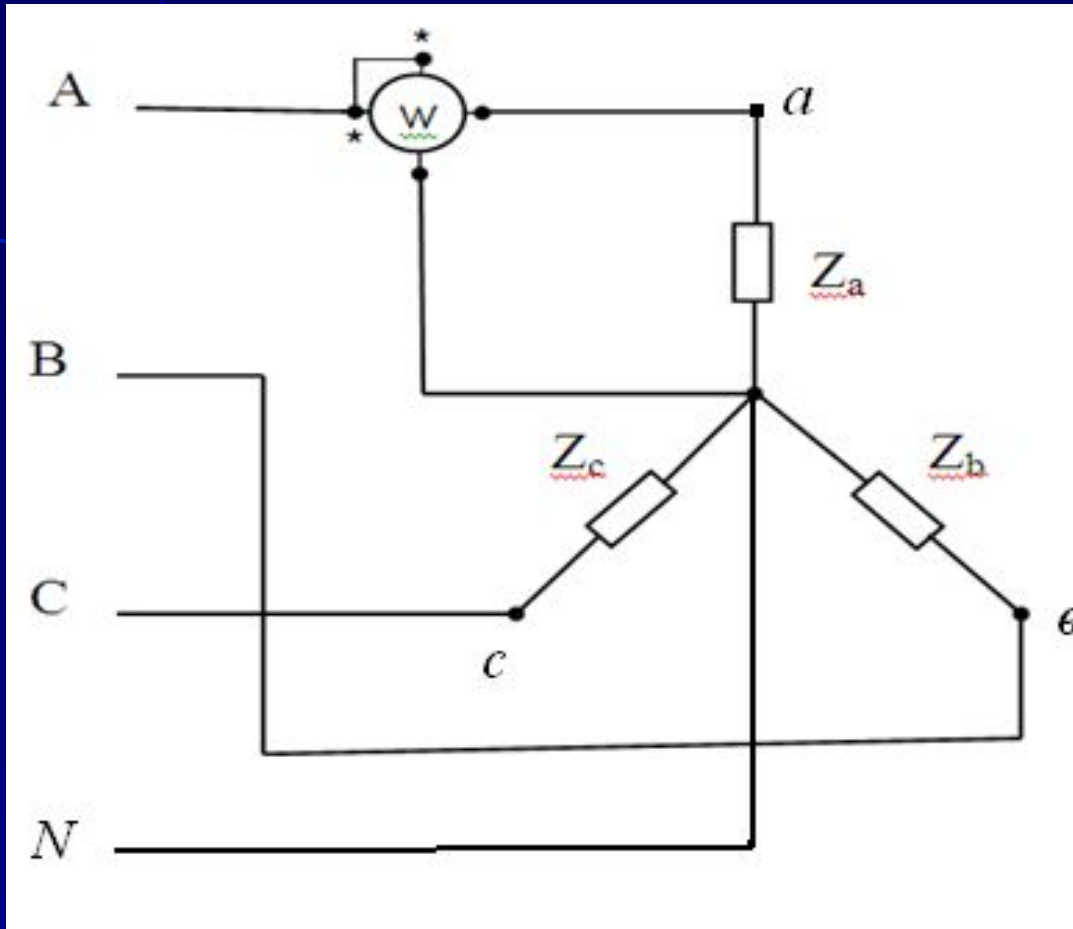

Given

$$V_L = 380 \text{ V}$$


$$I_a = 2 \text{ A}; \cos \phi = 0,8$$

Define:

$$P_w = ?$$

$$P_w = U_a I_a \cos(\hat{U}_a, \hat{I}_a) = 220 \cdot 2 \cdot 0,8 = 352 \text{ W}$$

Problem 8

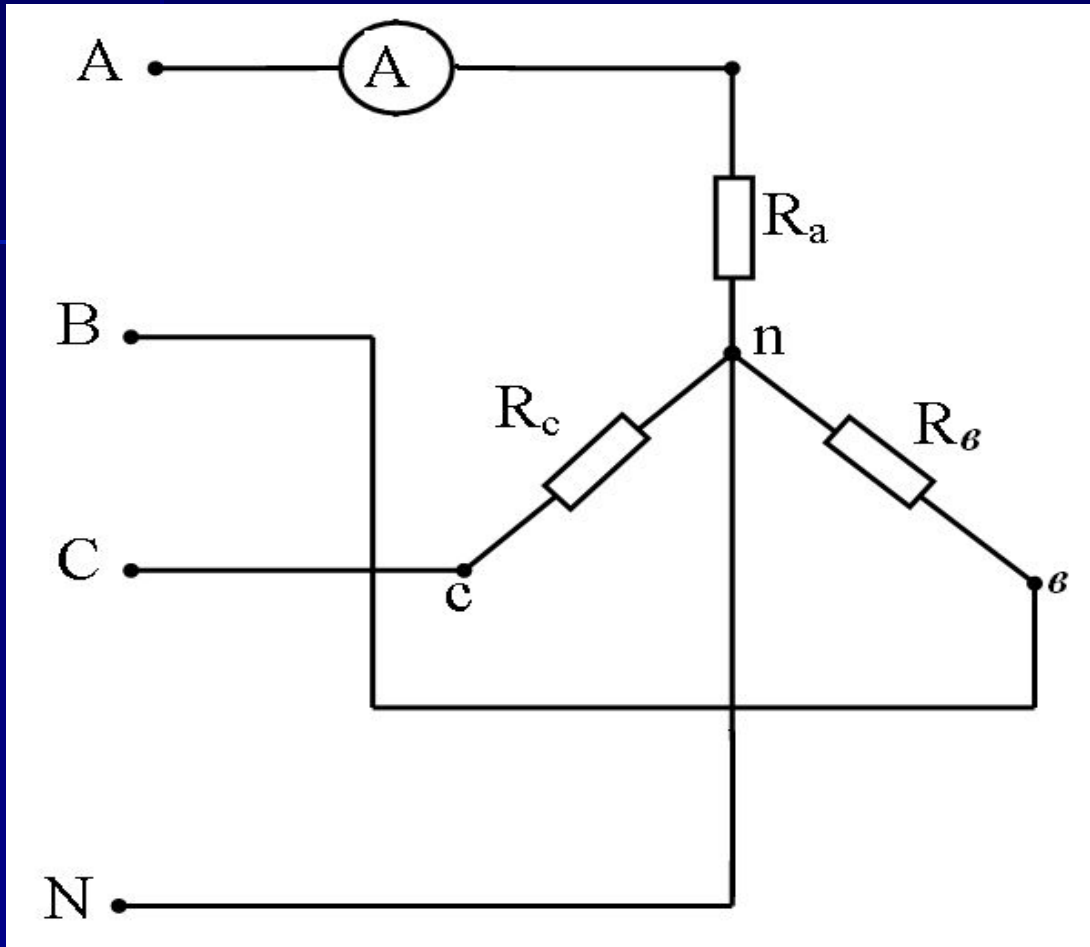

Given

$$\underline{U}_l = 380 \text{ B}$$

$$R_a = 10 \text{ Ом};$$

$$R_b = 20 \text{ Ом};$$

$$R_c = 30 \text{ Ом}.$$

Define instrument readings - ?

$$I_a = \frac{U_a}{R_a} = \frac{220}{10} = 22 \text{ A}$$

Problem 9

Given:

$$S=1000 \text{ VA}$$

$$P=600 \text{ Wt.}$$


Define:

Power factor - ?

$$P = UI \cos \varphi = S \cos \varphi$$

$$\cos \varphi = \frac{P}{S} = 0,6$$

Problem 10

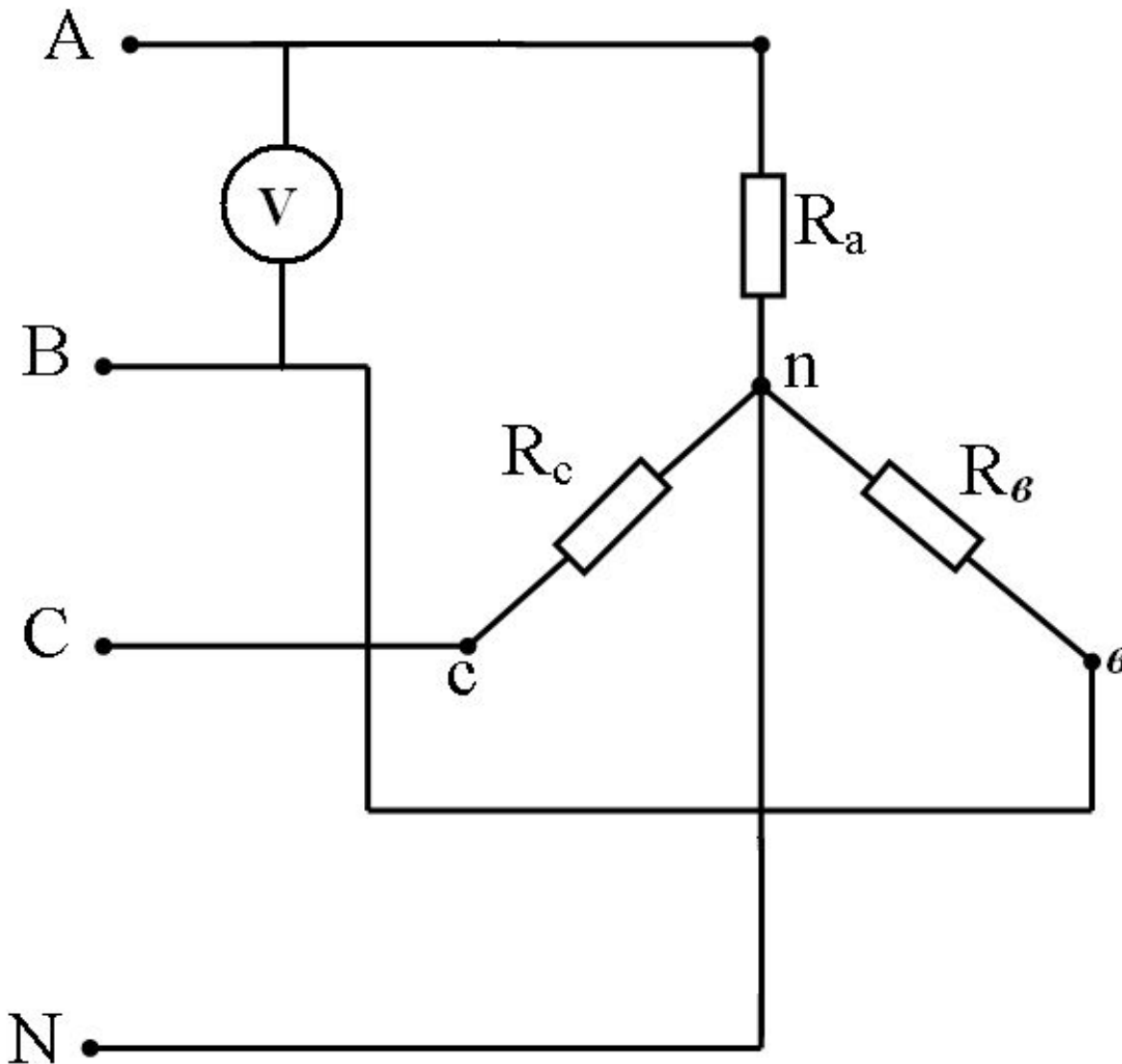

Given:

$$R_a = 10 \text{ } \Omega,$$

$$R_b = 20 \text{ } \Omega,$$

$$R_c = 30 \text{ } \Omega,$$

$$I_{\text{л}} = 22 \text{ A.}$$


Define instrument readings - ?

$$I_a = I_l = 22 \text{ A}$$

$$U_\phi = R_a \cdot I_a = 10 \cdot 22 = 220 \text{ B}$$

$$U_l = \sqrt{3} \cdot U_\phi = 1,73 \cdot 220 = 380 \text{ B}$$

Problem 11

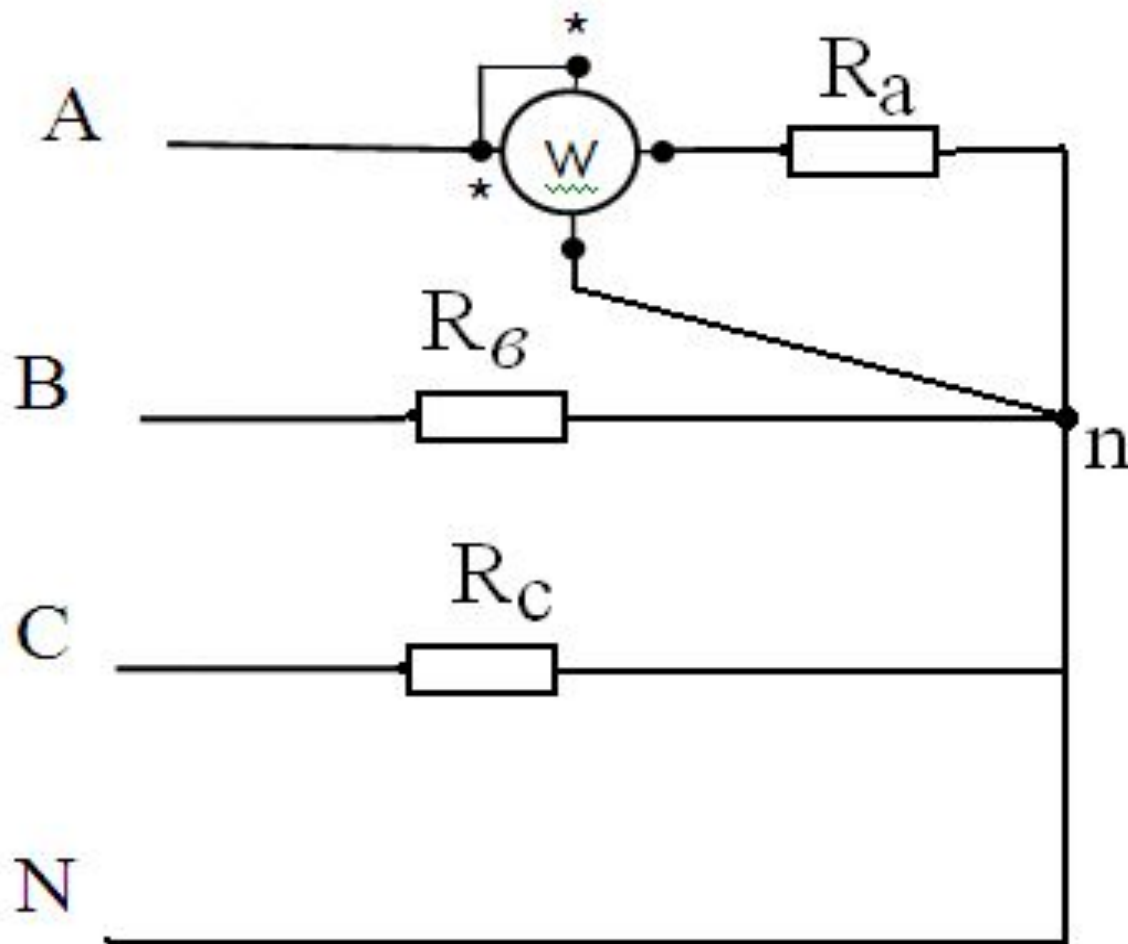

Given:

$$R_a = 10 \text{ } \Omega,$$

$$R_b = 20 \text{ } \Omega,$$

$$R_c = 30 \text{ } \Omega,$$

$$I_a = 22 \text{ A.}$$

Define
instrument
readings - ?


$$P_w = I_a^2 R_a = 484 \cdot 10 = 4840 \text{ W}$$

Three-wire three-phase chain (practical training)

For symmetrical receiver phase connections, a three-wire three-phase circuit is used by the star.

Symmetrical receiver - three-phase electric motors, electric furnaces.

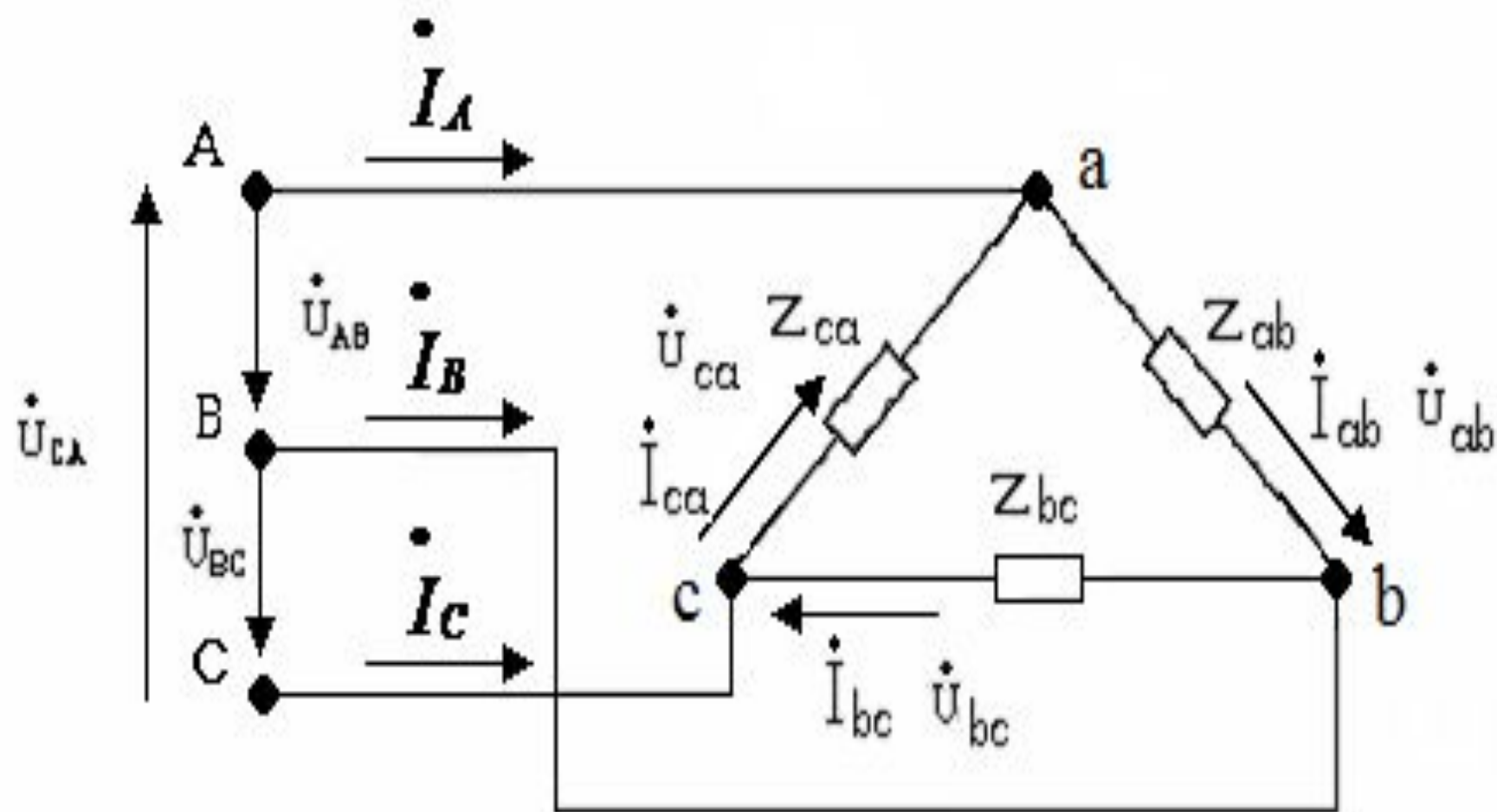A three-wire three-phase circuit can be used under an unsymmetrical load, but the load is connected by a triangle.



$$\dot{U}_{ab} = \dot{U}_{AB} = U_{\text{л}} e^{j30^\circ}$$

$$\dot{U}_{bc} = \dot{U}_{BC} = U_{\text{л}} e^{-j90^\circ}$$

$$\dot{U}_{ca} = \dot{U}_{CA} = U_{\text{л}} e^{j150^\circ}$$

$$U_{\phi} = U_{\text{л}}; \quad I_{\text{л}} = \sqrt{3} I_{\phi}.$$

At symmetrical loading


$$\dot{I}_A = \dot{I}_{ab} - \dot{I}_{ca};$$

$$\dot{I}_B = \dot{I}_{bc} - \dot{I}_{ab};$$


$$\dot{I}_C = \dot{I}_{ca} - \dot{I}_{bc};$$

$$\dot{I}_A + \dot{I}_B + \dot{I}_C = 0;$$

At any loading

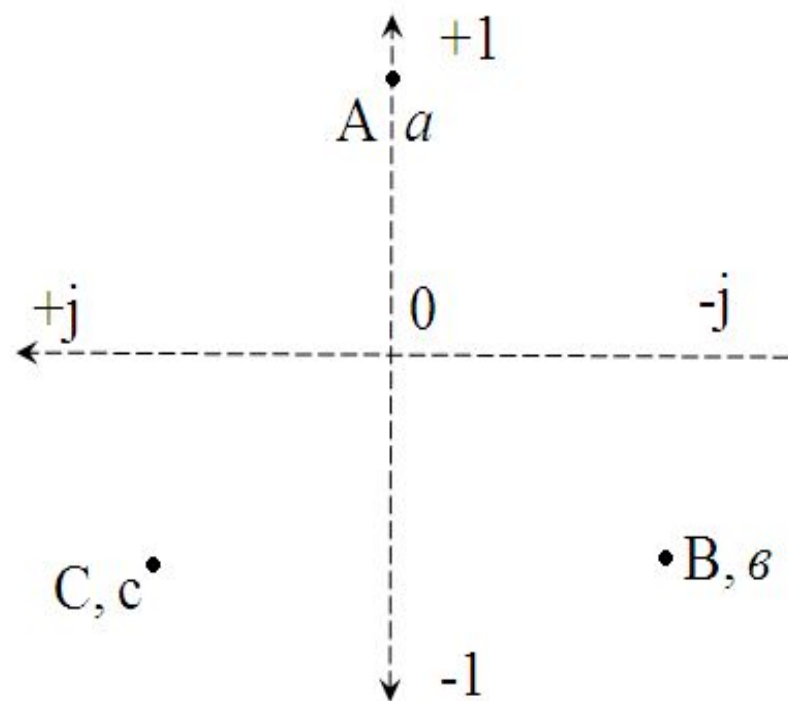

Потенциальная диаграмма

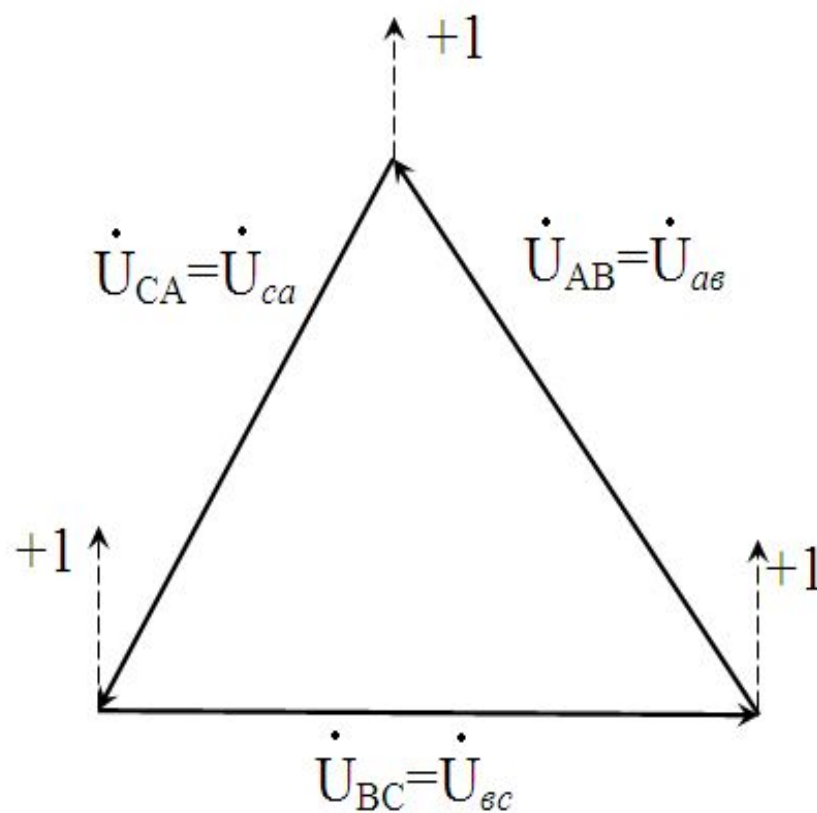

Векторная диаграмма

Problem 1

Given:

$$V_L = 380 \text{ B}, \quad R_{a\phi} = R_{\phi c} = R_{ca} = R = 10 \text{ Ом}$$



Define: I_ϕ, I_π - ?

Solution:

$$U_\phi = U_\pi = 380 \text{ V}$$

$$I_\phi = I_{a\phi} = I_{\phi c} = I_{ca} = U_\phi / R = 380 / 10 = 38 \text{ A}$$

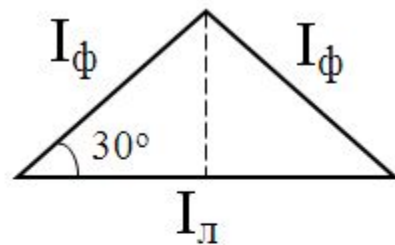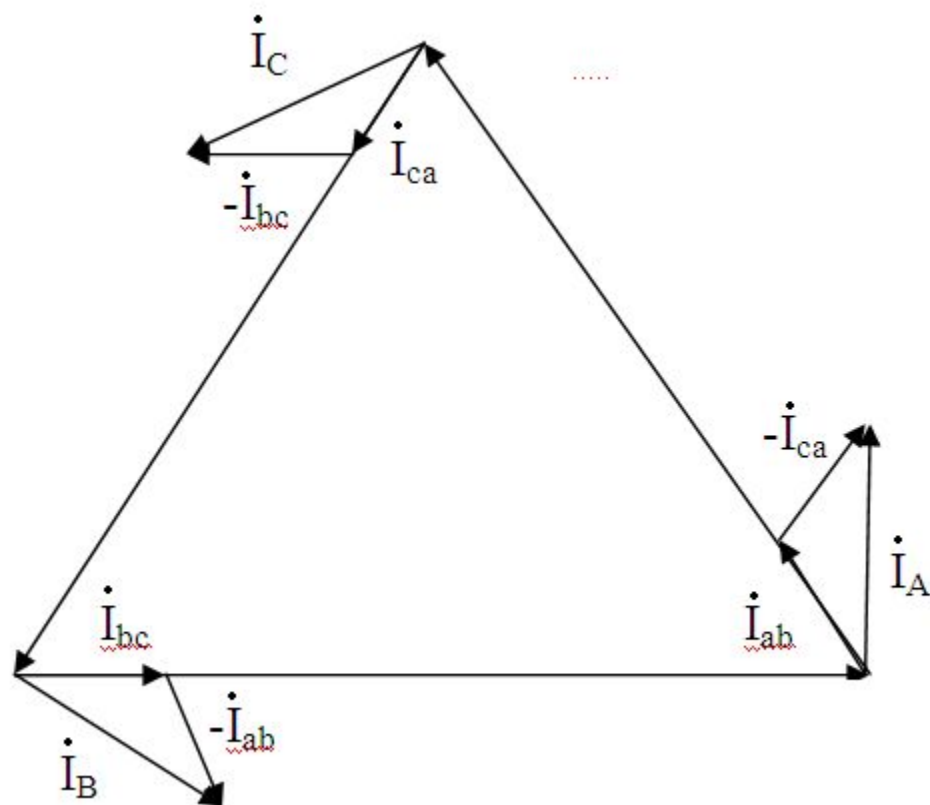
$$\dot{I}_A = \dot{I}_{a\phi} - \dot{I}_{ca}; \quad \dot{I}_B = \dot{I}_{\phi c} - \dot{I}_{a\phi}; \quad \dot{I}_C = \dot{I}_{ca} - \dot{I}_{\phi c}.$$



$$\frac{I_L}{2} = I_\phi \cos 30^\circ = I_\phi \frac{\sqrt{3}}{2}$$

$$I_L = \sqrt{3} I_\phi = \sqrt{3} \cdot 38 = 66 \text{ A}$$

Problem 2

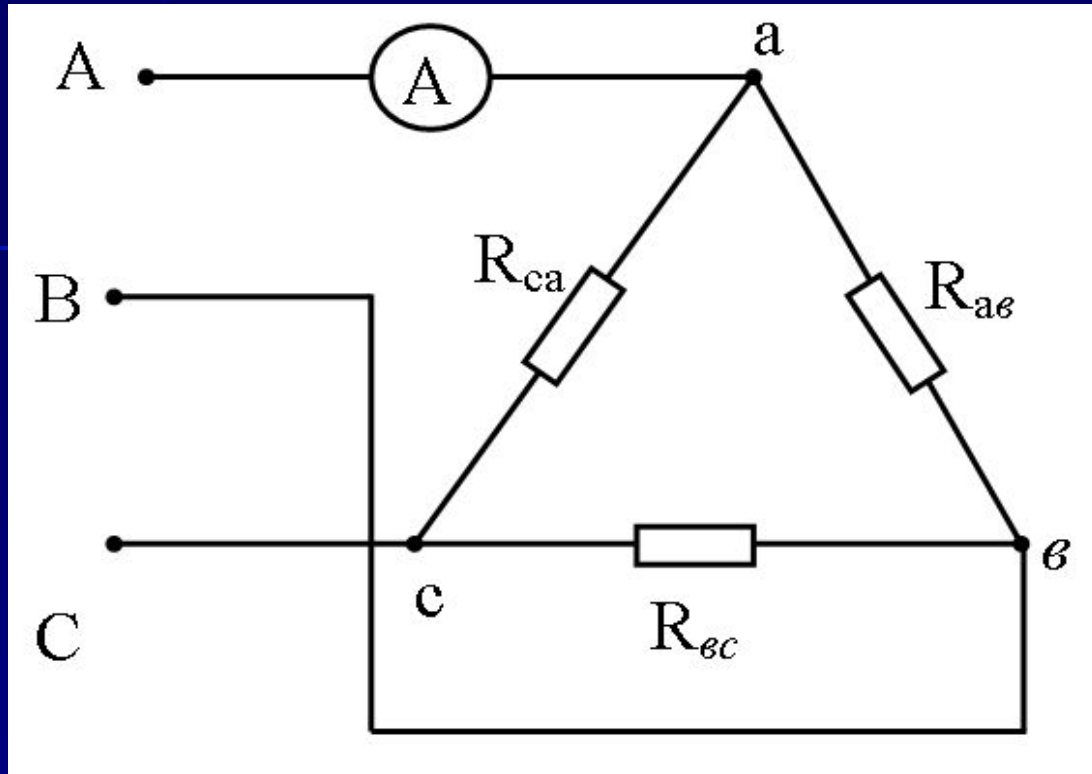

Given:

$$V_L = 220 \text{ V}$$


$$R_{ae} = R_{ca} = R_{ec} = 10 \text{ Ohm.}$$

Determine of reading ammeter I_L - ?

$$I_L = \sqrt{3} I_\phi \quad I_\phi = \frac{U_L}{R_\phi} = \frac{U_\phi}{R_\phi} = \frac{220}{10} = 22 \text{ A}$$

$$I_L = 1,73 \cdot 22 = 38 \text{ A}$$

Problem 3

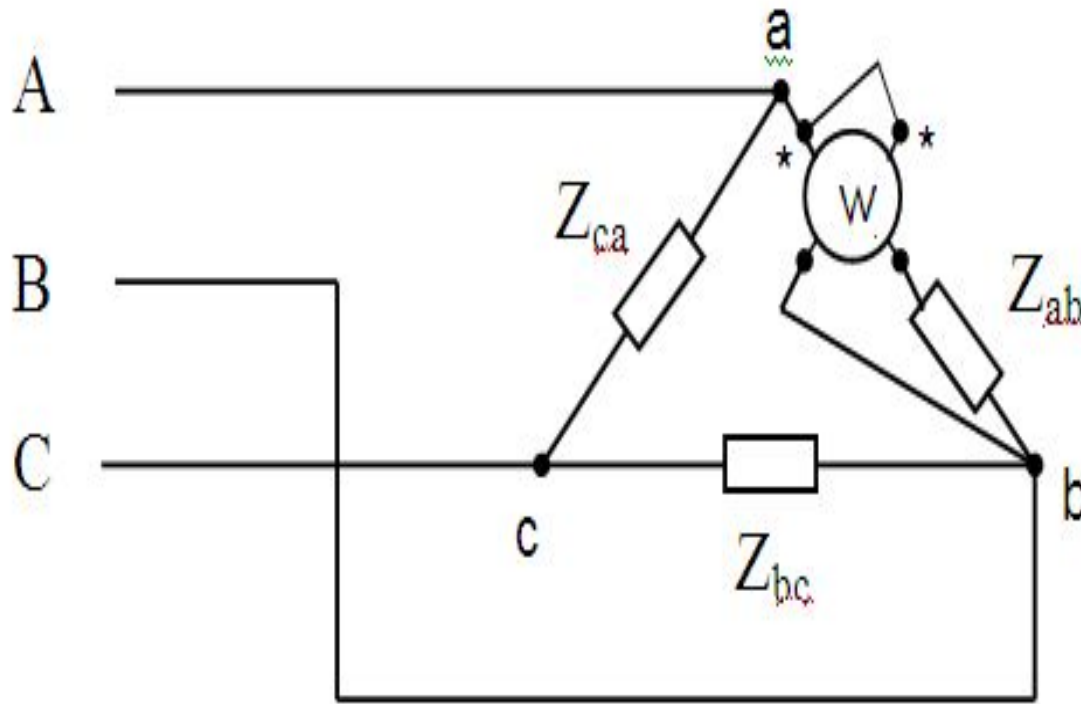

Given

$$V_L = 220 \text{ V}$$

$$I_L = 17,3 \text{ A}$$

$$\cos \phi = 0.6$$


$$Z_{ab} = Z_{bc} = Z_{ca} = Z$$

Determine of reading
wattmeter- ?

$$I_\phi = \frac{I_L}{\sqrt{3}} = \frac{17,3}{\sqrt{3}} = 10 \text{ A}$$

$$\begin{aligned} P_w &= U_\phi I_\phi \cos(\hat{U}_\phi, I_\phi) = U_{ab} I_{ab} \cos \varphi_\phi = \\ &= 220 \cdot \frac{17,3}{1,73} \cdot 0,6 = 1320 \text{ W} \end{aligned}$$

Problem 4

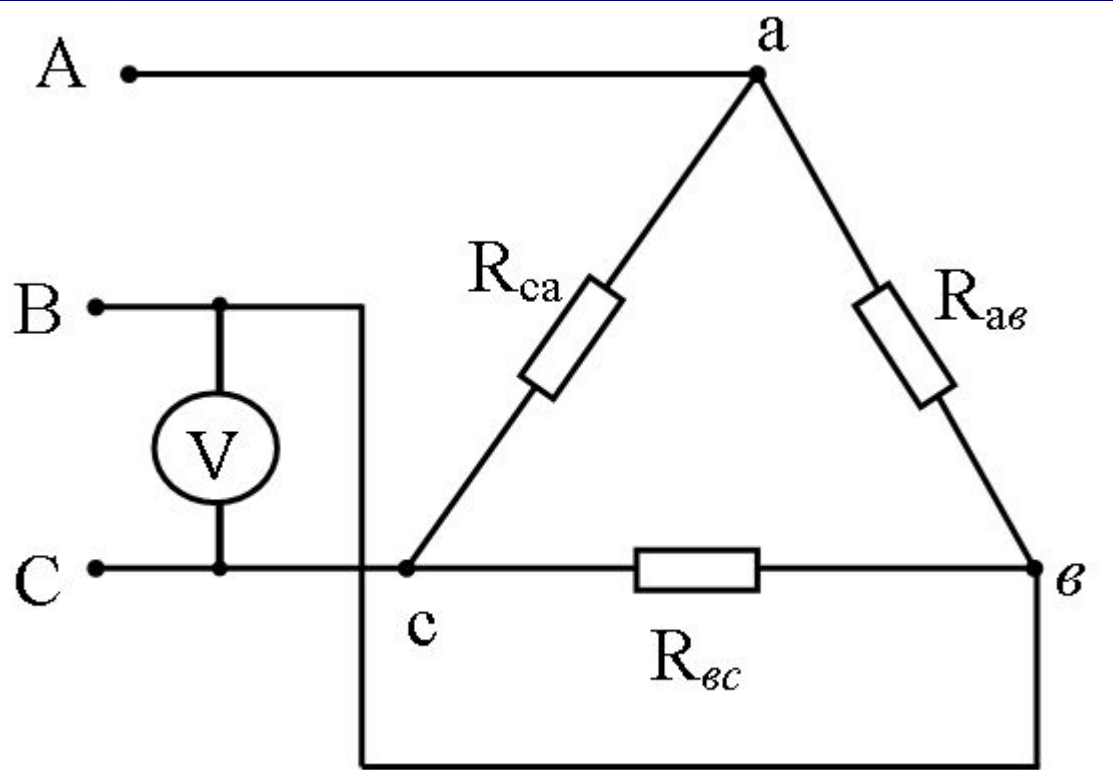

Given

$$I_{ae} = 22 \text{ A},$$

$$R_{ae} = 10 \text{ } \Omega,$$

$$R_{ec} = 20 \text{ } \Omega,$$

$$R_{ca} = 30 \text{ } \Omega.$$

Determine of
reading
voltmeter- ?

$$U_{BC} = U_l = U_\phi = I_{ae} \cdot R_{ae} =$$

$$= 22 \cdot 10 = 220 \text{ V}$$

Problem 5

Given: $V_L = 220 \text{ V}$

$$R_{a\bar{b}} = 10 \text{ } \Omega, \quad R_{\bar{b}c} = 4 \text{ } \Omega, \quad R_{ca} = 5 \text{ } \Omega$$

$$\dot{U}_{AB} = 220 e^{j30^\circ} \quad \phi_{a\bar{b}} = \phi_{\bar{b}c} = \phi_{ca} = \phi = 0$$

Define:

$$I_{a\bar{b}}, I_{\bar{b}c}, I_{ca}, I_A, I_B, I_C - ?$$

Solution:

$$\dot{I}_{a\bar{b}} = \frac{\dot{U}_{a\bar{b}}}{R_{a\bar{b}}} = \frac{U_{\text{л}} e^{j30^\circ}}{R_{a\bar{b}}} = 22 e^{j30^\circ}$$


$$\dot{I}_{bc} = \frac{\dot{U}_{bc}}{R_{bc}} = \frac{220 e^{-j90^\circ}}{4} = 55 e^{-j90^\circ}$$

$$\dot{I}_{ca} = \frac{\dot{U}_{ca}}{R_{ca}} = \frac{220 e^{j150^\circ}}{5} = 44 e^{j150^\circ}$$

$$\dot{I}_A = \dot{I}_{ab} - \dot{I}_{ca} = 58,1 e^{-j10,55^\circ}$$


$$\dot{I}_B = \dot{I}_{bc} - \dot{I}_{ab} = 68,6 e^{-j106^\circ}$$

$$\dot{I}_C = \dot{I}_{ca} - \dot{I}_{bc} = 86 e^{j116^\circ}$$

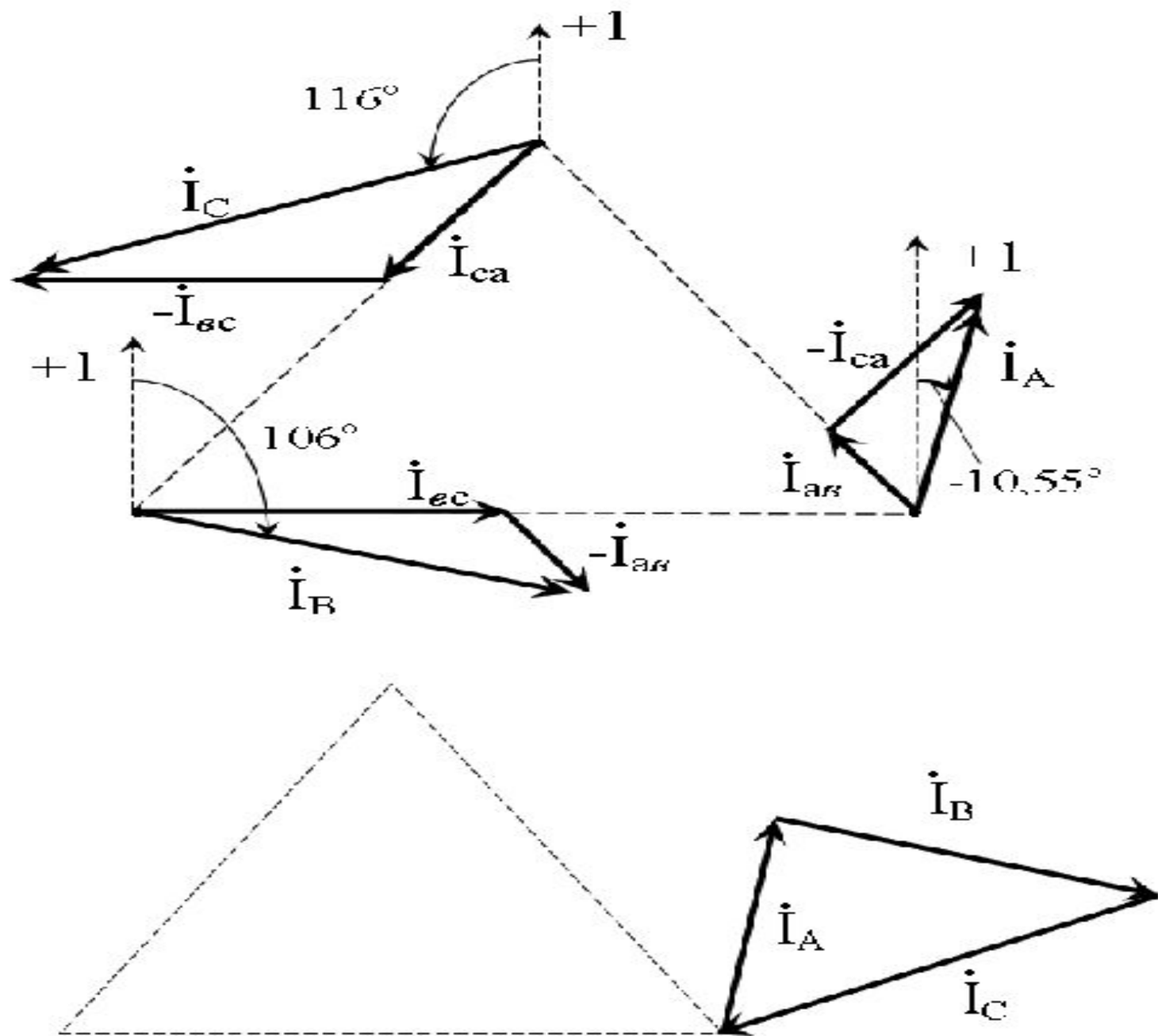

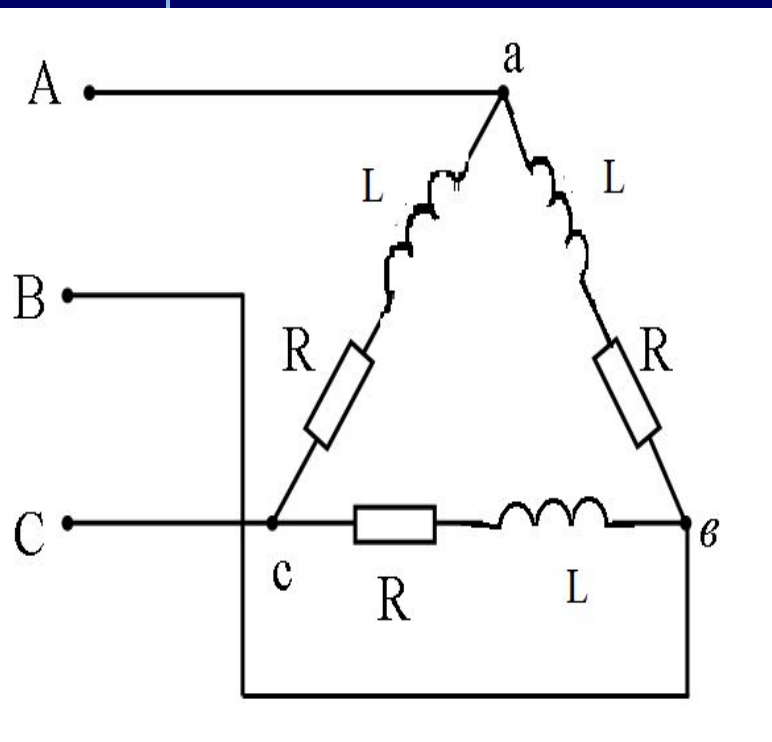Problem 6

Симметричная нагрузка,
включенная треугольником.



$$R = X_L = 50 \text{ Ом}; U_{\text{л}} = 380 \text{ В.}$$

Решение:

Полное сопротивление фазы

$$Z_{\phi} = \sqrt{R^2 + X_L^2} = 70.7 \text{ Ом}$$

$$U_{\phi} = U_{\text{л}} = 380 \text{ В}$$

$$I_{\phi} = U_{\phi} / Z_{\phi} = 5.37 \text{ А}$$


$$I_{\text{л}} = \sqrt{3} \cdot I_{\phi} = 9.3 \text{ А}$$

Фазный ток

Линейный ток

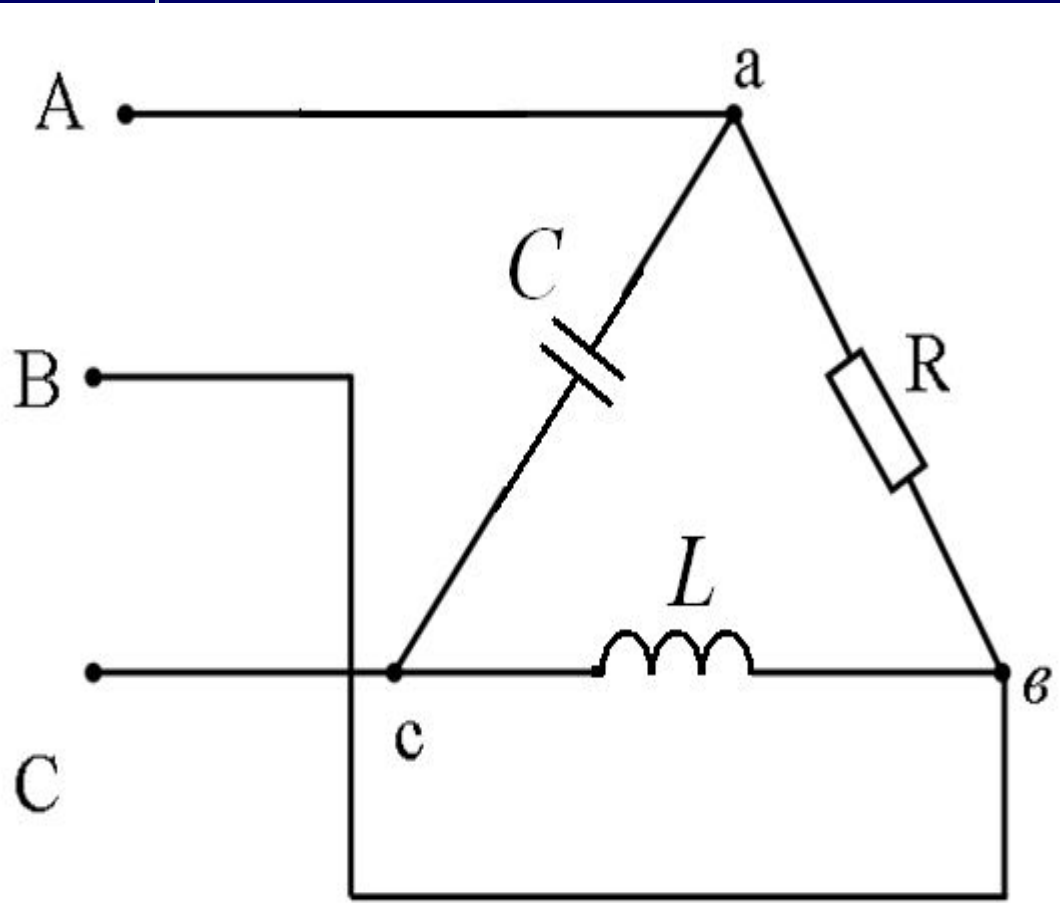Problem 7

The asymmetric load included by the triangle.



Given:

$$R = X_L = X_C = 10 \, \Omega$$

$$V_L = 220 \, V$$

Define:

$$I_\phi - ?$$

$$\dot{I}_{av} = \frac{\dot{U}_{av}}{Z_{av}} = \frac{\dot{U}_n}{R} = \frac{220 e^{j30^\circ}}{10} = 22 e^{j30^\circ} A$$

$$\dot{I}_{vc} = \frac{\dot{U}_{ec}}{Z_{vc}} = \frac{220 e^{-j90^\circ}}{j10} = 22 e^{-j180^\circ} A$$

$$\dot{I}_{ca} = \frac{\dot{U}_{ca}}{Z_{ca}} = \frac{220 e^{j150^\circ}}{-j10} = 22 e^{j240^\circ} A$$

