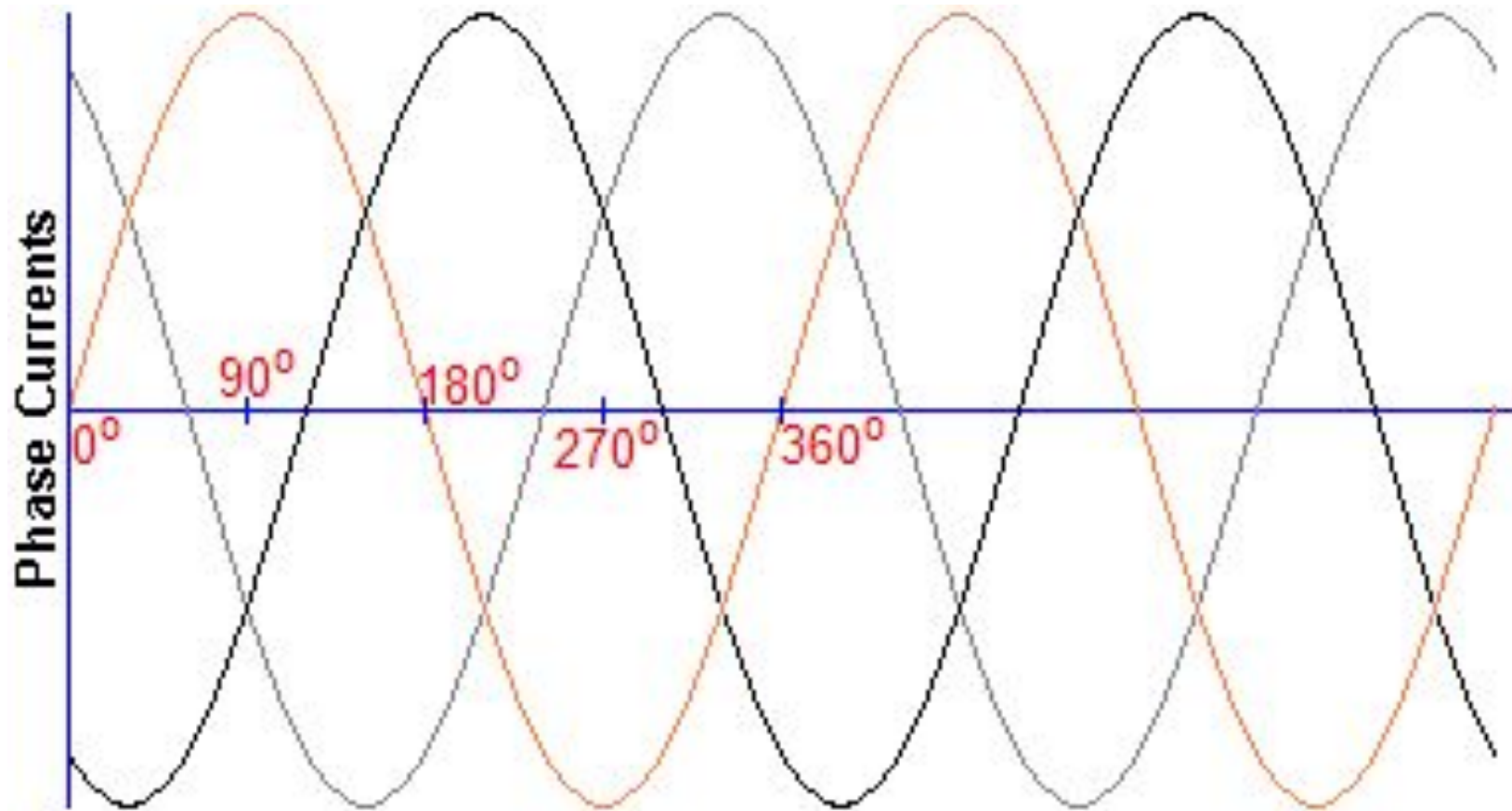



## **Unit 302: Principles of electrical science**

### **Star–delta configurations**

## Three-phase supplies



## Star connection

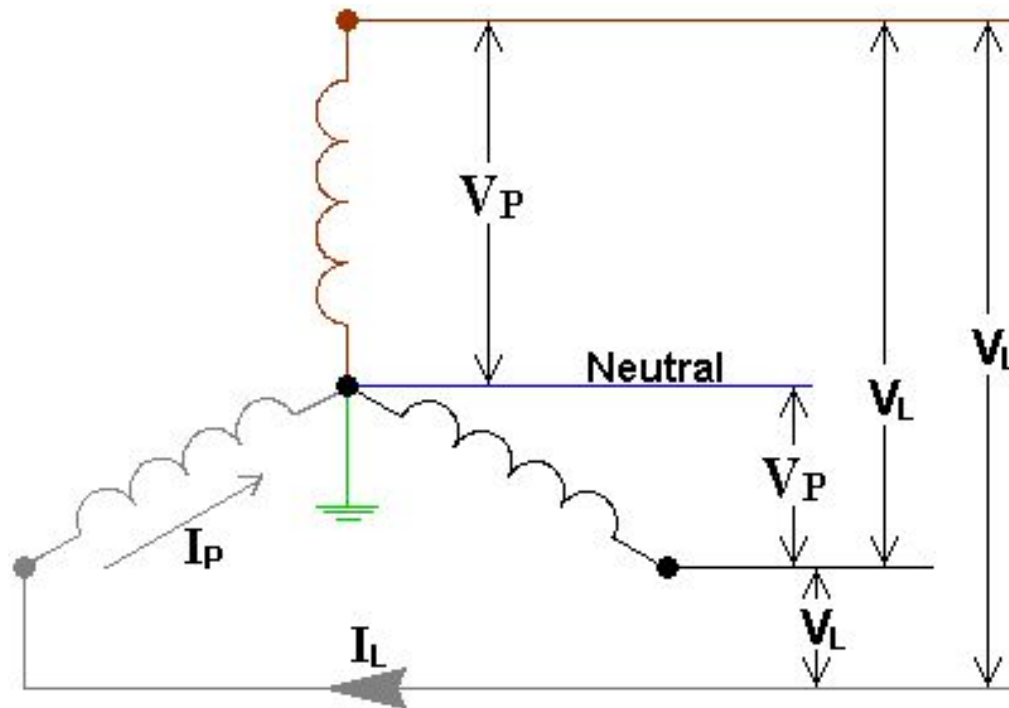

$$V_L = \sqrt{3} \times V_P$$

$$I_L = I_P$$

**EXAMPLE 1** – A three-phase, four-wire Star connected transformer has a line voltage of 520 volts and supplies a line current of 25 amps.

Calculate:

- ) the phase voltage of the transformer
- ) the phase current in each winding.


**a) In star**

$$\begin{aligned}V_L &= \sqrt{3} \times V_P \\V_P &= \frac{V_L}{\sqrt{3}} \\&= \frac{520}{\sqrt{3}} \\&= \mathbf{300 \text{ volts}}\end{aligned}$$

**b) In star**

$$\begin{aligned}I_L &= I_P \\&= \mathbf{25 \text{ amperes}}\end{aligned}$$

## Delta connection

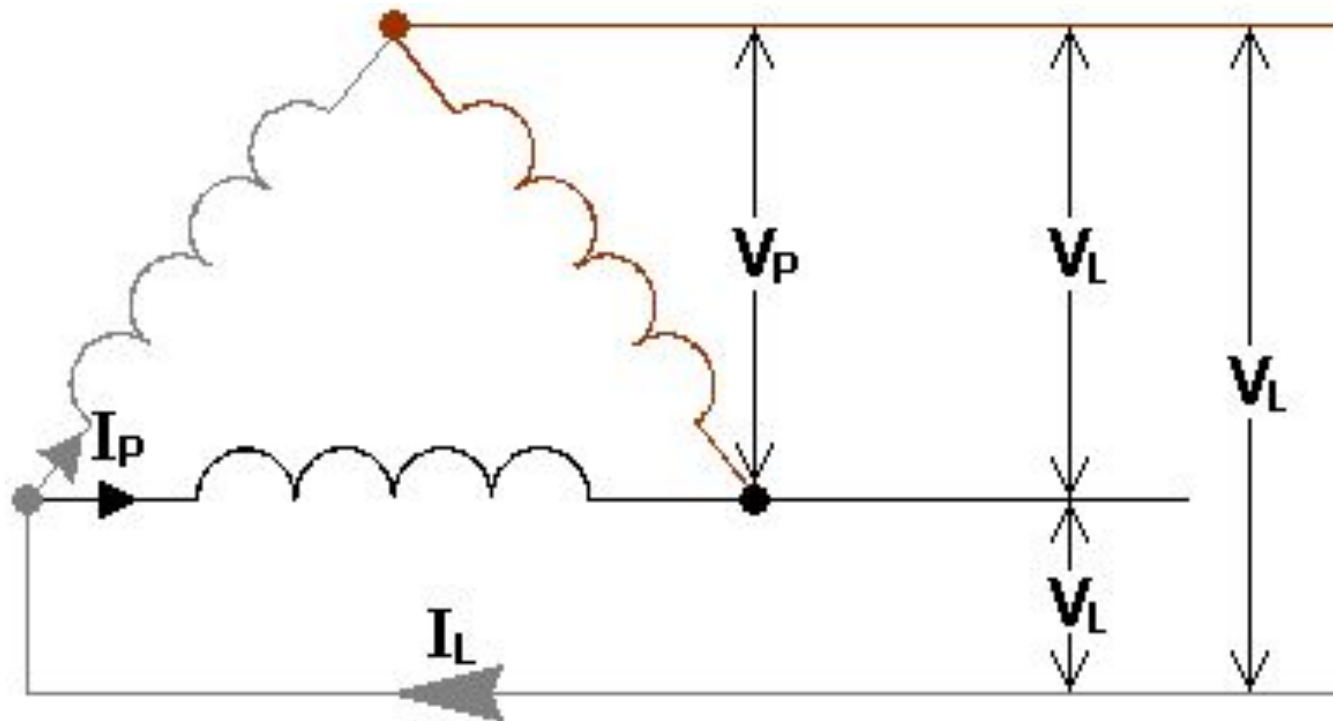

$$V_L = V_P$$

$$I_L = \sqrt{3} \times I_P$$

**EXAMPLE 2** – A three-phase balanced Delta connected resistive load is supplied from a transformer at a line voltage of 400 volts and draws a line current of 13.86 amps. Calculate:

- a) the phase voltage
- b) the phase current
- c) the resistance of the load.

**a) In delta**

$$V_P = V_L$$
$$= 400 \text{ volts}$$

**b) In delta**

$$I_L = \sqrt{3} \times I_P$$
$$I_P = \frac{I_L}{\sqrt{3}}$$
$$= \frac{13.86}{\sqrt{3}}$$
$$= 8 \text{ amperes}$$


**EXAMPLE 2** – A three-phase balanced Delta connected resistive load is supplied from a transformer at a line voltage of 400 volts and draws a line current of 13.86 amps. Calculate:

- a) the phase voltage
- b) the phase current
- c) the resistance of the load.

**c)**

$$\begin{aligned} R &= \frac{V_P}{I_P} \\ &= \frac{400}{8} \\ &= \mathbf{50 \, \Omega} \end{aligned}$$

## Balancing loads

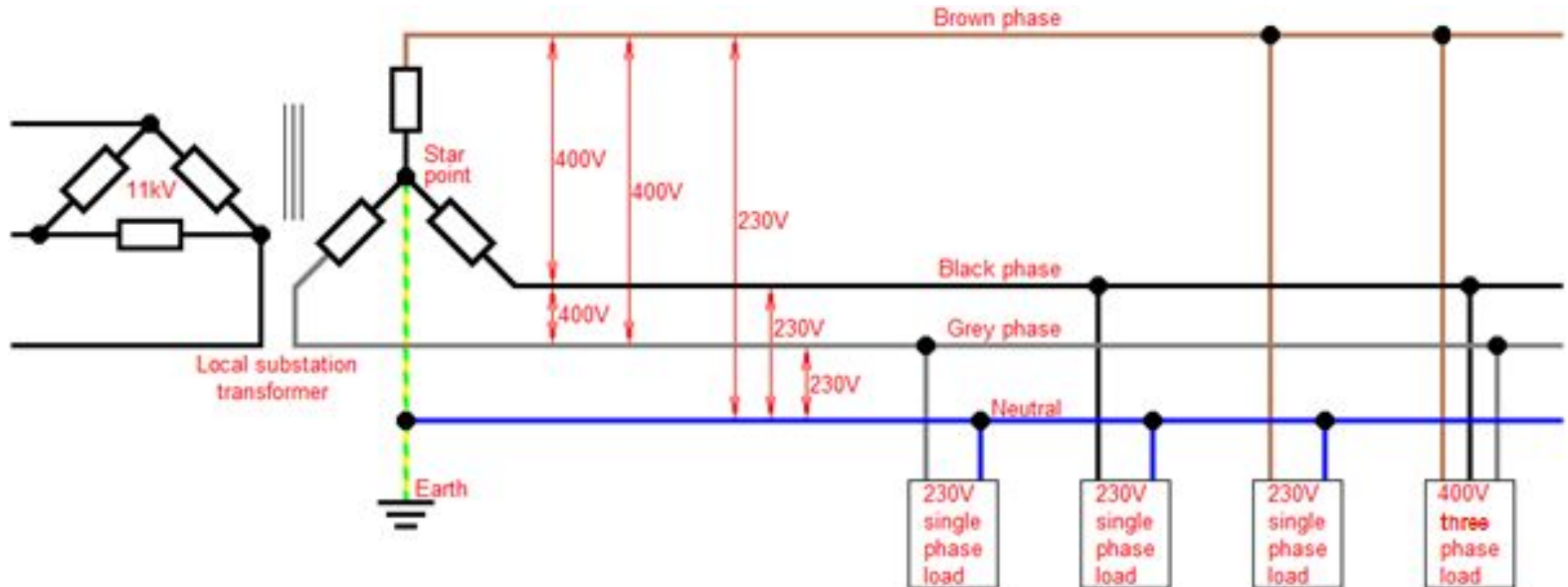




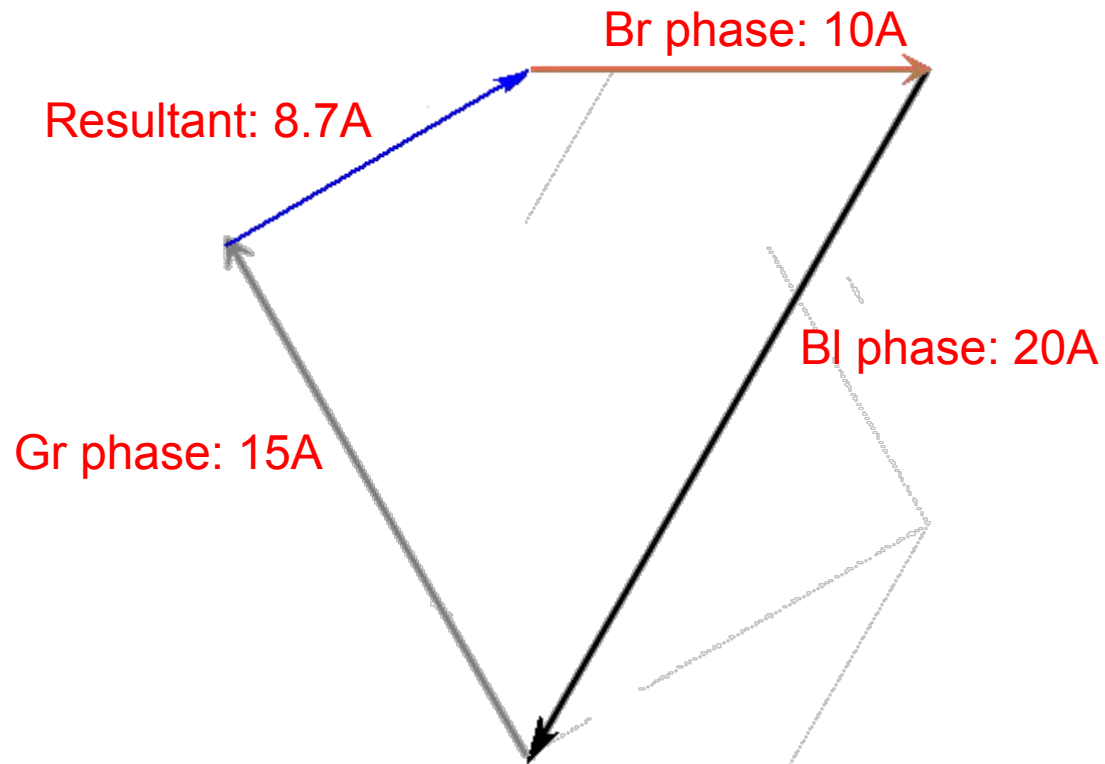**EXAMPLE 3** – A three-phase unbalanced star connected system has the following loads connected to each phase:

- Brown phase – 10 amperes
- Black phase – 20 amperes
- Grey phase – 15 amperes

Using the graphical method (phasors) determine the neutral current.



$$I_n = \sqrt{((I_a^2 + I_b^2 + I_c^2) - (I_a \times I_b) - (I_b \times I_c) - (I_a \times I_c))}$$

Where:  $I_n$  = neutral current

Where:  $I_a$  = current in brown phase

Where:  $I_b$  = current in black phase

Where:  $I_c$  = current in grey phase

**EXAMPLE 4** – Using the figures in Example 3, calculate the neutral current.

$$\begin{aligned} I_n &= \sqrt{((I_a^2 + I_b^2 + I_c^2) - (I_a \times I_b) - (I_b \times I_c) - (I_a \times I_c))} \\ &= \sqrt{((10^2 + 20^2 + 15^2) - (10 \times 20) - (20 \times 15) - (10 \times 15))} \\ &= \sqrt{(725 - 200 - 300 - 150)} \\ &= \sqrt{75} \\ &= \mathbf{8.66 \text{ amperes}} \end{aligned}$$

# Any questions?