

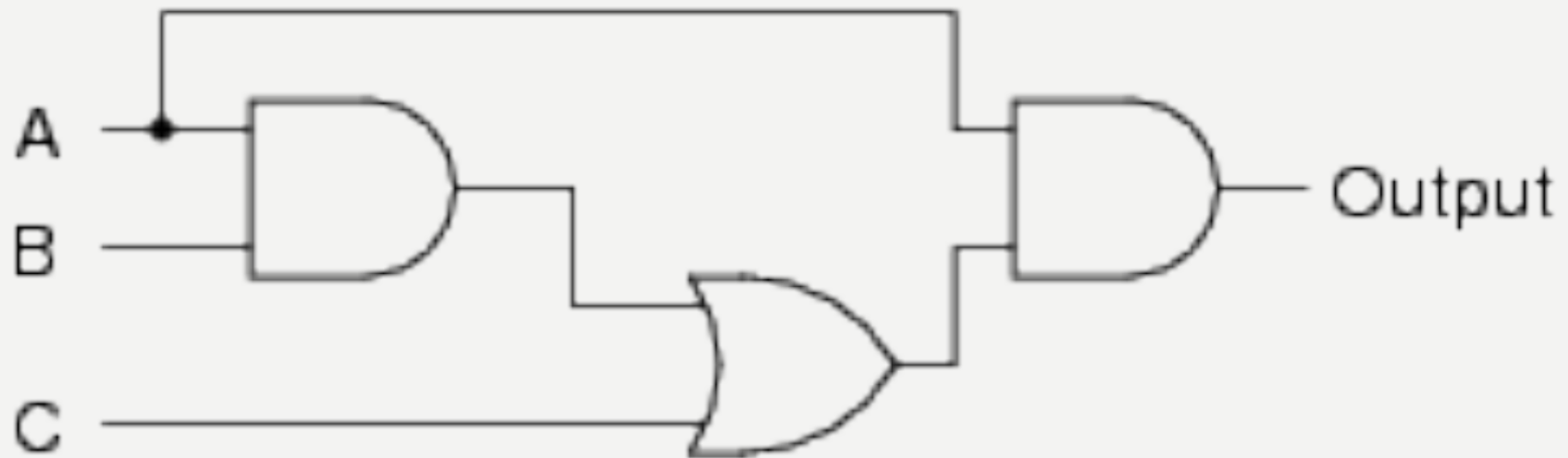


$$[(A*B)+C]*A$$

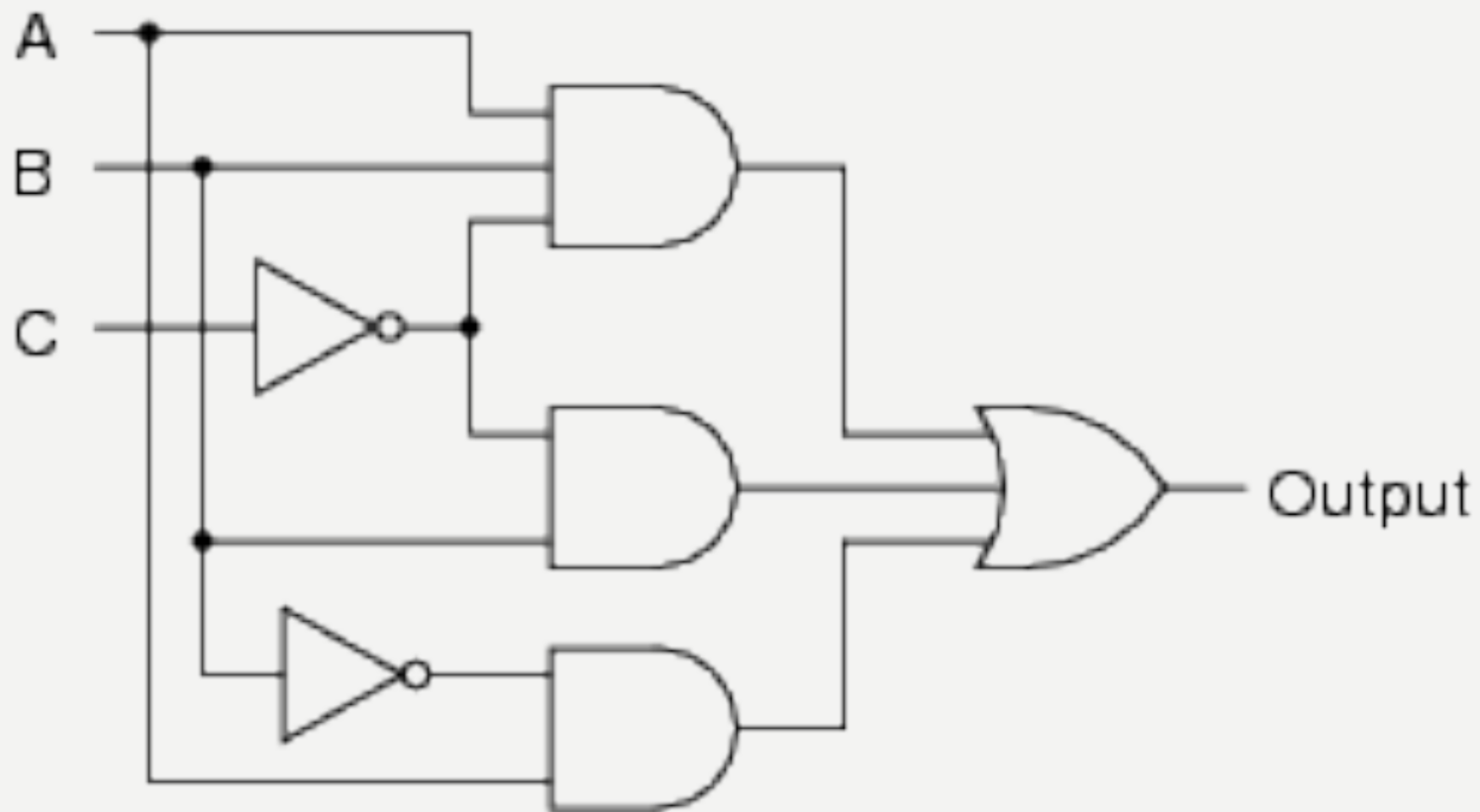


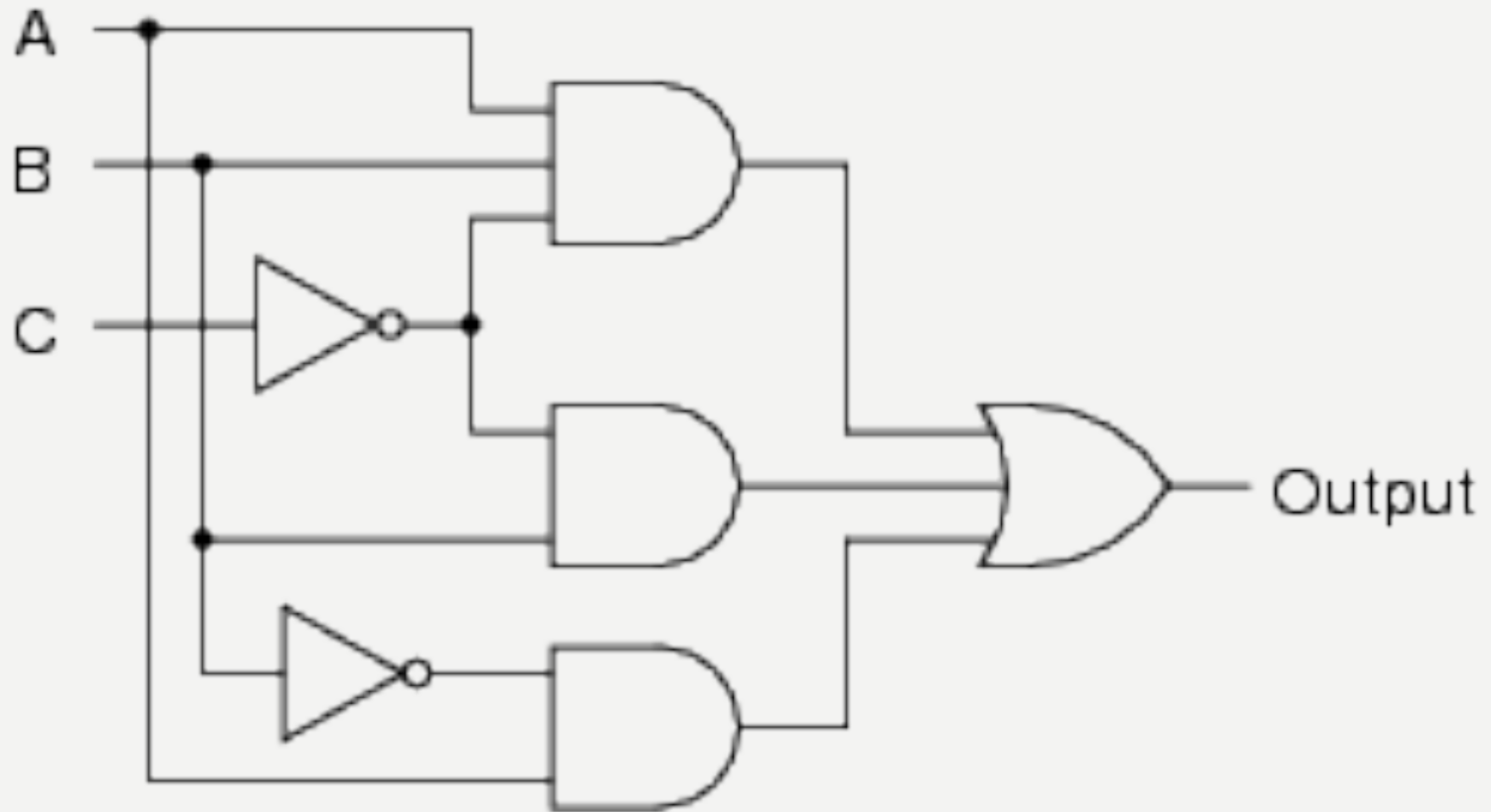


$$[A*B] + [C'*B] + [A*B']$$



LOGIC DIAGRAM

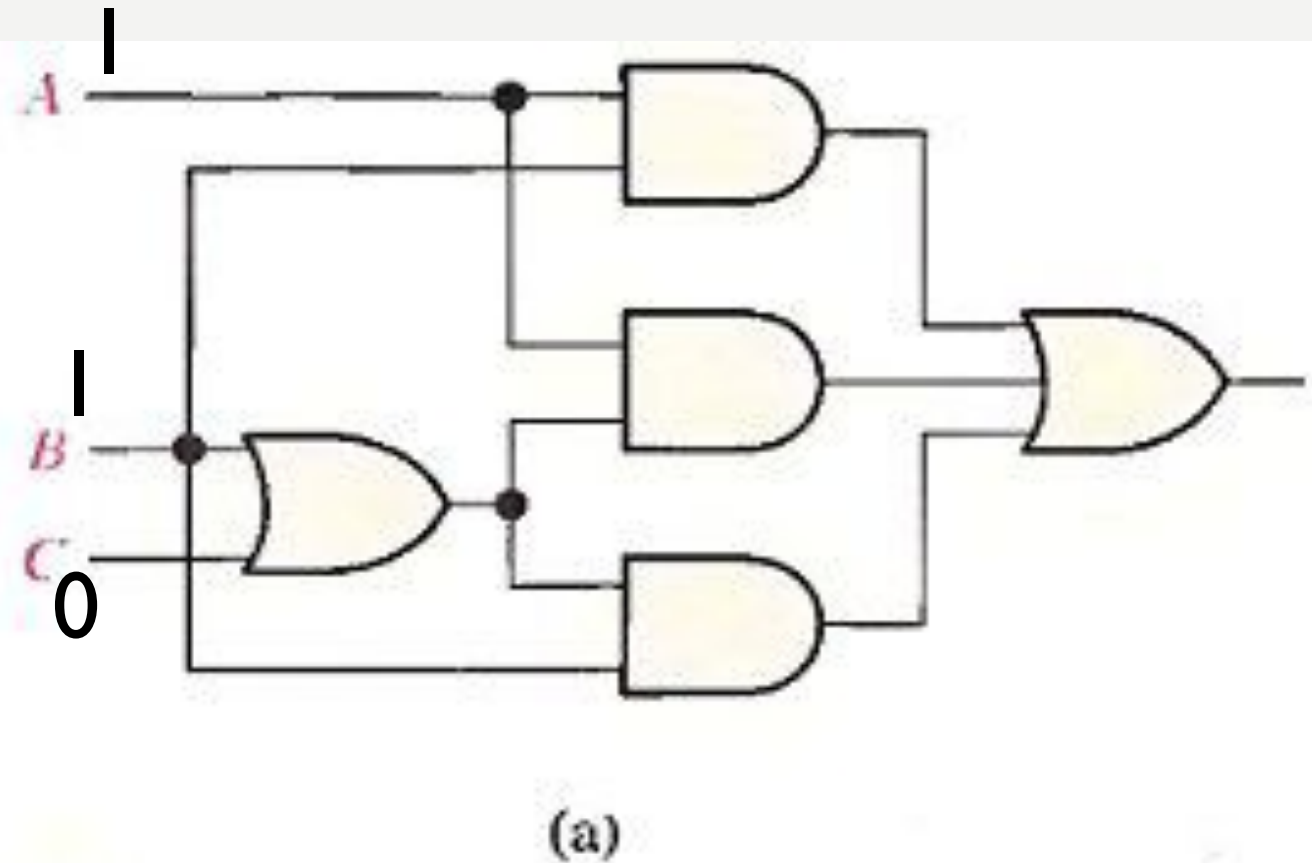

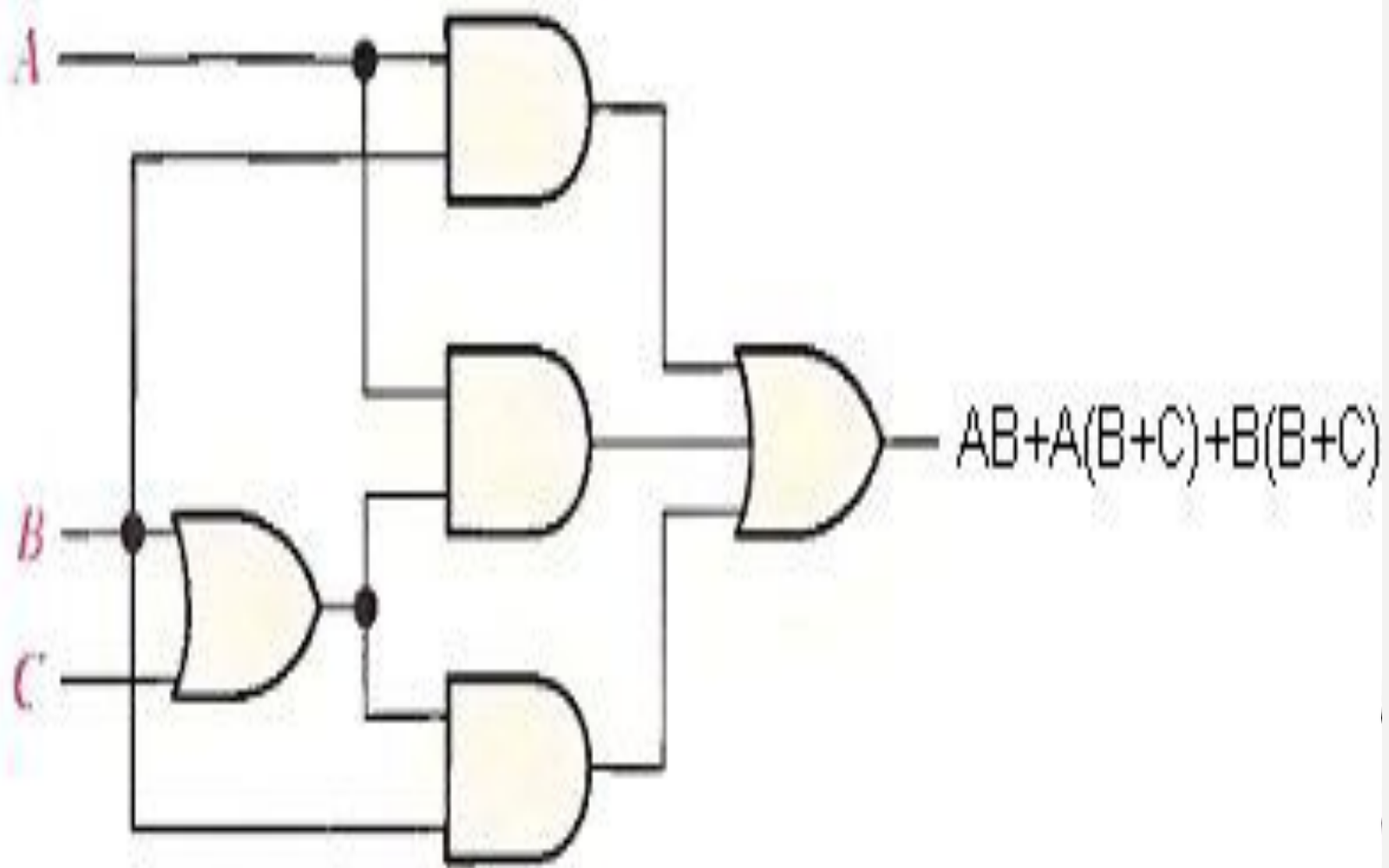

(a)

PROBLEM 1

- A system used 3 switches A,B and C; a combination of switches determines whether an alarm, X, sounds:
- If switch A or Switch B are in the ON position and if switch C is in the OFF position then a signal to sound an alarm, X is produced.

Convert this problem into a logic statement.

1) solve logistics problems at an elementary level

**2) SIMPLIFY A LOGIC
CIRCUIT/EXPRESSION USING
BOOLEAN ALGEBRA**

Table 4-1 Basic rules of Boolean algebra.

1. $A + 0 = A$

2. $A + 1 = 1$

3. $A \cdot 0 = 0$

4. $A \cdot 1 = A$

5. $A + A = A$

6. $A + \bar{A} = 1$

7. $A \cdot A = A$

8. $A \cdot \bar{A} = 0$

9. $\bar{\bar{A}} = A$

10. $A + AB = A$

11. $A + \bar{A}B = A + B$

12. $(A + B)(A + C) = A + BC$

A , B , or C can represent a single variable or a combination of variables.

COMMUTATIVE LAWS

- $A + B = B + A$

ASSOCIATIVE LAWS :

- $A + (B + C) = (A + B) + C$

DISTRIBUTIVE LAW:

- $A(B + C) = AB + AC$

DEMORGAN'S THEOREMS

- $\overline{X} + \overline{Y} = \overline{XY}$

EXAMPLE

Apply DeMorgan's theorems to the expressions \overline{XYZ} and $\overline{X + Y + z}$.

$$\overline{XYZ} = \overline{X} + \overline{Y} + \overline{Z}$$

$$\overline{X + y + Z} = \overline{X} \overline{Y} \overline{Z}$$

Example

Apply DeMorgan's theorems to the expressions \overline{WXYZ} and $\overline{W + X + y + z}$.

$$\overline{WXYZ} = \overline{W} + \overline{X} + \overline{y} + \overline{Z}$$

$$\overline{W + X + y + Z} = \overline{W} \overline{X} \overline{Y} \overline{Z}$$

- Using Boolean algebra techniques, simplify this expression:

- $AB + A(B + C) + B(B + C)$

- $X = A.B.C + A'.C$

- $Y = (Q + R)(Q' + R')$

- $W = A.B.C + A.B'.C + A'$

- $X = A.B.C + A'.C$

- $Y = (Q + R)(Q' + R')$

- $W = A.B.C + A.B'.C + A'$

- $Y = (Q + R)(Q' + R')$

- Answer :

- $= Q.Q' + Q.R' + Q'.R + R.R'$

- $= Q.R' + Q'.R$

- $W = A.B.C + A.B'.C + A'$

- Answer :

- $= A.C (B+B') + A'$

- $= A.C + A'$