

The Verilog Language

**These slides were developed by
Prof. Stephen A. Edwards
CS dept., Columbia University**

these slides are used for
educational purposes only

The Verilog Language

- Originally a modeling language for a very efficient event-driven digital logic simulator
- Later pushed into use as a specification language for logic synthesis
- Now, one of the two most commonly-used languages in digital hardware design (VHDL is the other)
- Virtually every chip (FPGA, ASIC, etc.) is designed in part using one of these two languages
- Combines structural and behavioral modeling styles

Structural Modeling

- When Verilog was first developed (1984) most logic simulators operated on netlists
- Netlist: list of gates and how they're connected
- A natural representation of a digital logic circuit
- Not the most convenient way to express test benches

Behavioral Modeling

- A much easier way to write testbenches
- Also good for more abstract models of circuits
 - Easier to write
 - Simulates faster
- More flexible
- Provides sequencing
- Verilog succeeded in part because it allowed both the model and the testbench to be described together

How Verilog Is Used

- **Virtually every ASIC is designed using either Verilog or VHDL (a similar language)**
- **Behavioral modeling with some structural elements**
- **“Synthesis subset”**
 - **Can be translated using Synopsys’ Design Compiler or others into a netlist**
- **Design written in Verilog**
- **Simulated to death to check functionality**
- **Synthesized (netlist generated)**
- **Static timing analysis to check timing**

Two Main Components of Verilog

- **Concurrent, event-triggered processes (behavioral)**
 - *Initial* and *Always* blocks
 - Imperative code that can perform standard data manipulation tasks (assignment, if-then, case)
 - Processes run until they delay for a period of time or wait for a triggering event
- **Structure (Plumbing)**
 - Verilog program build from modules with I/O interfaces
 - Modules may contain instances of other modules
 - Modules contain local signals, etc.
 - Module configuration is static and all run concurrently

Two Main Data Types

- **Nets represent connections between things**
 - Do not hold their value
 - Take their value from a driver such as a gate or other module
 - Cannot be assigned in an *initial* or *always* block
- **Regs represent data storage**
 - Behave exactly like memory in a computer
 - Hold their value until explicitly assigned in an *initial* or *always* block
 - Never connected to something
 - Can be used to model latches, flip-flops, etc., but do not correspond exactly
 - Shared variables with all their attendant problems

Discrete-event Simulation


- **Basic idea: only do work when something changes**
- **Centered around an event queue**
 - **Contains events labeled with the simulated time at which they are to be executed**
- **Basic simulation paradigm**
 - **Execute every event for the current simulated time**
 - **Doing this changes system state and may schedule events in the future**
 - **When there are no events left at the current time instance, advance simulated time soonest event in the queue**

Four-valued Data

- Verilog's nets and registers hold four-valued data
- 0, 1
 - Obvious
- Z
 - Output of an undriven tri-state driver
 - Models case where nothing is setting a wire's value
- X
 - Models when the simulator can't decide the value
 - Initial state of registers
 - When a wire is being driven to 0 and 1 simultaneously
 - Output of a gate with Z inputs

Four-valued Logic

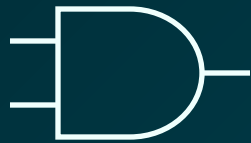- Logical operators work on three-valued logic



	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X

← Output 0 if one input is 0

← Output X if both inputs are gibberish

Structural Modeling

Nets and Registers

- Wires and registers can be bits, vectors, and arrays

```
wire a;           // Simple wire
tri [15:0] dbus;   // 16-bit tristate bus
tri #(5,4,8) b;    // Wire with delay
reg [-1:4] vec;    // Six-bit register
triereg (small) q; // Wire stores a small charge
integer imem[0:1023]; // Array of 1024 integers
reg [31:0] dcache[0:63]; // A 32-bit memory
```

Modules and Instances

- Basic structure of a Verilog module:

```
module mymod(output1, output2, ... input1, input2);  
output output1;  
output [3:0] output2;  
input input1;  
input [2:0] input2;  
...  
endmodule
```

Verilog convention
lists outputs first



Instantiating a Module

- Instances of

```
module mymod(y, a, b);
```

- look like

```
mymod mm1(y1, a1, b1);    // Connect-by-position
```

```
mymod (y2, a1, b1),
```

```
    (y3, a2, b2);          // Instance names omitted
```

```
mymod mm2(.a(a2), .b(b2), .y(c2)); // Connect-by-name
```

Gate-level Primitives

- Verilog provides the following:

and	nand	logical AND/NAND
or	nor	logical OR/NOR
xor	xnor	logical XOR/XNOR
buf	not	buffer/inverter
bufif0	notif0	Tristate with low enable
bifif1	notif1	Tristate with high enable

Delays on Primitive Instances

- Instances of primitives may include delays

```
buf      b1(a, b);    // Zero delay
buf #3    b2(c, d);    // Delay of 3
buf #(4,5) b3(e, f);    // Rise=4, fall=5
buf #(3:4:5) b4(g, h); // Min-typ-max
```


User-Defined Primitives

- Way to define gates and sequential elements using a truth table
- Often simulate faster than using expressions, collections of primitive gates, etc.
- Gives more control over behavior with X inputs
- Most often used for specifying custom gate libraries

A Carry Primitive

```
primitive carry(out, a, b, c);
```

```
output out;
```

```
input a, b, c;
```

```
table
```

```
  00? : 0;
```

```
  0?0 : 0;
```

```
  ?00 : 0;
```

```
  11? : 1;
```

```
  1?1 : 1;
```

```
  ?11 : 1;
```

```
endtable
```

```
endprimitive
```

Always have exactly
one output

Truth table may
include don't-care (?)
entries

A Sequential Primitive

```
Primitive dff( q, clk, data);
```

```
output q; reg q;
```

```
input clk, data;
```

```
table
```

```
// clk data q  new-q
```

```
(01)  0  : ? :  0;    // Latch a 0
```

```
(01)  1  : ? :  1;    // Latch a 1
```

```
(0x)  1  : 1 :  1;    // Hold when d and q both 1
```

```
(0x)  0  : 0 :  0;    // Hold when d and q both 0
```

```
(?0)  ?  : ? :  -;    // Hold when clk falls
```

```
?  (??) : ? :  -;    // Hold when clk stable
```

```
endtable
```

```
endprimitive
```

Continuous Assignment

- Another way to describe combinational function
- Convenient for logical or datapath specifications

```
wire [8:0] sum;  
wire [7:0] a, b;  
wire carryin;
```

Define bus widths



```
assign sum = a + b + carryin;
```

Continuous
assignment:
permanently sets the
value of sum to be
 $a+b+carryin$

Recomputed when a,
b, or carryin changes

Behavioral Modeling

Initial and Always Blocks

- Basic components for behavioral modeling

initial

begin

... imperative statements ...

end

Runs when simulation starts

**Terminates when control
reaches the end**

Good for providing stimulus

always

begin

... imperative statements ...

end

Runs when simulation starts

**Restarts when control reaches
the end**

**Good for modeling/specifying
hardware**

Initial and Always

- Run until they encounter a delay

initial begin

#10 a = 1; b = 0;

#10 a = 0; b = 1;

end

- or a wait for an event

always @(posedge clk) q = d;

always begin wait(i); a = 0; wait(~i); a = 1; end

Procedural Assignment

- Inside an initial or always block:

```
sum = a + b + cin;
```

- Just like in C: RHS evaluated and assigned to LHS before next statement executes
- RHS may contain wires and regs
 - Two possible sources for data
- LHS must be a reg
 - Primitives or cont. assignment may set wire values

Imperative Statements

```
if (select == 1)  y = a;  
else             y = b;
```

```
case (op)  
  2'b00: y = a + b;  
  2'b01: y = a - b;  
  2'b10: y = a ^ b;  
  default: y = 'hxxxx;  
endcase
```

For Loops

- A increasing sequence of values on an output

```
reg [3:0] i, output;
```

```
for ( i = 0 ; i <= 15 ; i = i + 1 ) begin
```

```
    output = i;
```

```
    #10;
```

```
end
```

While Loops

- A increasing sequence of values on an output

```
reg [3:0] i, output;
```

```
i = 0;
```

```
while (i <= 15) begin
```

```
    output = i;
```

```
    #10 i = i + 1;
```

```
end
```

Modeling A Flip-Flop With Always

- Very basic: an edge-sensitive flip-flop

```
reg q;
```

```
always @(posedge clk)
```

```
    q = d;
```

- **q = d assignment runs when clock rises: exactly the behavior you expect**

Blocking vs. Nonblocking

- Verilog has two types of procedural assignment
- Fundamental problem:
 - In a synchronous system, all flip-flops sample simultaneously
 - In Verilog, always @(posedge clk) blocks run in some undefined sequence

A Flawed Shift Register

- This doesn't work as you'd expect:

```
reg d1, d2, d3, d4;
```

```
always @(posedge clk) d2 = d1;
```

```
always @(posedge clk) d3 = d2;
```

```
always @(posedge clk) d4 = d3;
```

- These run in some order, but you don't know which

Non-blocking Assignments

- This version does work:

```
reg d1, d2, d3, d4;
```


```
always @(posedge clk) d2 <= d1;
```

```
always @(posedge clk) d3 <= d2;
```


```
always @(posedge clk) d4 <= d3;
```

Nonblocking rule:

RHS evaluated when
assignment runs



LHS updated only after
all events for the current
instant have run



Nonblocking Can Behave Oddly

- A sequence of nonblocking assignments don't communicate

a = 1;

b = a;

c = b;

a <= 1;

b <= a;

c <= b;

Blocking assignment:

a = b = c = 1

Nonblocking assignment:

a = 1

b = old value of a

c = old value of b


Nonblocking Looks Like Latches

- RHS of nonblocking taken from latches
- RHS of blocking taken from wires

`a = 1;`
`b = a;`
`c = b;`



`a <= 1;`
`b <= a;`
`c <= b;`

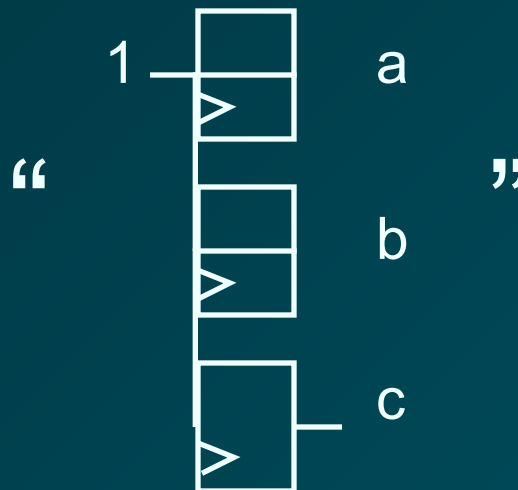

Building Behavioral Models

Modeling FSMs Behaviorally

- There are many ways to do it:
- Define the next-state logic combinationaly and define the state-holding latches explicitly
- Define the behavior in a single always @(posedge clk) block
- Variations on these themes

FSM with Combinational Logic

```
module FSM(o, a, b, reset);  
output o;  
reg o;  
input a, b, reset;  
reg [1:0] state, nextState;
```

```
always @(a or b or state)  
case (state)  
  2'b00: begin  
    nextState = a ? 2'b00 : 2'b01;  
    o = a & b;  
  end  
  2'b01: begin nextState = 2'b10; o = 0; end  
endcase
```

Output o is declared a reg because it is assigned procedurally, not because it holds state

Combinational block must be sensitive to any change on any of its inputs

(Implies state-holding elements otherwise)

FSM with Combinational Logic

```
module FSM(o, a, b, reset);
```

```
...
```

```
always @(posedge clk or reset)
```

```
  if (reset)
```

```
    state <= 2'b00;
```

```
  else
```

```
    state <= nextState;
```



Latch implied by
sensitivity to the clock
or reset only

FSM from Combinational Logic

```
always @(a or b or state)
case (state)
  2'b00: begin
    nextState = a ? 2'b00 : 2'b01;
    o = a & b;
  end
  2'b01: begin nextState = 2'b10; o = 0; end
endcase
```

This is a Mealy machine because the output is directly affected by any change on the input

```
always @(posedge clk or reset)
if (reset)
  state <= 2'b00;
else
  state <= nextState;
```

FSM from a Single Always Block

```
module FSM(o, a, b);  
output o; reg o;  
input a, b;  
reg [1:0] state;
```

```
always @(posedge clk or reset)  
if (reset) state <= 2'b00;  
else case (state)  
2'b00: begin  
state <= a ? 2'b00 : 2'b01;  
o <= a & b;  
end  
2'b01: begin state <= 2'b10; o <= 0; end  
endcase
```

Expresses Moore machine behavior:

Outputs are latched

Inputs only sampled at clock edges


Nonblocking assignments used throughout to ensure coherency.

RHS refers to values calculated in previous clock cycle

Simulating Verilog

How Are Simulators Used?

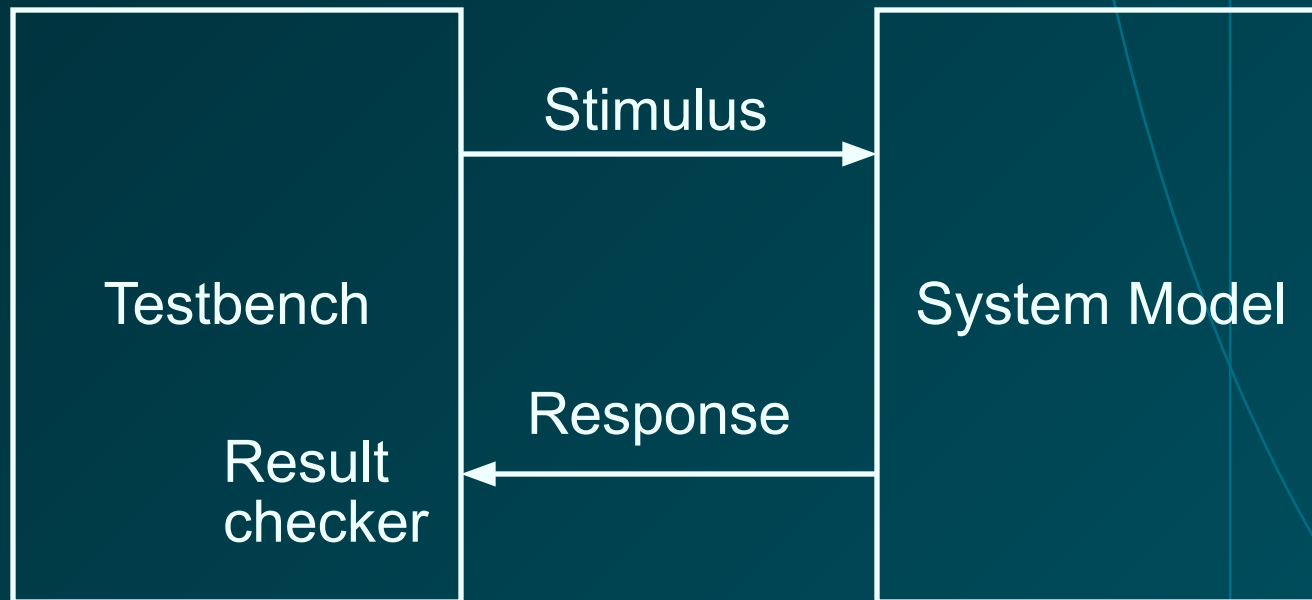
- Testbench generates stimulus and checks response
- Coupled to model of the system
- Pair is run simultaneously



Writing Testbenches

```
module test;  
reg a, b, sel;
```

Inputs to device
under test



```
mux m(y, a, b, sel);
```

Device under test



```
initial begin
```

\$monitor is a built-in
event driven “printf”



```
$monitor($time,, “a = %b b=%b sel=%b y=%b”,  
          a, b, sel, y);
```

```
a = 0; b= 0; sel = 0;
```


```
#10 a = 1;
```

```
#10 sel = 1;
```

```
#10 b = 1;
```

```
end
```

Stimulus generated by
sequence of
assignments and delays



Simulation Behavior

- Scheduled using an event queue
- Non-preemptive, no priorities
- A process must explicitly request a context switch
- Events at a particular time unordered
- Scheduler runs each event at the current time, possibly scheduling more as a result

Two Types of Events

- Evaluation events compute functions of inputs
- Update events change outputs
- Split necessary for delays, nonblocking assignments, etc.

Update event
writes new value
of a and
schedules any
evaluation events
that are sensitive
to a change on a

$$a \leq b + c$$

Evaluation event
reads values of b and
c, adds them, and
schedules an update
event

Simulation Behavior

- Concurrent processes (initial, always) run until they stop at one of the following
 - #42
 - Schedule process to resume 42 time units from now
 - wait(cf & of)
 - Resume when expression “cf & of” becomes true
 - @(a or b or y)
 - Resume when a, b, or y changes
 - @(posedge clk)
 - Resume when clk changes from 0 to 1

Simulation Behavior

- Infinite loops are possible and the simulator does not check for them
- This runs forever: no context switch allowed, so ready can never change

```
while (~ready)  
    count = count + 1;
```

- Instead, use

```
wait(ready);
```

Simulation Behavior

- Race conditions abound in Verilog
- These can execute in either order: final value of a undefined:

```
always @(posedge clk) a = 0;
```

```
always @(posedge clk) a = 1;
```

Simulation Behavior

- **Semantics of the language closely tied to simulator implementation**
- **Context switching behavior convenient for simulation, not always best way to model**
- **Undefined execution order convenient for implementing event queue**

Verilog and Logic Synthesis

Logic Synthesis

- Verilog is used in two ways
 - Model for discrete-event simulation
 - Specification for a logic synthesis system
- Logic synthesis converts a subset of the Verilog language into an efficient netlist
- One of the major breakthroughs in designing logic chips in the last 20 years
- Most chips are designed using at least some logic synthesis

Logic Synthesis

- Takes place in two stages:
- Translation of Verilog (or VHDL) source to a netlist
 - Register inference
- Optimization of the resulting netlist to improve speed and area
 - Most critical part of the process
 - Algorithms very complicated and beyond the scope of this class: Take Prof. Nowick's class for details

Translating Verilog into Gates

- **Parts of the language easy to translate**
 - **Structural descriptions with primitives**
 - Already a netlist
 - **Continuous assignment**
 - Expressions turn into little datapaths
- **Behavioral statements the bigger challenge**

What Can Be Translated

- **Structural definitions**
 - Everything
- **Behavioral blocks**
 - Depends on sensitivity list
 - Only when they have reasonable interpretation as combinational logic, edge, or level-sensitive latches
 - Blocks sensitive to both edges of the clock, changes on unrelated signals, changing sensitivity lists, etc. cannot be synthesized
- **User-defined primitives**
 - Primitives defined with truth tables
 - Some sequential UDPs can't be translated (not latches or flip-flops)

What Isn't Translated

- **Initial blocks**
 - Used to set up initial state or describe finite testbench stimuli
 - Don't have obvious hardware component
- **Delays**
 - May be in the Verilog source, but are simply ignored
- **A variety of other obscure language features**
 - In general, things heavily dependent on discrete-event simulation semantics
 - Certain “disable” statements
 - Pure events

Register Inference


- The main trick
- reg does not always equal latch
- Rule: Combinational if outputs always depend exclusively on sensitivity list
- Sequential if outputs may also depend on previous values

Register Inference

- Combinational:

```
reg y;  
always @(a or b or sel)  
  if (sel) y = a;  
  else y = b;
```

Sensitive to changes
on all of the variables
it reads



Y is always assigned



- Sequential:

```
reg q;  
always @(d or clk)  
  if (clk) q = d;
```

q only assigned when
clk is 1



Register Inference

- A common mistake is not completely specifying a case statement
- This implies a latch:

```
always @(a or b)
```

```
case ({a, b})
```


```
  2'b00 : f = 0;
```

```
  2'b01 : f = 1;
```

```
  2'b10 : f = 1;
```

```
endcase
```

f is not assigned
when {a,b} = 2b'11

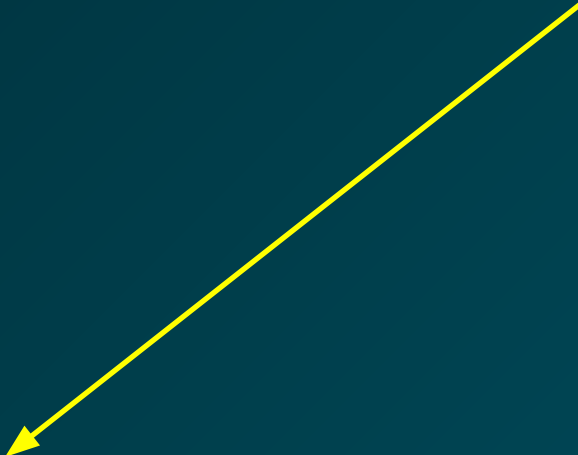

Register Inference

- The solution is to always have a default case

always @(a or b)

case ({a, b})

2'b00: f = 0;

2'b01: f = 1;

2'b10: f = 1;

default: f = 0;

endcase

f is always assigned



Inferring Latches with Reset

- Latches and Flip-flops often have reset inputs
- Can be synchronous or asynchronous
- Asynchronous positive reset:

```
always @(posedge clk or posedge reset)
  if (reset)
    q <= 0;
  else q <= d;
```

Simulation-synthesis Mismatches

- Many possible sources of conflict
- Synthesis ignores delays (e.g., #10), but simulation behavior can be affected by them
- Simulator models X explicitly, synthesis doesn't
- Behaviors resulting from shared-variable-like behavior of regs is not synthesized
 - always @(posedge clk) a = 1;
 - New value of a may be seen by other @(posedge clk) statements in simulation, never in synthesis

Compared to VHDL

- Verilog and VHDL are comparable languages
- VHDL has a slightly wider scope
 - System-level modeling
 - Exposes even more discrete-event machinery
- VHDL is better-behaved
 - Fewer sources of nondeterminism (e.g., no shared variables)
- VHDL is harder to simulate quickly
- VHDL has fewer built-in facilities for hardware modeling
- VHDL is a much more verbose language
 - Most examples don't fit on slides