

Chapter 7

Virtex Arithmetic Structures

Overview

- Addition and subtraction
- Multiplication
- DSP48
- DSP48E


Basic Adder Equations

$$S_i = A_i \text{ XOR } B_i \text{ XOR } C_i$$

$$C_{i+1} = A_i B_i + (A_i \text{ XOR } B_i) C_i$$

Note: not unique expression for C_{i+1}

Basic Ripple Adder

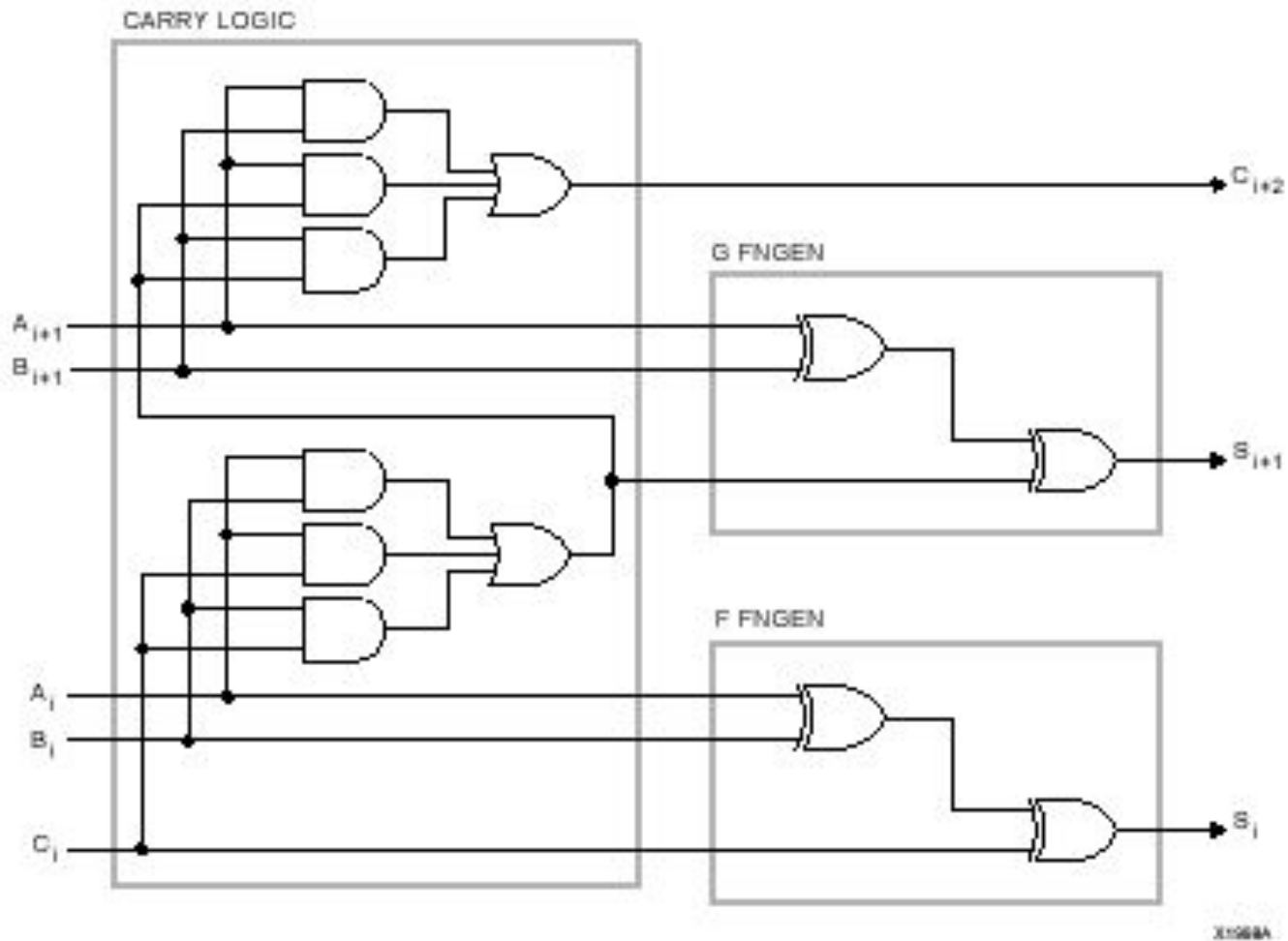


Fast Carry Chains


A	B	C	C _{OUT}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$A = B, C_{OUT} = A$
 $A \neq B, C_{OUT} = C_{IN}$
 $A = B, C_{OUT} = A$


XC002A

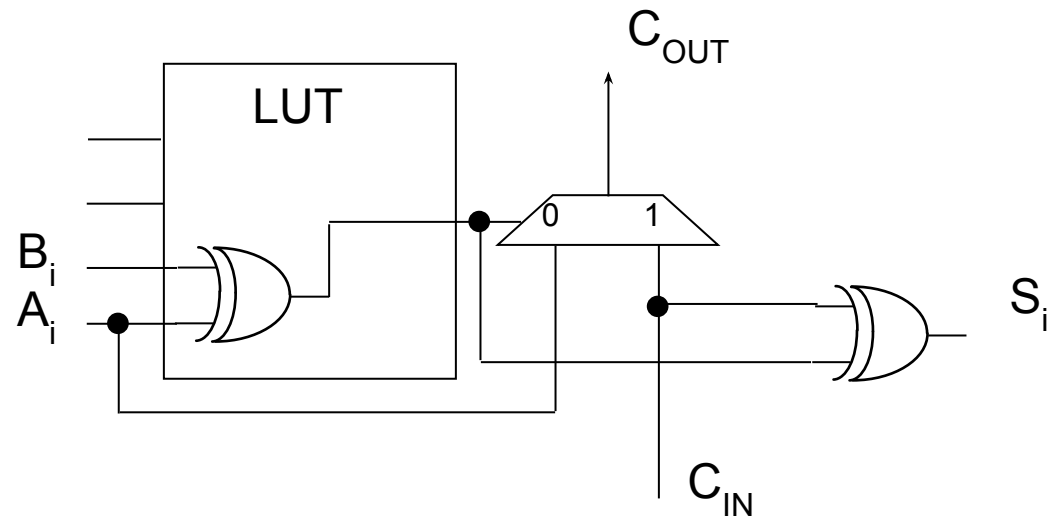

Tracing Carry Chain

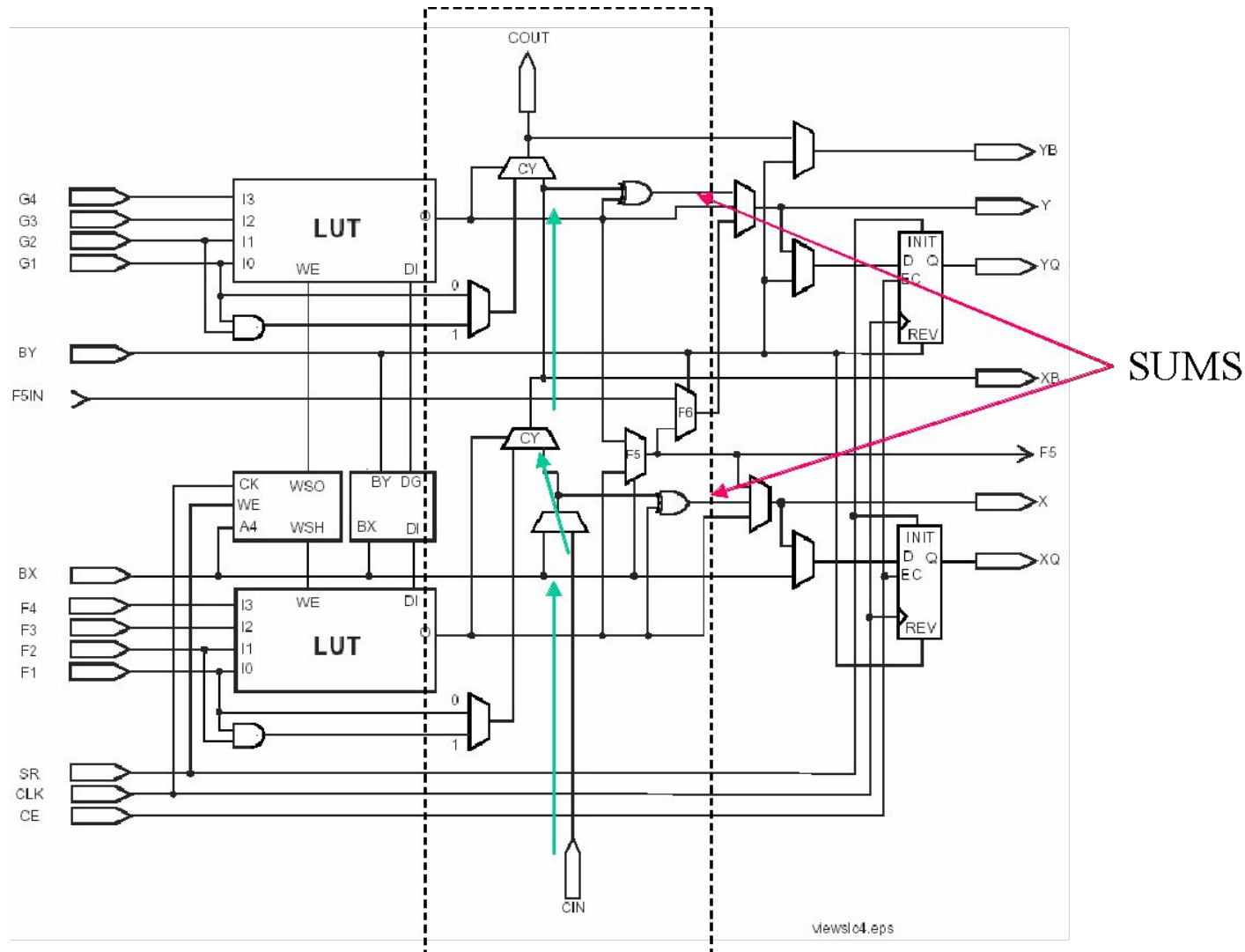

Counters Built from Adders

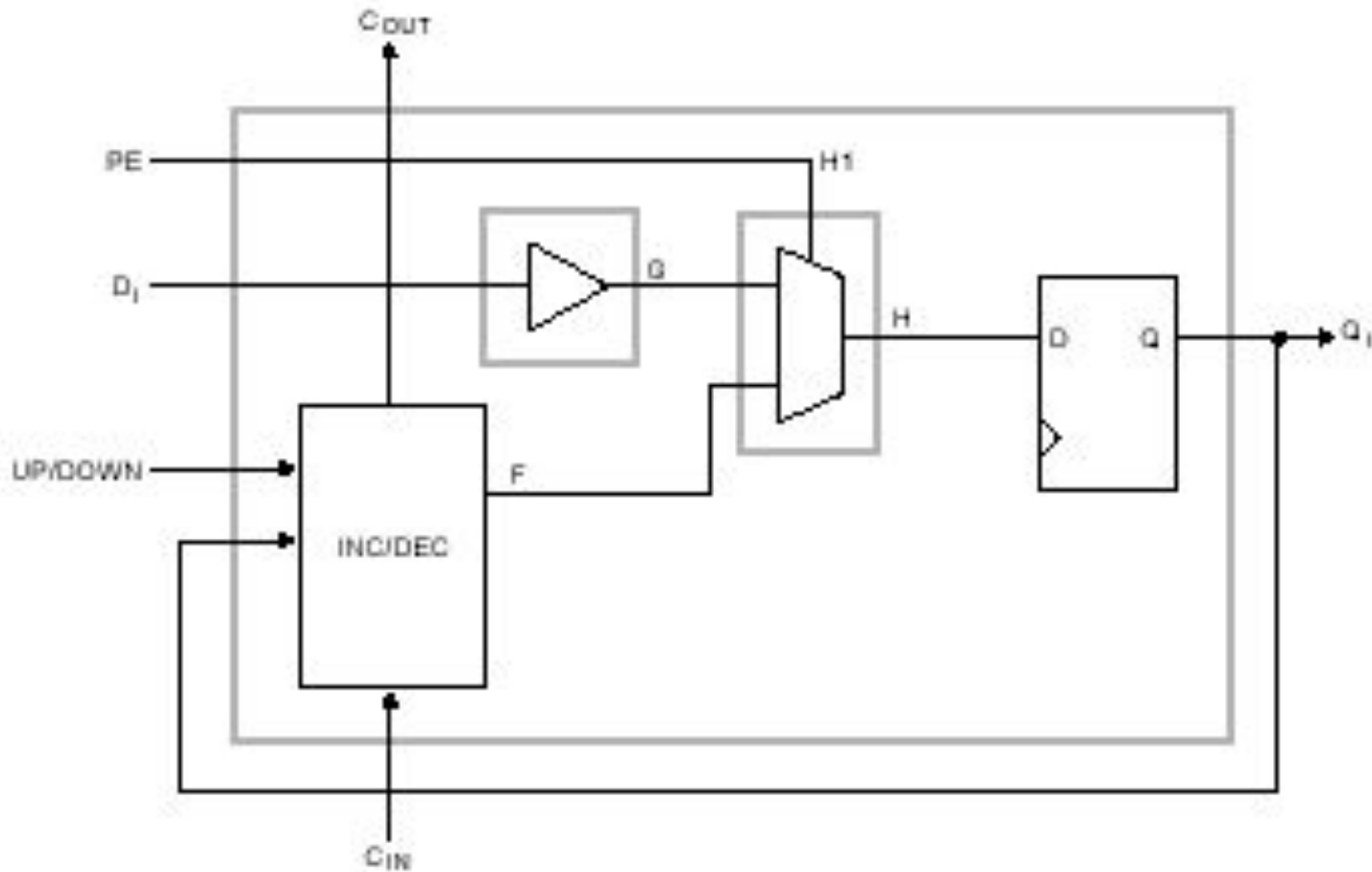

Multiplication Review

$$\begin{array}{rcccccc}
 & & & & A_3 & A_2 & A_1 & A_0 \\
 & & & & X & & B_1 & B_0 \\
 \hline
 & & & A_3 B_0 & A_2 B_0 & A_1 B_0 & A_0 B_0 \\
 A_3 B_1 & & A_2 B_1 & A_1 B_1 & A_0 B_1 & & & \\
 \hline
 P_5 & P_4 & P_3 & P_2 & P_1 & P_0
 \end{array}$$

Just like in the third grade . . .

Fabric Based Multiplier

(comment: should be C_{OUT})


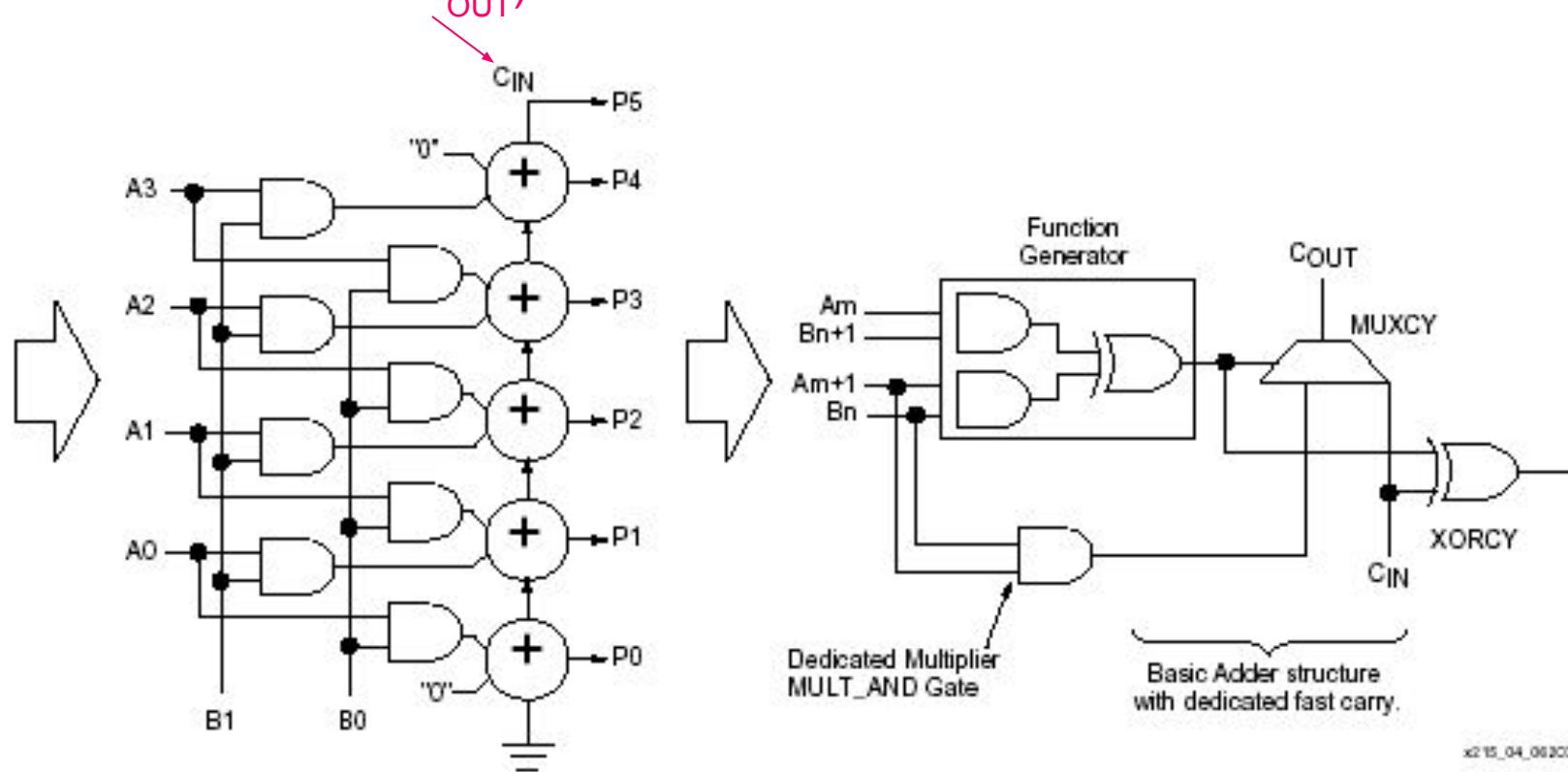


Figure 5: N x 2 Full Multiplier Implementation

Mult/AND Identification

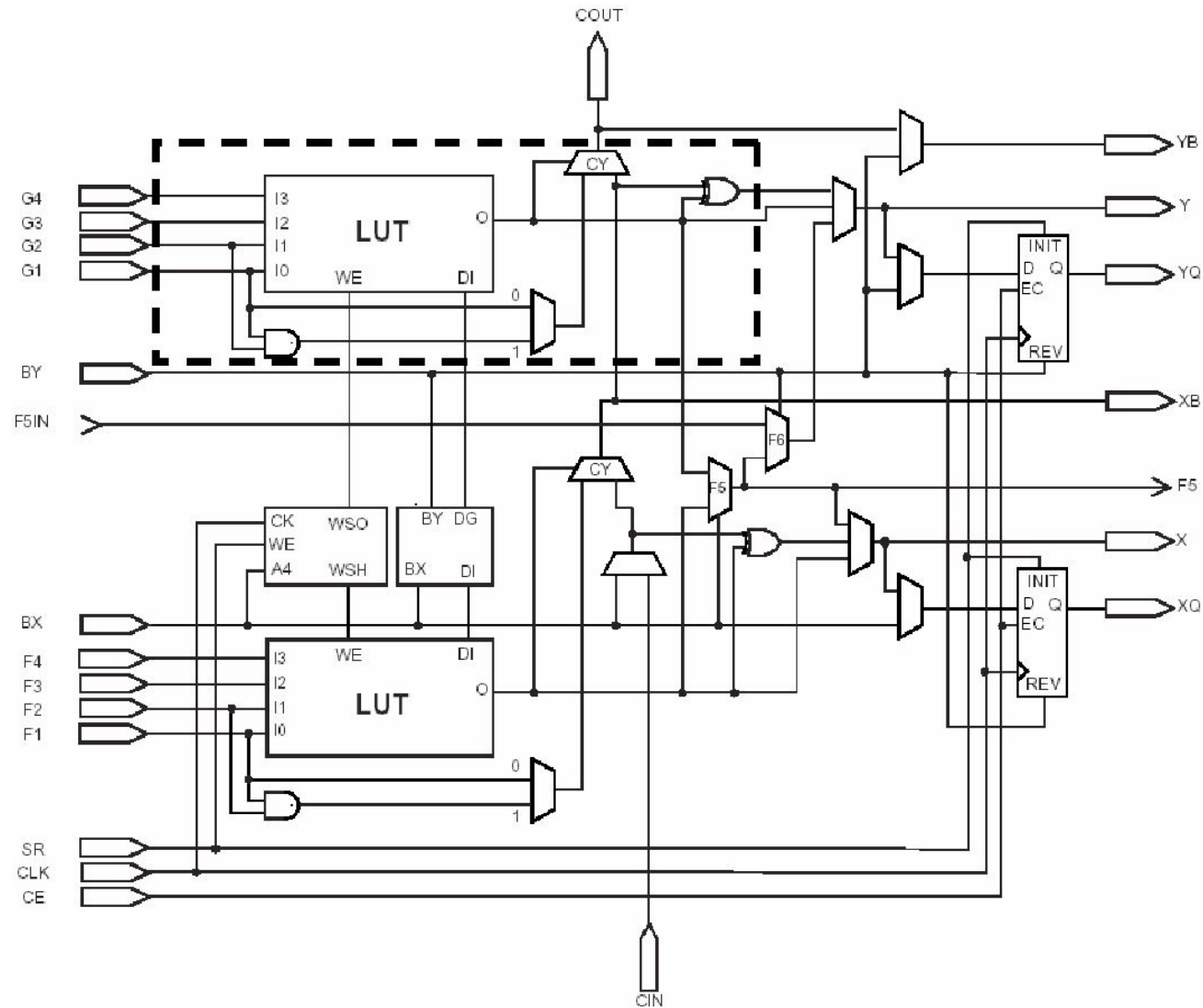


Block Multipliers

- Xilinx Spartan 3/E and Virtex II = 18 bit
- Applications needing fewer bits can tie off higher order bits appropriately
- Applications needing more bits must either:
 - Cascade block multipliers
 - Combine blocks with fabric multipliers
- Other uses for block multipliers

Virtex II/Spartan 3/E Block Multipliers

Primitive	A Width	B Width	P Width	Signed/Unsigned	Output
MULT18X18	18	18	36	Signed (Two's Complement)	Combinatorial
MULT18X18S	18	18	36	Signed (Two's Complement)	Registered

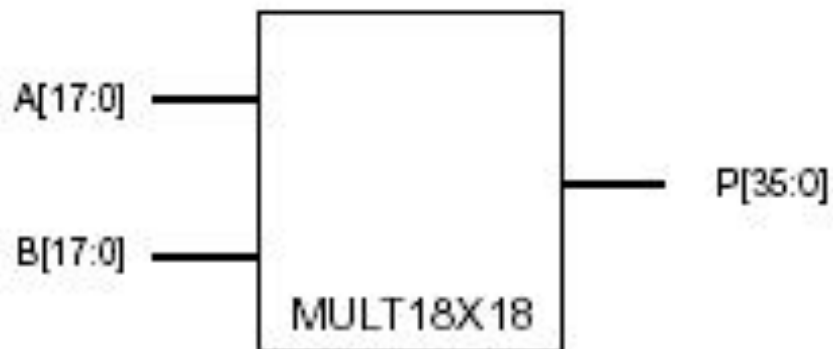

Combinational 2's Complement




Sequential 2's Complement

Spartan 3 Multiplier Mix

Device	Multiplier Columns	Multipliers
XC3S50	1	4
XC3S200	2	12
XC3S400	2	16
XC3S1000	2	24
XC3S1500	2	32
XC3S2000	2	40
XC3S4000	4	96
XC3S5000	4	104

With this many multipliers, better be something we can do with them if we Don't need this many. Also, must be other sizes we can create – somehow.
See **XAPP 467**

22 X 16 Bit Multiplier

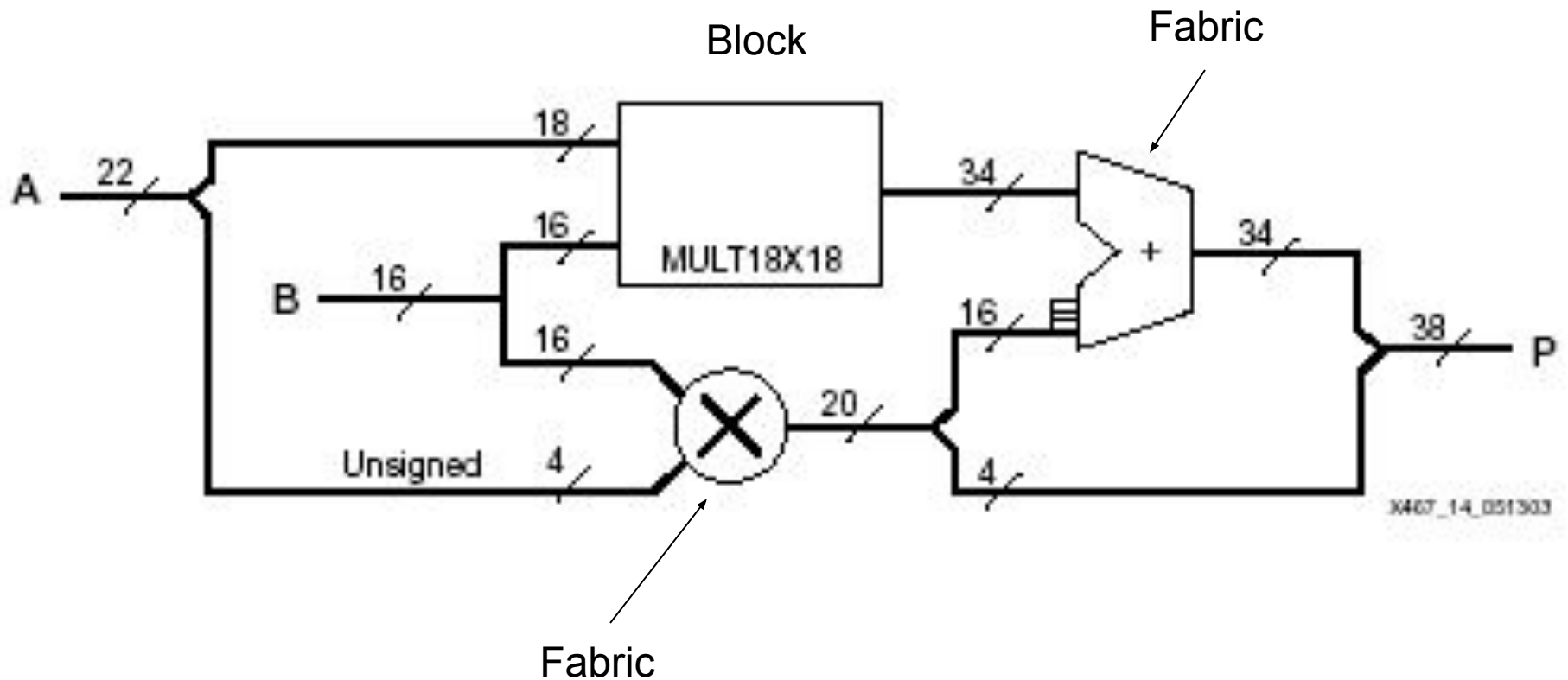


Other Uses

- Multiply several small numbers with one block multiplier
- Division by repeated multiplication
- Barrel shift using multiplier
- Take two's complement of a number
- Get the magnitude of a two's complement number
- There are others


DSP 48

- Introduced for Virtex 4
- Designed to efficiently cascade
- Xilinx teamed with outside arithmetic specialists to get best speed/area blocks
- Supports multiple rounding formats
- Not present in all V4 families

Two Slice DSP 48

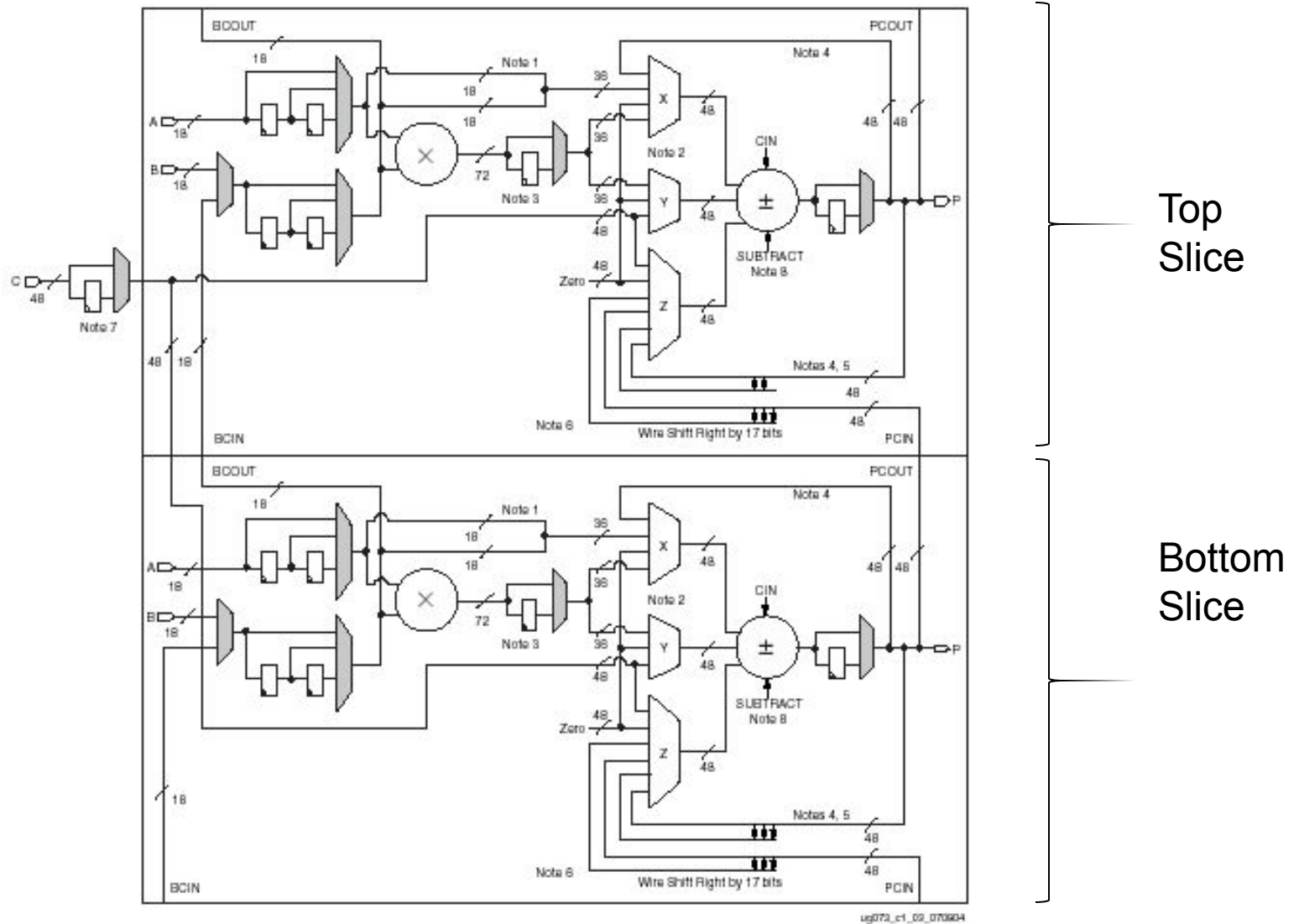

Simplified DSP 48

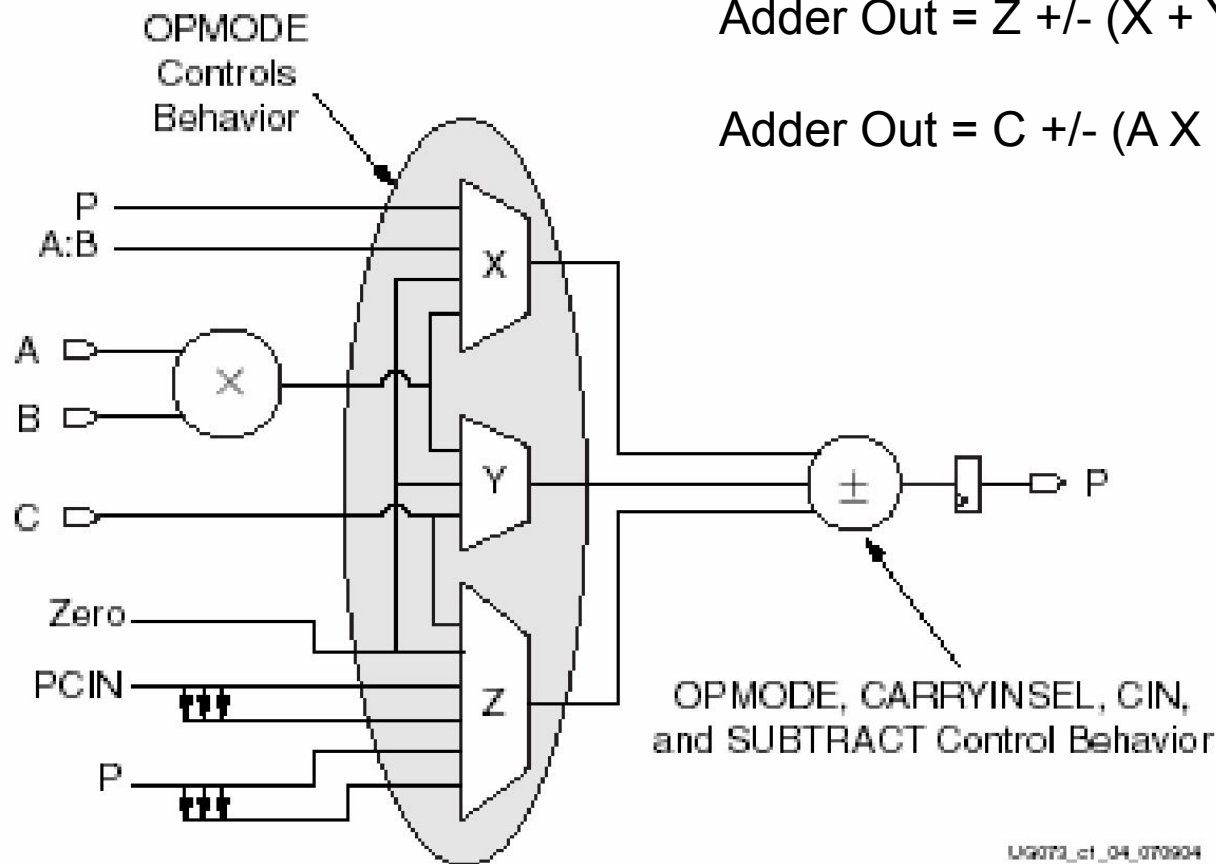


$$\text{Adder Out} = Z \pm (X + Y + \text{CIN})$$

$$\text{Adder Out} = C \pm (A \times B + \text{CIN})$$


Hex OPMODE	Binary OPMODE	XYZ Multiplexer Outputs and Adder/Subtractor Output			
[6:0]	Z Y X	Z	Y	X	Adder/Subtractor Output
0x00	000 00 00	0	0	0	$\pm \text{CIN}$
0x02	000 00 10	0	0	P	$\pm(P + \text{CIN})$
0x03	000 00 11	0	0	A:B	$\pm(A:B + \text{CIN})$
0x05	000 01 01	0	Note 1		$\pm(A \times B + \text{CIN})$
0x0c	000 11 00	0	C	0	$\pm(C + \text{CIN})$
0x0e	000 11 10	0	C	P	$\pm(C + P + \text{CIN})$
0x0f	000 11 11	0	C	A:B	$\pm(A:B + C + \text{CIN})$
0x10	001 00 00	PCIN	0	0	$\text{PCIN} \pm \text{CIN}$
0x12	001 00 10	PCIN	0	P	$\text{PCIN} \pm (P + \text{CIN})$
0x13	001 00 11	PCIN	0	A:B	$\text{PCIN} \pm (A:B + \text{CIN})$
0x15	001 01 01	PCIN	Note 1		$\text{PCIN} \pm (A \times B + \text{CIN})$
0x1c	001 11 00	PCIN	C	0	$\text{PCIN} \pm (C + \text{CIN})$
0x1e	001 11 10	PCIN	C	P	$\text{PCIN} \pm (C + P + \text{CIN})$
0x1f	001 11 11	PCIN	C	A:B	$\text{PCIN} \pm (A:B + C + \text{CIN})$
0x20	010 00 00	P	0	0	$P \pm \text{CIN}$
0x22	010 00 10	P	0	P	$P \pm (P + \text{CIN})$
0x23	010 00 11	P	0	A:B	$P \pm (A:B + \text{CIN})$
0x25	010 01 01	P	Note 1		$P \pm (A \times B + \text{CIN})$
0x2c	010 11 00	P	C	0	$P \pm (C + \text{CIN})$
0x2e	010 11 10	P	C	P	$P \pm (C + P + \text{CIN})$
0x2f	010 11 11	P	C	A:B	$P \pm (A:B + C + \text{CIN})$
0x30	011 00 00	C	0	0	$C \pm \text{CIN}$
0x32	011 00 10	C	0	P	$C \pm (P + \text{CIN})$
0x33	011 00 11	C	0	A:B	$C \pm (A:B + \text{CIN})$
0x35	011 01 01	C	Note 1		$C \pm (A \times B + \text{CIN})$
0x3c	011 11 00	C	C	0	$C \pm (C + \text{CIN})$
0x3e	011 11 10	C	C	P	$C \pm (C + P + \text{CIN})$
0x3f	011 11 11	C	C	A:B	$C \pm (A:B + C + \text{CIN})$
0x50	101 00 00	Shift(PCIN)	0	0	$\text{Shift}(\text{PCIN}) \pm \text{CIN}$
0x52	101 00 10	Shift(PCIN)	0	P	$\text{Shift}(\text{PCIN}) \pm (P + \text{CIN})$
0x53	101 00 11	Shift(PCIN)	0	A:B	$\text{Shift}(\text{PCIN}) \pm (A:B + \text{CIN})$
0x55	101 01 01	Shift(PCIN)	Note 1		$\text{Shift}(\text{PCIN}) \pm (A \times B + \text{CIN})$
0x5c	101 11 00	Shift(PCIN)	C	0	$\text{Shift}(\text{PCIN}) \pm (C + \text{CIN})$
0x5e	101 11 10	Shift(PCIN)	C	P	$\text{Shift}(\text{PCIN}) \pm (C + P + \text{CIN})$
0x5f	101 11 11	Shift(PCIN)	C	A:B	$\text{Shift}(\text{PCIN}) \pm (A:B + C + \text{CIN})$
0x60	110 00 00	Shift(P)	0	0	$\text{Shift}(P) \pm \text{CIN}$
0x62	110 00 10	Shift(P)	0	P	$\text{Shift}(P) \pm (P + \text{CIN})$
0x63	110 00 11	Shift(P)	0	A:B	$\text{Shift}(P) \pm (A:B + \text{CIN})$
0x65	110 01 01	Shift(P)	Note 1		$\text{Shift}(P) \pm (A \times B + \text{CIN})$
0x6c	110 11 00	Shift(P)	C	0	$\text{Shift}(P) \pm (C + \text{CIN})$
0x6e	110 11 10	Shift(P)	C	P	$\text{Shift}(P) \pm (C + P + \text{CIN})$
0x6f	110 11 11	Shift(P)	C	A:B	$\text{Shift}(P) \pm (A:B + C + \text{CIN})$

The DSP 48 Instruction Set

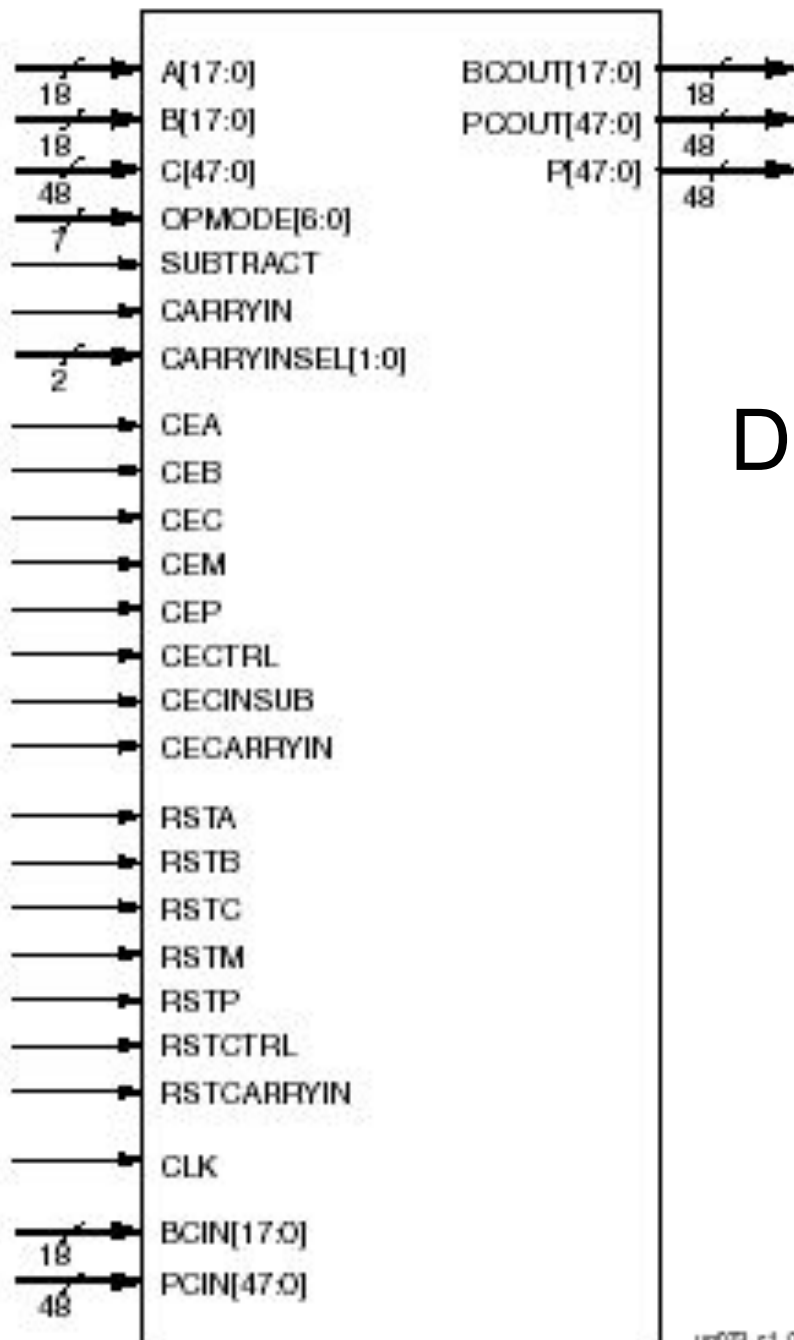


DSP 48 Primitive Symbol

DSP 48 Timing

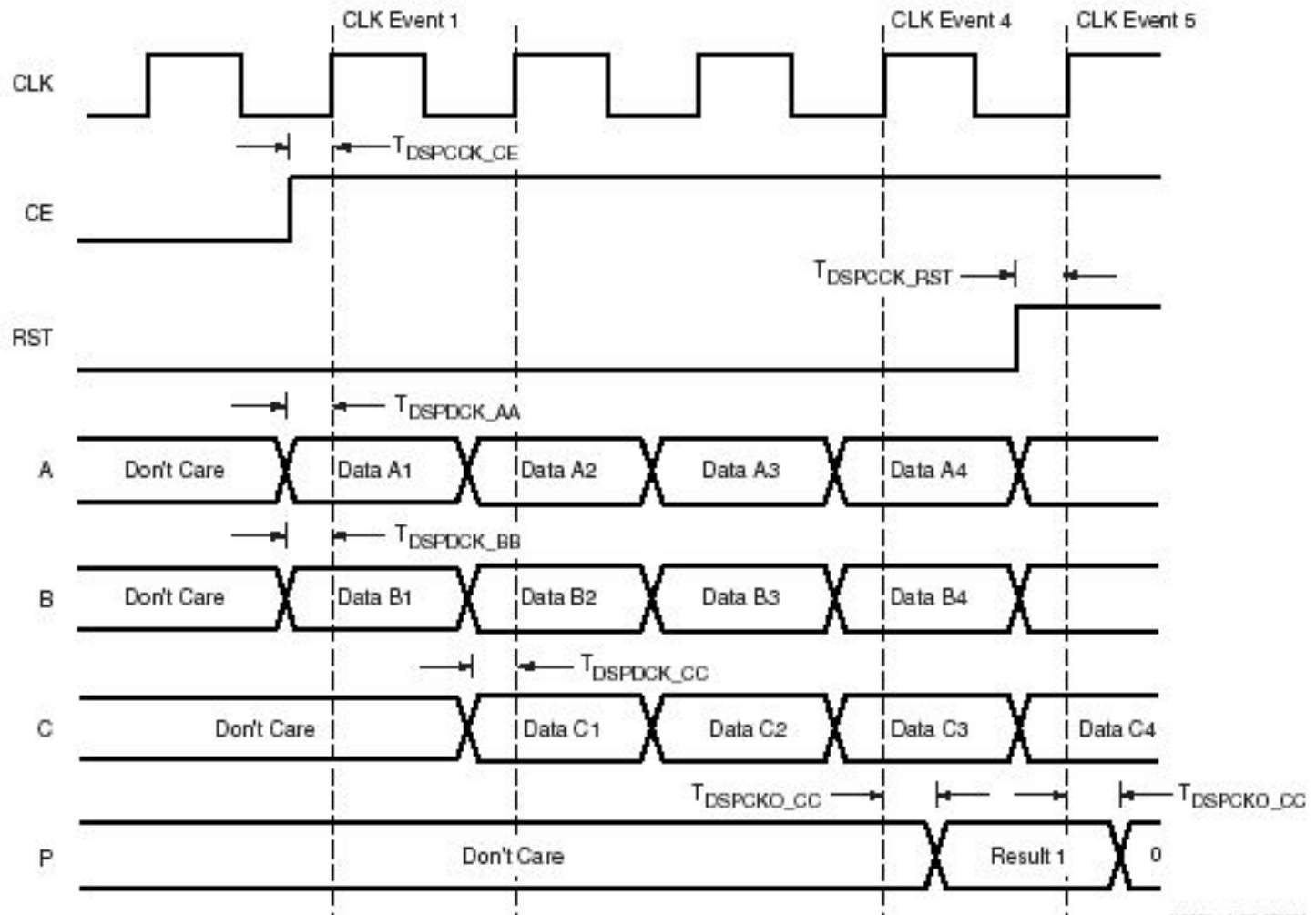

Doing Other Things - SQRT

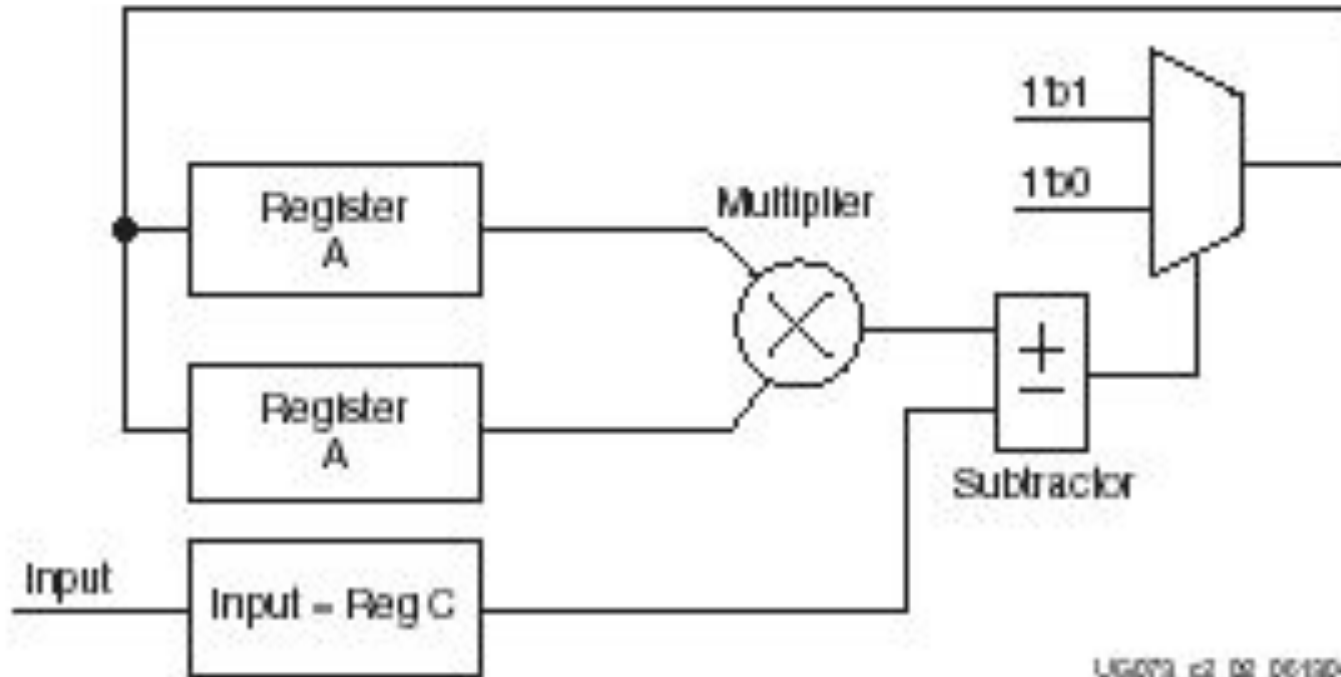


Important to Do Other Things with DSP 48

- Divider
- Large multiplexer
- Barrel shifters
- Two's Complement converters
- Large counters
- Etc.


DSP 48 Handbook available on Xilinx website

Virtex 5 DSP48E

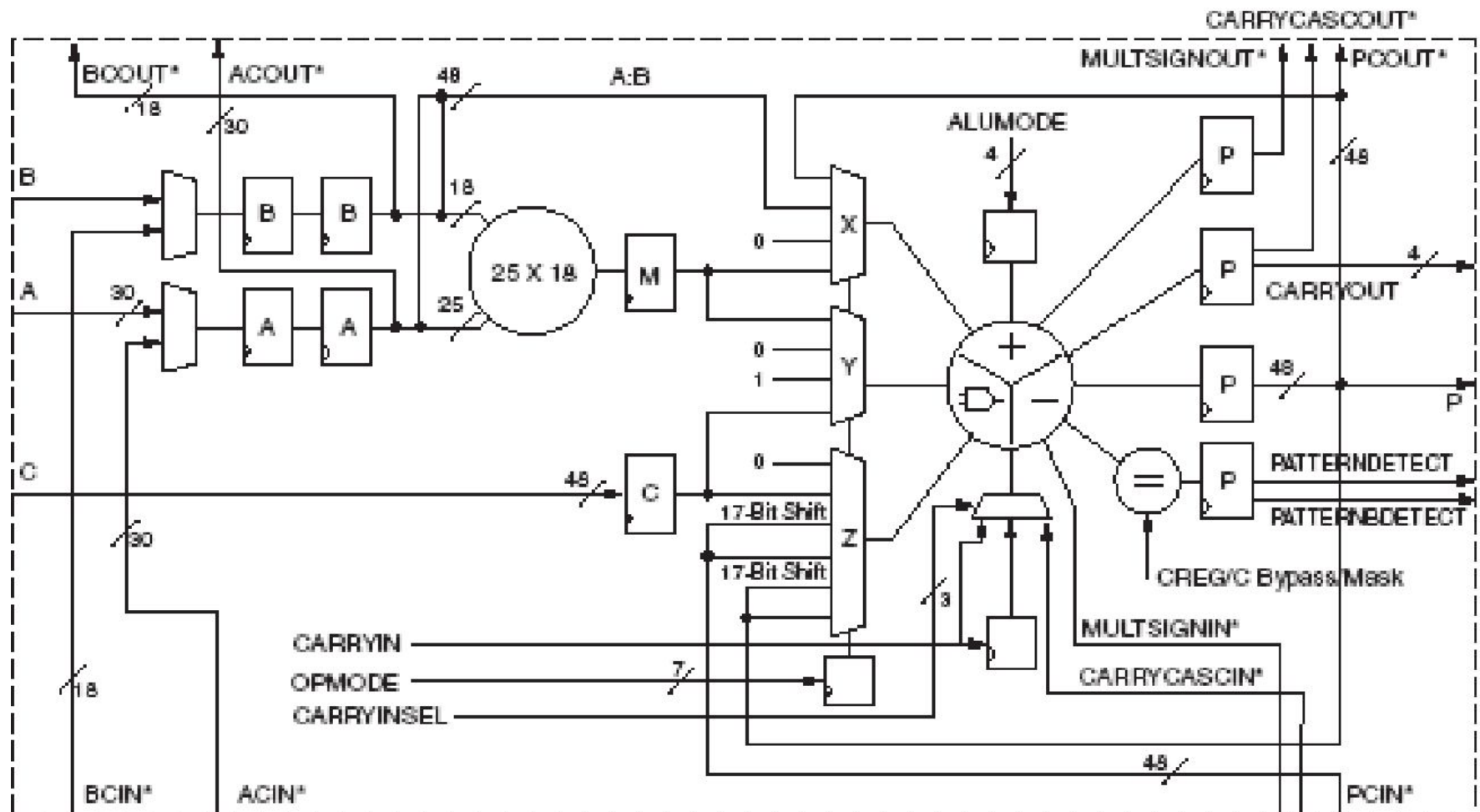

^aThese signals are dedicated routing paths internal to the DSP48E column. They are not accessible via fabric routing resources.

Simpler DSP48E

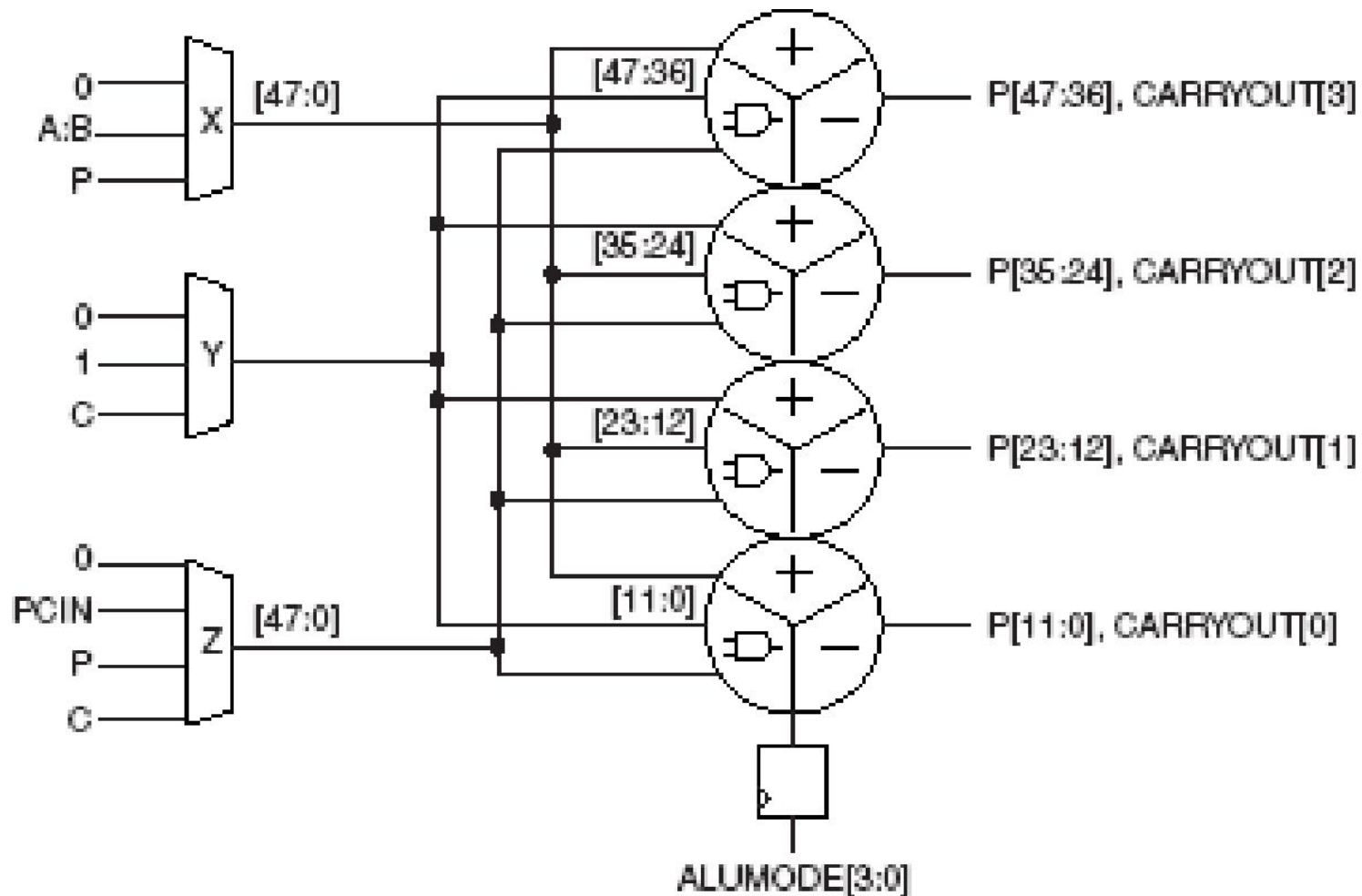

Other Useful Functions

- Building up “word wise” logic
 - AND,OR
- Same list as for the DSP48

Support

- Xilinx offers an elaborate (read:\$) set of tools that interface to the MatLab toolchain
- Focused on DSP algorithm development
- Permits “hardware in the loop” simulation
- Also working on higher level compile tools as DSP developers tend to be more mathematicians and less “hardware designers” (read: C, C++ oriented)